



abc

Basic Connections

Alberto Piganti





ABC: Basic Connections

by Alberto Piganti

Copyright © 2017 Alberto Piganti. All rights reserved.

Printed in Spain by Artes Graficas Mawijo, S.A.

Published by Alberto Piganti – ESY3370544T

C/ Perú 4 planta 1 oficina 2

28290 Las Rozas, Madrid (Spain)

PighiXXX books can be purchased for educational, business, or promotional use. For more information, distribution, translations or bulk sales please contact our sales department at contact@abcthebook.com

Printing History:

November 2017:

First Edition

The PighiXXX logo is a registered trademark of Alberto Piganti. Other product and company names mentioned herein may be the trademarks of their respective owners. Rather than use a trademark symbol with every occurrence of a trademarked name, we are using the names only in an editorial fashion and to the benefit of the trademark owner, with no intention of infringement of the trademark.

ISBN: 978-84-946930-0-7





abc

Basic Connections

Important Message:

Your safety is your own responsibility, including proper use of equipment and safety gear, and determining whether you have adequate skill and experience to complete a specific project. In order to show the project steps more clearly, some illustrations do not depict safety precautions or equipment. Electricity and other resources are dangerous unless used properly and with adequate precautions, including safety gear. The projects included in this book are not intended for use by unsupervised children.

Use the instructions and suggestions in ABC: Basic Connections at your own risk. PighiXXX and the author disclaim all responsibility for any resulting damage, injury, or expense.





Dedicated to the people who have always believed in me:
My wife Olga and my mother





Table of Contents

Basic Concepts

Ohm's Law	A1
Resistors	A2
Capacitors	A3
Components in Series	A4
Components in Parallel	A5
Diodes	A6
Transistors	A7

Reference

E24 Resistors	R1
E48 Resistors	R2
E96/E192 Resistors	R3
Capacitors (Markings)	R4
Capacitors (Color Code)	R5
NPN Transistor Selector	R6
PNP Transistor Selector	R7

Basic Connections

LED	1
Test Code	1
Typical LED Current Limiting Resistor Values ...	1
Alternating LEDs	2
Bi-Color LED	3
2-Lead LEDs	3
3-Lead LEDs	3





Basic Connections

LED Cluster	4
RGB LEDs	5
Common Cathode Configuration	5
Common Anode Configuration	5
LED Strip	6
Digitally-Addressable LEDs	7
Charlieplexing	8
LED Matrix	9
Multiple LED Clusters	10
ULN2803 Pinout	10
ULN2803 Port Schematic	10
Decoder/Demultiplexer	11
74HC238 Pinout	11
Connecting Multiple 74HC238	11
Shift Register	12
74HC595 Pinout	12
Connecting Multiple 74HC595	12
Input Shift Register Via SPI	13
74HC165 Pinout	13
Connecting Multiple 74HC165	13
MAX7219 7-Segment Display Driver	14
MAX7219 Pinout	14
Calculating the Value of Rx	14
LEDM88G 8x8 LED Matrix	15
LEDM88G 8x8 LED Matrix Schematic	15
Connecting Multiple MAX7219	15
TLC5940 LED Driver	16
TLC5940 Pinout	16
Calculating the Value of Rx	16
Connecting LEDs	16
Connecting Servos	16
Connecting High-Power LEDs	16
Connecting Multiple TLC5940	16
7-Segment Display	17





Basic Connections

4-Digit 7-Segment Display	18
I/O Expander	19
MCP23017 Pinout	19
Connecting a LED	19
Connecting a Pushbutton	19
Analog Mux/Demux	20
4051 Pinout	20
Doubling the Number of Ports	20
DC Light Bulb: Low-Power Load	21
DC Light Bulb: High-Power Load	22
DC Motor	23
Solenoid	24
Relay	25
Test Code	25
Status LED	25
Opto-Isolated Relay	26
Logic-Level MOSFET	27
Non-Logic-Level MOSFET	28
Servo	29
Magnetic Buzzer	30
With External Power Supply	31
Piezo Buzzer	31
Note Frequency	31
IR Detector	32
Common IR Detectors	32
IR Emitter	33
Constant-Current IR Emitter	34
HD44780-Based LCD	35
HD44780-Based LCD Pinout	35
LCD Backlight Control	35
HD44780-Based LCD Via I2C	36
PCF8574 Pinout	36
I2C Pull-Up Resistors	36
Nokia 5110 LCD	37





Basic Connections

OLED LCD	38
UC1701 128x64 LCD	39
ST7032i LCD	40
DS Touchscreen	41
Simple Touch Sensor	42
Pushbutton	43
Test Code	43
Using Internal Pull-Up Resistors	43
Pushbutton to 12V	44
Toggle Switch	45
Using One Analog Input	45
Multiple Pushbuttons	46
Rotary Encoder: Internal Pull-Up Resistors	47
Rotary Encoder	48
Simple Debouncing Circuit	49
Debouncing: Theory	50
Debouncing	51
Rotary Encoder Debouncing	52
74LS14 & 74LS74 Pinout	52
Keypad	53
Keypad Pinout	53
Membrane Keypad	54
Membrane Keypad Pinout	54
Keypad With 1 Analog Pin	54
Thumbwheel Switch	55
Rotary Switch	56
PS/2 Keyboard	57
Trimmer	58
Photoresistor (LDR)	59
Phototransistor	60
Opto-Isolated DC Input	61
Opto-Isolated AC Input	62
SPST CMOS Analog Switch	63
AC Current Sensor	64





Basic Connections

LM34/LM35 Temperature Sensor	65
LM34/LM35 Temperature Sensor: Full Range	66
TMP36 Temperature Sensor	67
MCP9700 Temperature Sensor	68
LM335 Temperature Sensor	69
Thermocouple	70
DHT11 Temperature & Humidity Sensor	71
DHT22 Temperature & Humidity Sensor	72
DHT11/DHT22 2-Wire Connection	73
DS18B20 Temperature Sensor	74
NTC Thermistor	75
RTD Temperature Sensor	76
Gas Sensor (MQ Series)	77
Sharp GP2Y0A21 Distance Sensor	78
DIY microSD Card Reader	79
SD Card Pinout	79
SD Card	80
SD Card Socket Pinout	80
3-Wire Computer Fan	81
4-Wire Computer Fan	82
Bi-Directional Level Converter	83
Voltage Divider Connections	83
3.3V to 5V Level Shifter	84
5V to 3.3V Level Shifter	84
4050 Level Shifter Pinout	85
74HC125 Level Shifter Pinout	86
Voltage Divider	87
TTL-CMOS Level Shifter	88
I/O Pin Protection	89
Using a Zener Diode	89
Using Clamping Diodes	89
I/O Pin Filtering & Protection	90
Two Microcontroller Boards	90
VGA Output	91





Basic Connections

Composite Output	92
Single-Transistor Amplifier	93
Audio Amplifier	94
Preamplifier	95
Microphone	96
Simple 5V Power Supply	97
Simple 3.3V Power Supply	98
Simple Adjustable Power Supply	99
Full-Wave Rectifier	100
TRIAC	101
Zero-Crossing Detector	102
Solid-State Relay	103
RC Snubber Network	104
Soft Latching Power ON Circuit	105
Reverse Voltage Protection	106
RS-485 Interface	107
Node Termination Jumpers	107
MIDI IN	108
MIDI OUT	109
Multiple MIDI OUT	110
MIDI Pinout	110
DMX Interface	111
DMX Pinout	111
RS-232 Interface	112
MAX232 Pinout	112
RS-232 Pinout	112
RTC	113
EEPROM	114
Digital Potentiometer	115
Buffer	116
Hall Effect Sensor	117
Spectrum Analyzer	118
Flex Sensor	119
Piezo Sensor	120





Basic Connections

Op-Amp Threshold Switch	121
DAC	122
H-Bridge	123
L293D Pinout	123
Unipolar Stepper Motor	124
Stepper Motor Basic Concepts	124
Bipolar Stepper Motor	125
Step Sequence	125
Stepper Motor Phases	126

Pinouts

ATmega328P	P1
ATtiny85	P2
ICSP Programming	P2
ATtiny84	P3
ICSP Programming	P3
ATtiny2313	P4
ESP8266	P5
ESP-12S Minimal Setup	P5
FTDI	P6
ICSP	P7

Bifold

UNO Pinout	B1
Leonardo Pinout	B2
FLUO Pinout	B3
Nano Pinout	B4
NodeMCU Pinout	B5
ESP-WROOM-32 Pinout	B6
DIY Microcontroller Board	B7
Stepper Motors	B8
L298N Motor Driver	B9








Graphic Symbols




Resistor

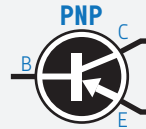

PNP Transistor




Trimmer or Potentiometer

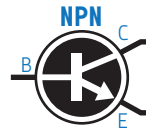

NPN Transistor




Ceramic Capacitor

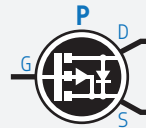

P-Channel MOSFET



Electrolytic Capacitor

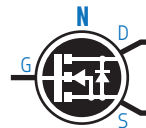


N-Channel MOSFET



Phototransistor



TRIAC

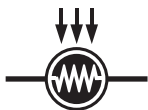

Photoresistor (LDR)



NTC Thermistor







Crystal



LED

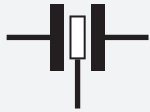


Resonator

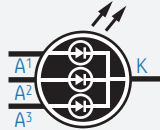

Common Cathode
RGB LED




Silicon
Diode

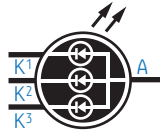

Common Anode
RGB LED




Zener
Diode

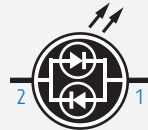

Bi-Color
LED



Schottky
Diode

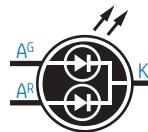

Bi-Color
LED



IR Emitter



Battery



IR Detector




Fuse





Pushbutton

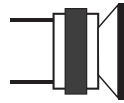


Buzzer



Switch (SPST)



Piezo Buzzer

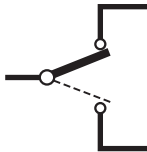


Switch (SPDT)




Piezo Element



Jumper

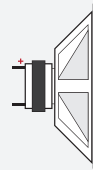

Speaker

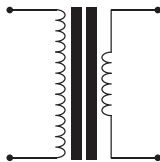

Transformer




Microphone




Bridge Rectifier



Device

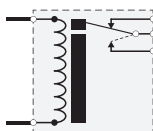

Relay

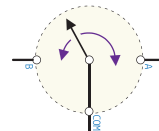

Encoder





Supply



Crossing



Ground



Connection




IN/OUT



Junction

Online Content

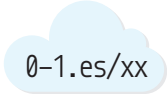You can download additional information, support files and code related each schematic from the URLs on the cloud icons.



0-1.es/xx

We have a web page for this book where we list errata, examples, and any additional information:

abcthebook.com

For technical questions about this book, please contact our support team at:

contact@abcthebook.com





Conventions

This book uses American English spelling and the decimal point as the decimal mark. Although the International System of Units prescribes inserting a space between a number and a unit of measurement, such spaces are omitted in this book for aesthetic reasons.

The following conventions are used in this book:



Standard Input/Output Signal



PWM Input/Output Signal



Interrupt Pin



Analog Input/Output Signal



Information

Useful tips about the circuit



Caution

Useful tips about common pitfalls and limitations of the circuit



Stop

Useful advice to help you avoid destroying any component



Information

Useful information about the circuit



Device Pin Name

Used also in pinout diagrams



Pin Name





Acknowledgments

I am most grateful to a great number of reviewers for their constructive criticism and suggestions. I am also indebted to the many authors whose books or websites I have consulted over the years.

This book has been realized by the effort and skill of many people.

I thank Raffaele Piacente (AKA Testato) for his excellent proofreading and testing work.


Thanks to Adafruit and Limor Fried for her support since the earliest days and for believing in my work.

On behalf of everyone who has downloaded user-contributed Arduino™ libraries, I would like to thank the authors who have generously shared their knowledge.

A big thanks to the entire Arduino™ community and to all my supporters that encourage me daily to create new content. Thanks to my friend Luis Estrella who has always believed in me and helped me in this publishing venture. And last, but not least, thanks to my wife Olga for her patience in the face of deadline-induced irritability.

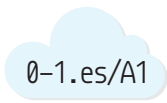And above all, thanks to all of you who supported us on our crowdfunding campaign. Thank you for making it possible!





A1

Ohm's Law

Basic Concepts

Ohm's law is one of the most fundamental relationships found in electric circuits: for a given resistance, current is directly proportional to voltage. In other words, if the voltage through a circuit with a fixed resistance increases, the current increases. If the voltage decreases, the current decreases as well. Ohm's law is expressed with a simple mathematical formula:

$$V = I \times R$$

Where **V** stands for voltage (in volts), **I** stands for current (in amperes), and **R** stands for resistance (in ohms). Ohm's law is very useful because it lets you calculate an unknown voltage, current, or resistance. If you know two of these three quantities you can calculate the third.

Known values	Resistance (R)	Current (I)	Voltage (V)	Power (P)
Current & Resistance			$V = I \times R$	$P = I^2 \times R$
Voltage & Current	$R = V / I$			$P = V \times I$
Power & Current	$R = P / I^2$		$V = P / I$	
Voltage & Resistance		$I = V / R$		$P = V^2 / R$
Power & Resistance		$I = \sqrt{P / R}$	$V = \sqrt{P \times R}$	
Voltage & Power	$R = V^2 / P$	$I = P / V$		






A1

0-1.es/A1


Ohm's Law

Basic Concepts

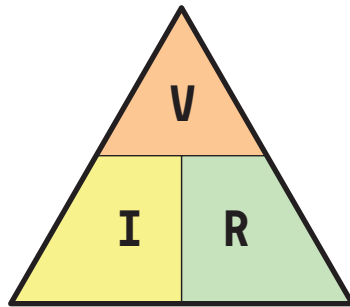
It is easier to remember this Ohm's law relationship by using pictures. Here the three quantities of **V**, **I** and **R** have been superimposed onto a triangle (called the Ohm's Law Triangle). This arrangement represents the position of each quantity within the Ohm's law formulas, making it easier to remember.



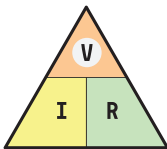
Transposing the standard Ohm's Law equation above will give us the following combinations of the same equation:



$$V = I \times R$$

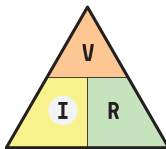

$$I = \frac{V}{R}$$

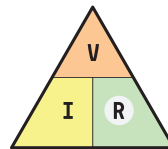

$$R = \frac{V}{I}$$






0-1.es/A1

A1


Ohm's Law

Basic Concepts


Electric Power (**P**) is the rate at which energy is absorbed or produced within a circuit. Electric power is measured in watts (**W**), that is, joules per second. A source of energy will supply power while the connected load absorbs it. A light bulb, for instance, would absorb power and convert it into both heat and light. The higher its value or rating in watts, the more electrical power it is likely to demand.

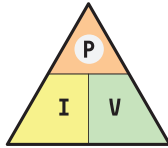


$$P = I \times V$$

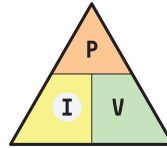

$$I = \frac{P}{V}$$

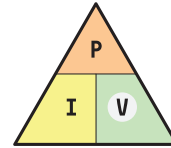

$$V = \frac{P}{I}$$

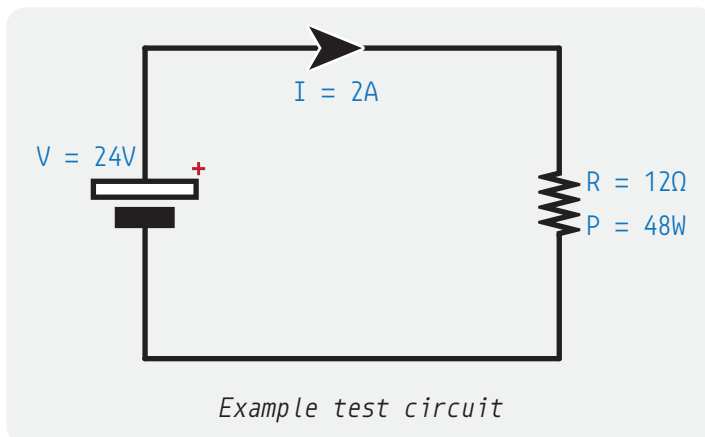





A1

0-1.es/A1

Ohm's Law

Pie Chart Reference

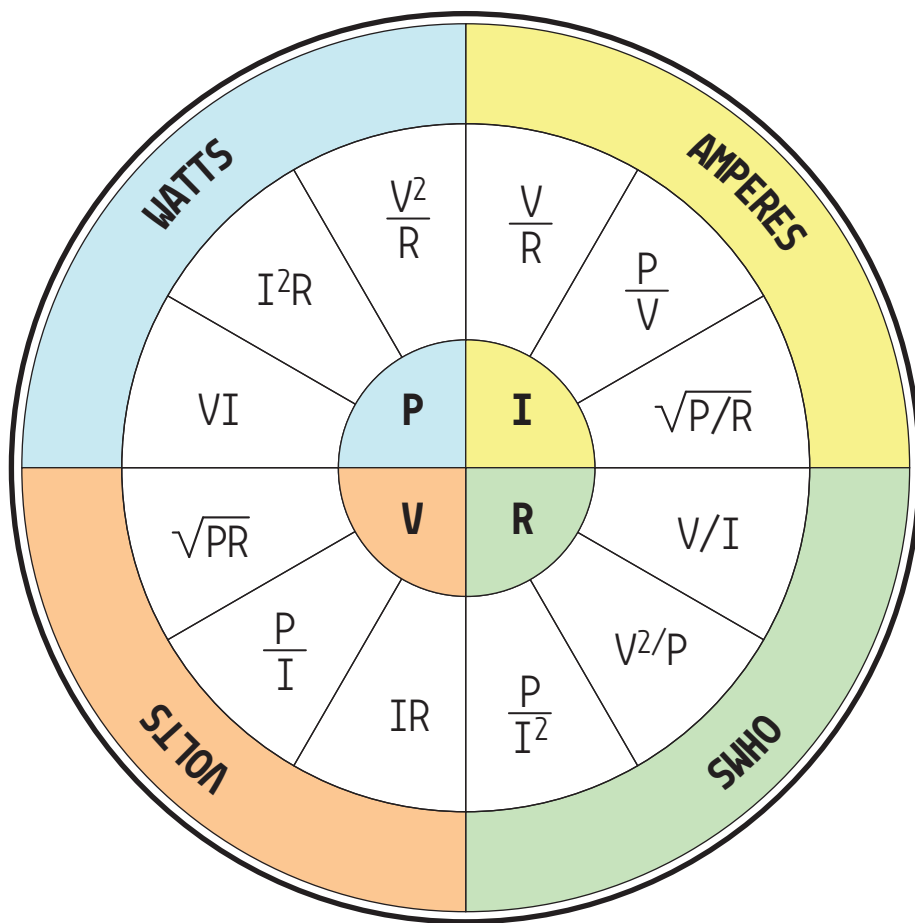

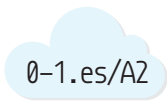


A2

Resistors

Basic Concepts

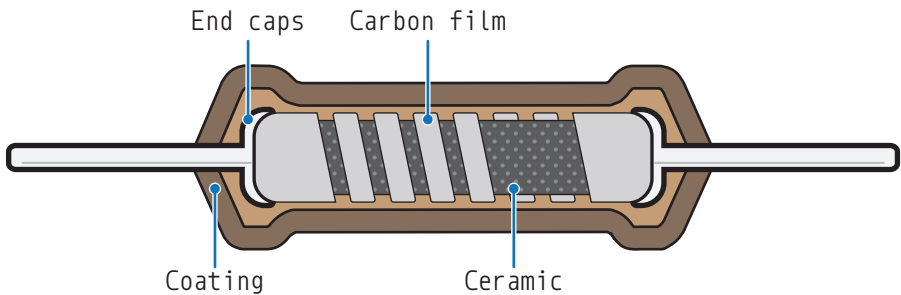Conductors are a materials that allow current to flow through them and insulators are materials that don't. The key factor that determines whether a material is a conductor or an insulator is how easily its atoms give up electrons to move charge along. Most atoms are very attached to their outermost electrons, and are therefore good insulators. But some atoms don't, making them good conductors.



If a conductor and an insulator are mixed together, the resulting material would not conduct current very well. Such a material would have an inherent resistance, resisting the flow of current through it. The degree to which the material resists current flow depends on its exact mixture of elements. A conducting material such as carbon might be mixed with an insulating material such as ceramic. If the mix is mostly carbon, the resistance of the mixture will be low. Whereas if the mix is mostly ceramic, its resistance will be high.






A2

0-1.es/A2

Resistors

Basic Concepts

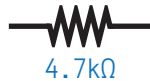Resistance is measured in ohms, represented by the Greek letter omega (Ω). The ohm is defined as the amount of resistance required to allow one ampere of current to flow when one volt of potential is applied to the circuit. In other words, if you connect a 1-ohm resistor across the terminals of a 1-volt battery, one amp of current will flow through the resistor.



In schematic diagrams, resistors are represented by a jagged line, with its resistance value typically written next to the resistor symbol.

The abbreviations k (for kilo) and M (for mega) are used for thousands and millions of ohms. Thus, a 1,000 ohm resistance is written as 1 k Ω , and a 1,000,000 ohm resistance is written as 1 M Ω .

The resistance value of a resistor can be determined by examining the color codes that are painted as stripes on its outer surface. These stripes indicate its resistance value in ohms and its tolerance, which indicates the maximum variation of the real resistance value compared to the value represented by the stripes.





0-1.es/R1

R1

E24 Resistors

Color Code



1ST Digit 2ND Digit Multiplier Tolerance

Black	0	0	x1	
Brown	1	1	x10	
Red	2	2	x100	
Orange	3	3	x1k	
Yellow	4	4	x10k	
Green	5	5	x100k	
Blue	6	6	x1M	
Violet	7	7		
Gray	8	8		
White	9	9		
Gold			x0.1	±5%
Silver				±10%






R1

0-1.es/R1


E24 Resistors

Common Standard Values

 1Ω	 10Ω	 100Ω	 1kΩ	 10kΩ	 100kΩ	 1MΩ
 1.2Ω	 12Ω	 120Ω	 1.2kΩ	 12kΩ	 120kΩ	 1.2MΩ
 1.5Ω	 15Ω	 150Ω	 1.5kΩ	 15kΩ	 150kΩ	 1.5MΩ
 1.8Ω	 18Ω	 180Ω	 1.8kΩ	 18kΩ	 180kΩ	 1.8MΩ
 2.2Ω	 22Ω	 220Ω	 2.2kΩ	 22kΩ	 220kΩ	 2.2MΩ
 2.7Ω	 27Ω	 270Ω	 2.7kΩ	 27kΩ	 270kΩ	 2.7MΩ
 3.3Ω	 33Ω	 330Ω	 3.3kΩ	 33kΩ	 330kΩ	 3.3MΩ
 3.9Ω	 39Ω	 390Ω	 3.9kΩ	 39kΩ	 390kΩ	 3.9MΩ
 4.7Ω	 47Ω	 470Ω	 4.7kΩ	 47kΩ	 470kΩ	 4.7MΩ
 5.6Ω	 56Ω	 560Ω	 5.6kΩ	 56kΩ	 560kΩ	 5.6MΩ
 6.8Ω	 68Ω	 680Ω	 6.8kΩ	 68kΩ	 680kΩ	 6.8MΩ
 8.2Ω	 82Ω	 820Ω	 8.2kΩ	 82kΩ	 820kΩ	 8.2MΩ

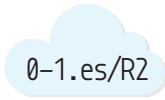 Partial list, full version available online






R2

E48 Resistors

Color Code

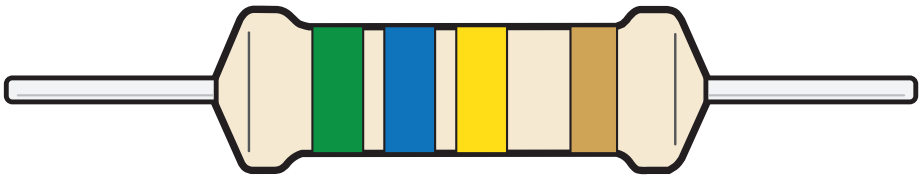

	1 ST Digit	2 ND Digit	Multiplier	Tolerance
Black	0	0	x1	
Brown	1	1	x10	
Red	2	2	x100	±2%
Orange	3	3	x1k	
Yellow	4	4	x10k	
Green	5	5	x100k	
Blue	6	6	x1M	
Violet	7	7		
Gray	8	8		
White	9	9		
Gold			x0.1	±5%
Silver			x0.01	±10%





R3

0-1.es/R3

E96/E192 Resistors

Color Code



	1 ST Digit	2 ND Digit	3 RD Digit	Multiplier	Tolerance
Black	0	0	0	x1	
Brown	1	1	1	x10	±1%
Red	2	2	2	x100	±2%
Orange	3	3	3	x1k	
Yellow	4	4	4	x10k	
Green	5	5	5	x100k	±0.5%
Blue	6	6	6	x1M	±0.25%
Violet	7	7	7	x10M	±0.10%
Gray	8	8	8		
White	9	9	9		
Gold				x0.1	±5%
Silver				x0.01	±10%






A3

Capacitors

Basic Concepts

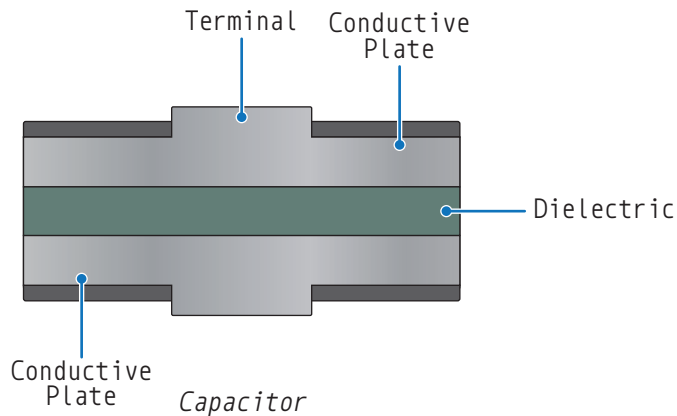Capacitors are components that store electric energy as an electric field. They consist of two plates made of a conducting material such as silver or aluminum, separated by a thin insulating material such as Mylar or ceramic. The two conducting plates are connected to terminals so that a voltage can be applied across them.



Because the two plates are separated by a dielectric, that is, an electrical insulator that can be polarized by an electric field, a closed circuit is not formed. Nevertheless, current flows for an instant. When the voltage from a source such as a battery is connected, the negative terminal of the battery immediately begins to push electrons toward one of the plates.






A3

Capacitors

Basic Concepts

At the same time, the positive side of the battery voltage begins to pull electrons (negative charges) away from the second plate. The electric field that builds up between the two plates allows current to flow. As the plate on the negative side of the circuit fills with electrons, the electric field created by them push the electrons away from the plate on the other side of the dielectric, toward the positive side of the battery voltage.

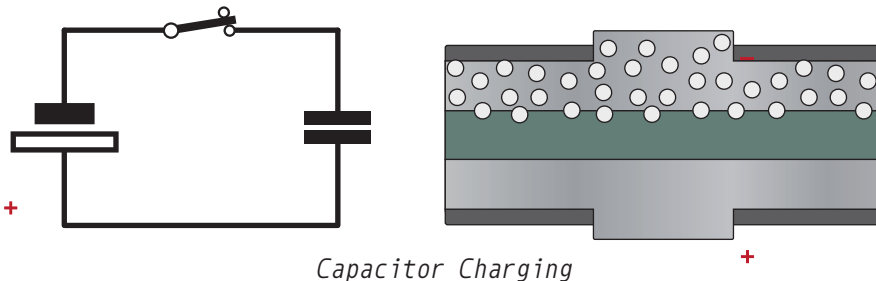

Capacitor Charging

As current flows, the negative plate of the capacitor builds up an excess of electrons, whereas the positive side develops a corresponding deficiency of electrons. At the same time, the voltage between the two plates increases proportionally to the difference in charge between the two plates.

The voltage continues to increase until the capacitor voltage equals the battery voltage. Once they are the same, current stops flowing through the circuit, and the capacitor is said to be charged.







0-1.es/A3

A3

Capacitors



Basic Concepts

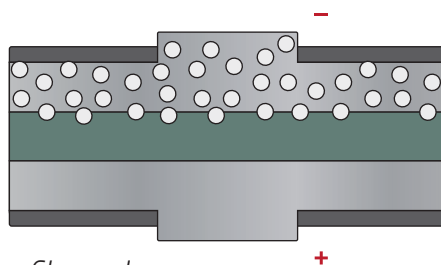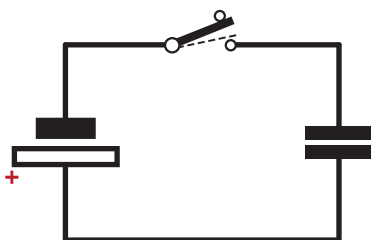Once the capacitor has been charged it will acquire the same voltage as the battery, and the charge will remain in the capacitor even when disconnected. The amount of charge capacitors can store is proportional to the area of their plates.



Capacitor Charged

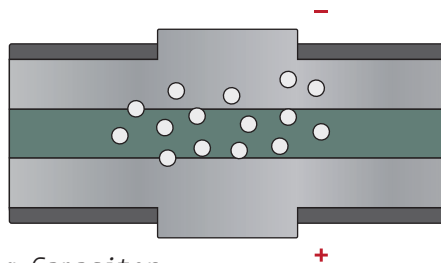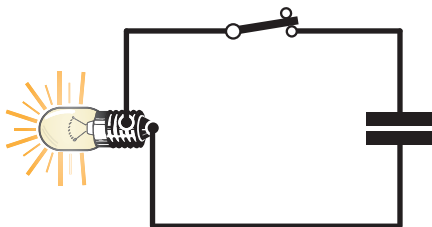When a charged capacitor is connected to a circuit, the voltage across its plates will drive current through the circuit, discharging the capacitor.



Discharging Capacitor





A3


0-1.es/A3

Capacitors

Basic Concepts

Capacitance is the electrical property of a capacitor that defines its ability to store an electric charge onto its two plates, with the unit of capacitance being the farad (**F**). A 1-farad capacitor can store 1 coulomb of charge at 1 volt. A coulomb is 6.25×10^{18} (6.25 billion billion) electrons. Based on this definition, one ampere represents a rate of electron flow of 1 coulomb of electrons per second.

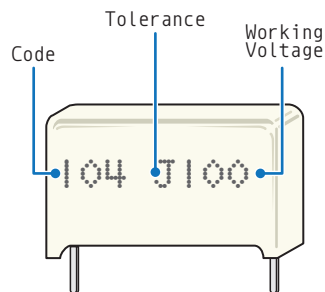As in the case of resistors, capacitors also have a manufacturing tolerance for their capacitance value.



If there is enough room on the package, most manufacturers print the capacitance value directly on the capacitor along with other information such as the voltage rating and the tolerance.






0-1.es/R4

R4

Capacitors

Markings

Multiplier	Multiply by
0	1
1	10
2	100
3	1,000
4	10,000
5	100,000
8	0,01
9	0,1

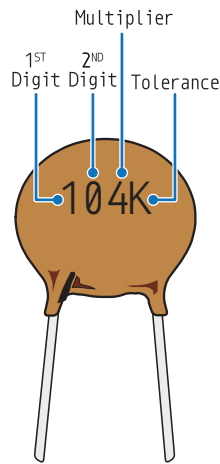

$$10 \times 10,000 = 100,000 \text{ pF}$$
$$100,000 \text{ pF} = \mathbf{0.1 \mu F \pm 10\%}$$

Letter	Tolerance >10pF	Tolerance <10pF
B		$\pm 0.1 \text{ pF}$
C		$\pm 0.25 \text{ pF}$
D		$\pm 0.5 \text{ pF}$
F	$\pm 1\%$	$\pm 1 \text{ pF}$
G	$\pm 2\%$	$\pm 2 \text{ pF}$
H	$\pm 3\%$	
J	$\pm 5\%$	
K	$\pm 10\%$	
M	$\pm 20\%$	

Conversion Table

picofarads pF	nanofarads nF	microfarads μF
1	0.001	0.000001
10	0.01	0.00001
100	0.1	0.0001
1,000	1	0.001
10,000	10	0.01
100,000	100	0.1
1,000,000	1,000	1
10,000,000	10,000	10
100,000,000	100,000	100






R5

0-1.es/R5

Capacitors Color Code

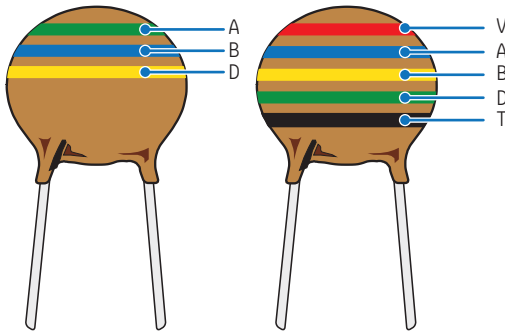

Type	Capacitor Type
J	Dipped tantalum
K	Mica
L	Polyester
M	Electrolytic, 4-band
N	Electrolytic, 3-band

	A	B	D	T		V				
	Digit A	Digit B	Multiplier	Tolerance >10pF	Tolerance <10pF	J	Voltage Rating			N
						K	L	M		
Black	0	0	x1	±20%	±2pF	4	100		10	10
Brown	1	1	x10	±1%	±0.1pF	6	200	100	1.6	
Red	2	2	x100	±2%	±0.25pF	10	300	250	4	35
Orange	3	3	x1k	±3%		15	400		40	
Yellow	4	4	x10k	±4%		20	500	400	6.3	6
Green	5	5	x100k	±5%	±0.5pF	25	600		16	15
Blue	6	6	x1M			35	700	630		20
Violet	7	7				50	800			
Gray	8	8	x0.01	+80% -20%			900		25	25
White	9	9	x0.1	±10%	±1pF	3	1000		2.5	3
Gold			x0.1	±5%			2000			
Silver			x0.01	±10%						






0-1.es/A4

A4

Components in Series

Capacitors

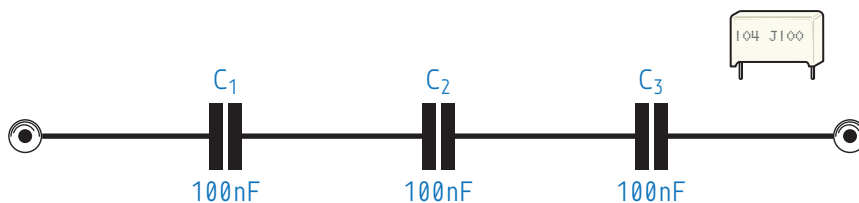


$$C_{TOTAL} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$C_{TOTAL} = \frac{1}{\frac{1}{100} + \frac{1}{100} + \frac{1}{100}}$$

$$C_{TOTAL} = \mathbf{33.33nF}$$

Resistors

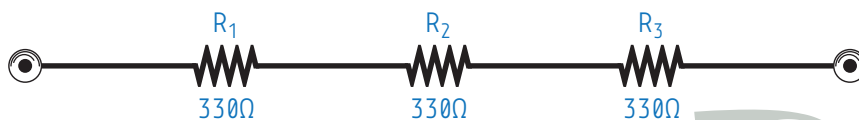

$$R_{TOTAL} = R_1 + R_2 + R_3$$

$$R_{TOTAL} = 330 + 330 + 330$$

$$R_{TOTAL} = \mathbf{990\Omega}$$






A5

0-1.es/A5

Components in Parallel



Capacitors

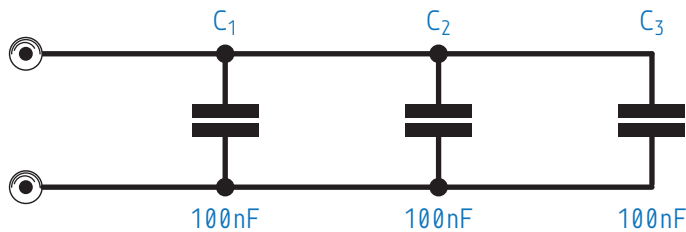

$$C_{TOTAL} = C_1 + C_2 + C_3 \quad C_{TOTAL} = 100 + 100 + 100$$

$$C_{TOTAL} = 300\text{nF}$$

Resistors

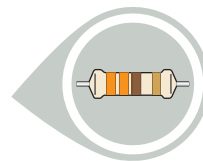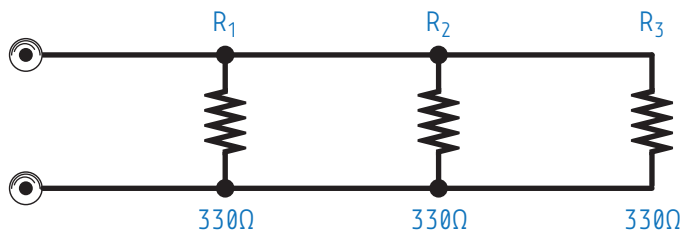

$$R_{TOTAL} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$R_{TOTAL} = \frac{1}{\frac{1}{330} + \frac{1}{330} + \frac{1}{330}}$$

$$R_{TOTAL} = 110\Omega$$







0-1.es/A6

A6

Diodes

Basic Concepts

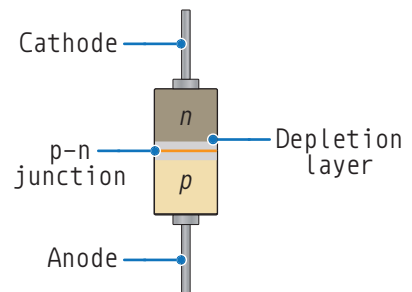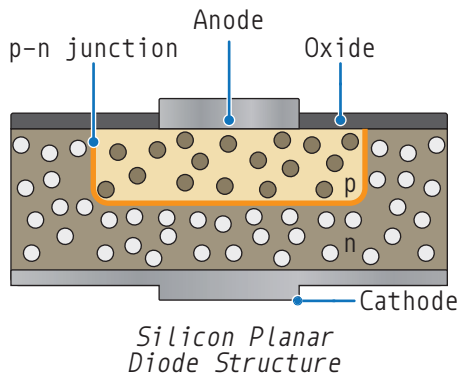Diodes are components made from a combination of a p-type and n-type semiconductor material, most commonly silicon.



The lead attached to the n-type semiconductor is called the cathode. Thus, the cathode is the negative side of the diode. Alternatively, the positive side of the diode, that is, the lead attached to the p-type semiconductor, is called the anode.



In the schematic symbol of the diode, the anode is represented as a triangle and the cathode is represented as a bar. You can think of the anode side of the symbol as an arrow that indicates the direction of conventional current flow, from positive to negative.






A6

0-1.es/A6

Diodes

Basic Concepts

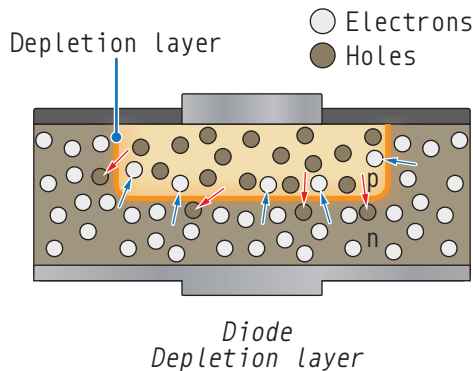When p-type and n-type silicon are placed together during the manufacturing process, a junction called p-n junction is created where the p-type and n-type materials meet. Holes, or lack of electrons, close to the junction in the p-type silicon are attracted into negatively charged n-type material at the other side of the junction.



At the same time, electrons close to the junction in the n-type silicon are attracted to the positively charged p-type silicon. The recombination of holes and electrons produces a narrow region at the junction called the depletion layer.






0-1.es/A6

A6


Diodes

Basic Concepts

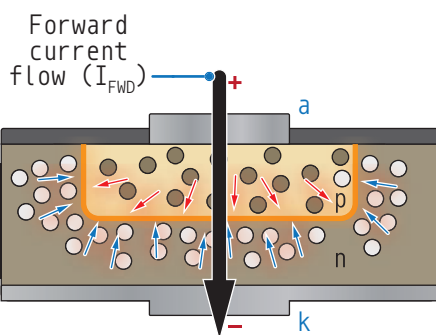When a voltage source is connected to a diode such that the positive side of the voltage source is on the anode and the negative side is on the cathode, the diode becomes conductive and allows current to flow. This configuration is called forward bias.



Diode in Forward Conduction

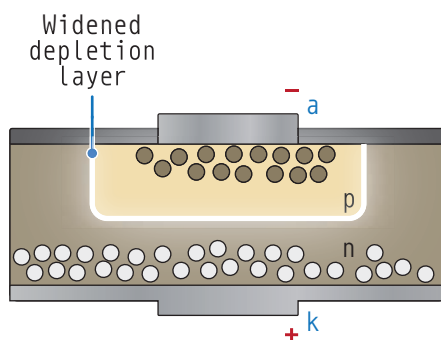

Reverse-Biased Diode

If the direction of the voltage is reversed, when connecting the positive side to the cathode and the negative side to the anode, current doesn't flow. In this case, the diode becomes an insulator. This configuration is called reverse bias.






A6

0-1.es/A6


Diodes

Basic Concepts

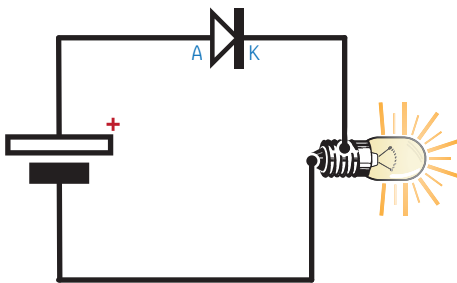Forward and reverse bias can be illustrated by connecting a light bulb to a battery with a diode in series. In the circuit on the left, the diode is forward biased, so current flows through the circuit and the light bulb lights up. In the circuit on the right, the diode is reverse biased, so current does not flow and the light bulb remains off.




Forward bias

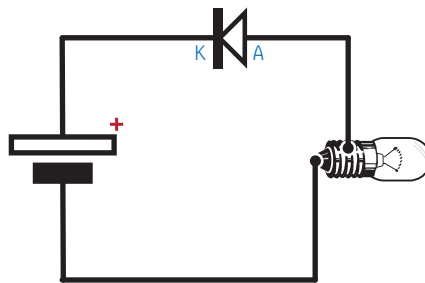

Reverse bias

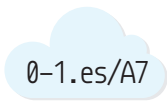When a diode is connected to a circuit, no current can flow between anode and cathode until the anode is made more positive than the cathode by a forward voltage sufficiently high to overcome the natural reverse potential of the p-n junction. This voltage, called forward voltage drop (V_F), is usually around 0.5V.






A7


Transistors

Basic Concepts

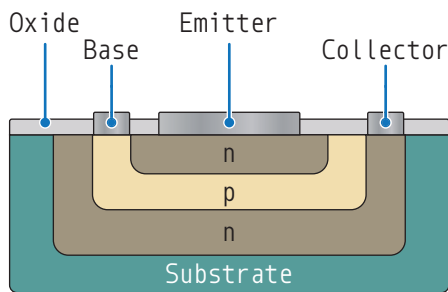Transistors similar to diodes but containing a third layer of either n-type or p-type semiconductor on one end. The interface between each of the three regions forms a p-n junction.



Planar transistor structure

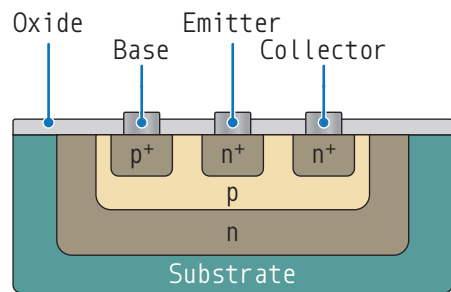

Lateral planar transistor structure

One way in which transistors are made is by sandwiching a p-type semiconductor between two n-type semiconductors. This type of transistors are called NPN because they have three regions: n-type, p-type, and n-type.

Alternatively, PNP transistors are made by sandwiching an n-type semiconductor between two p-type semiconductors.






A7

0-1.es/A7

Transistors

Basic Concepts

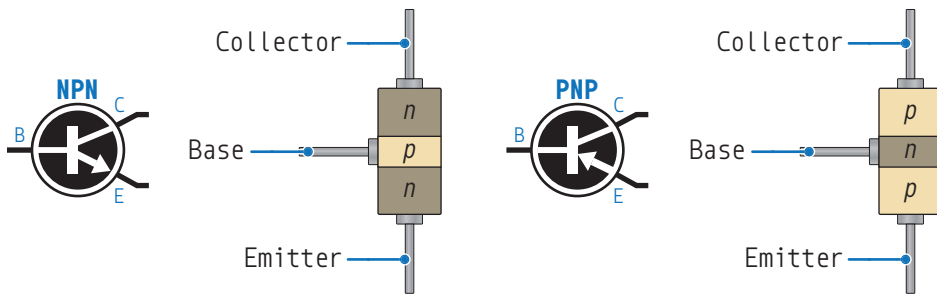Each of the three regions of semiconductor material in a transistor has a lead attached to it. They are called collector, base and emitter respectively.



Collector: Attached to the largest of the semiconductor regions. Current flows through the collector to the emitter as controlled by the base.

Emitter: Attached to the second largest of the semiconductor regions. Current flows from the collector to the emitter when the base voltage allows.

Base: Attached to the middle semiconductor region. This region serves as a valve that controls how much current is allowed to flow through the collector-emitter circuit. When sufficient voltage is applied to the base, current is allowed to flow.






0-1.es/A7

A7


Transistors

Basic Concepts

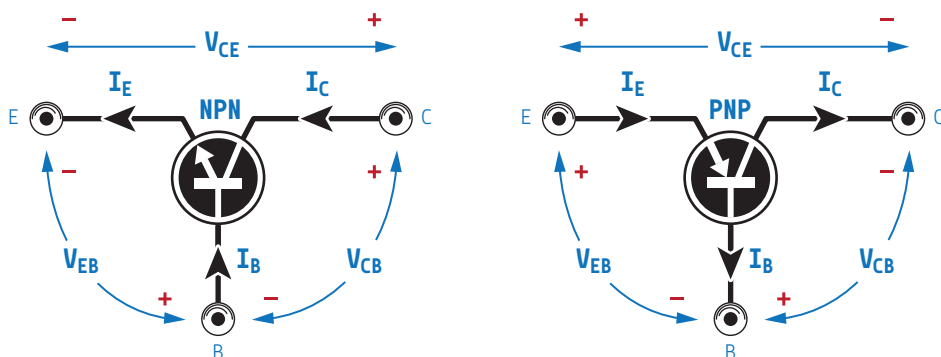Transistors are current-regulating devices that act as a current-controlled switches. The amount of current flowing through them varies proportionally with the amount of biasing voltage applied to their base terminal.



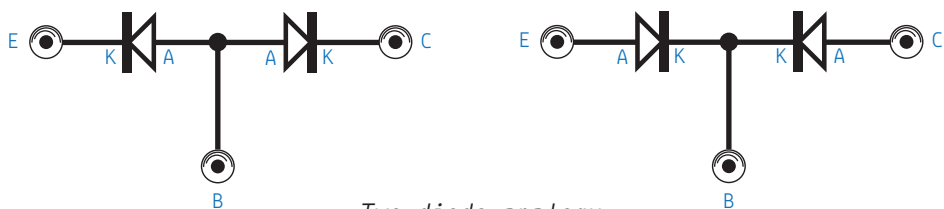The schematic symbols for both transistors have their arrows pointing in the direction of the conventional current flow, between the base terminal and its emitter terminal. The direction of the arrow points from the positive p-type region to the negative n-type region for both transistor types, the same occurs with the standard diode symbol.



Two diode analogy






A7

0-1.es/A7

Transistors

Basic Concepts

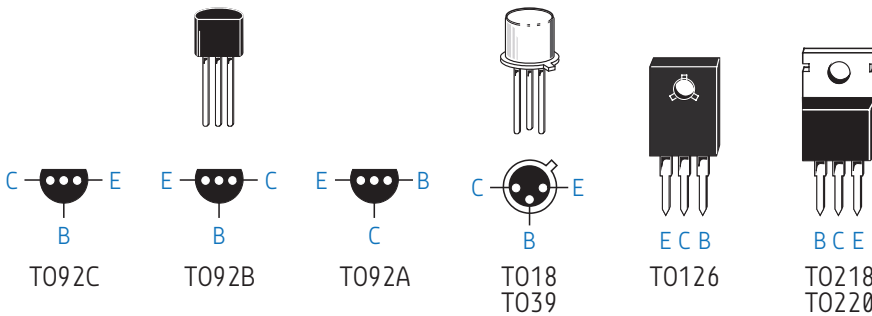Transistors come in a wide variety of physical packages. Package type is primarily dependent upon the required power dissipation of the transistor, with its physical size being proportional to its maximum power dissipation.



Note: It is very important to check the datasheet of each transistor since the pinouts are not standardized.

Symbol	Description
V_{CE}	Collector-Emitter Voltage
V_{EB}	Emitter-Base Voltage
V_{CB}	Collector-Base Voltage
I_E	Emitter Current
I_C	Collector Current
I_B	Base Current
hFE	Current Gain

Important transistor characteristics








0-1.es/R6

R6

Transistor Selector

NPN

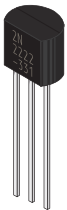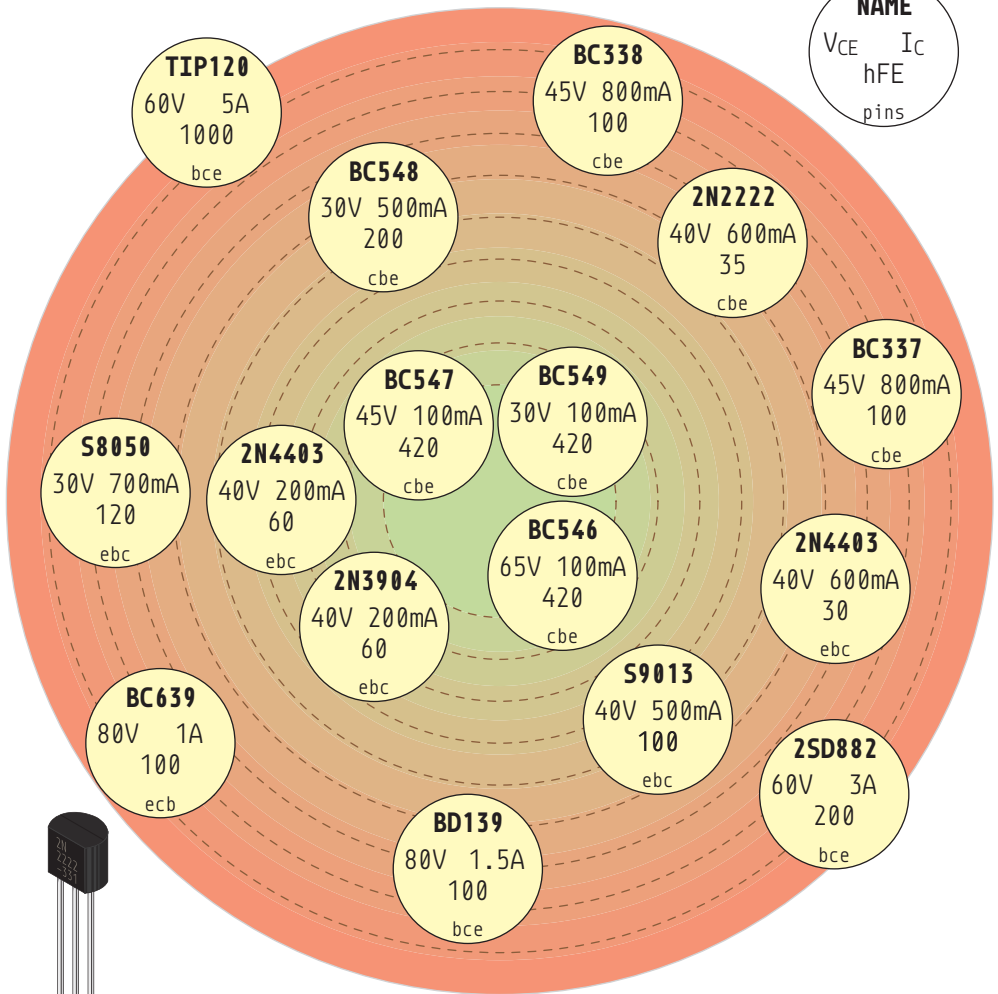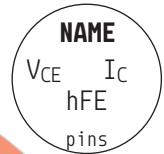





R7

0-1.es/R7

Transistor Selector

PNP

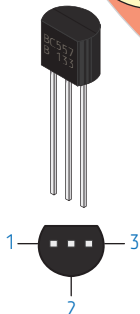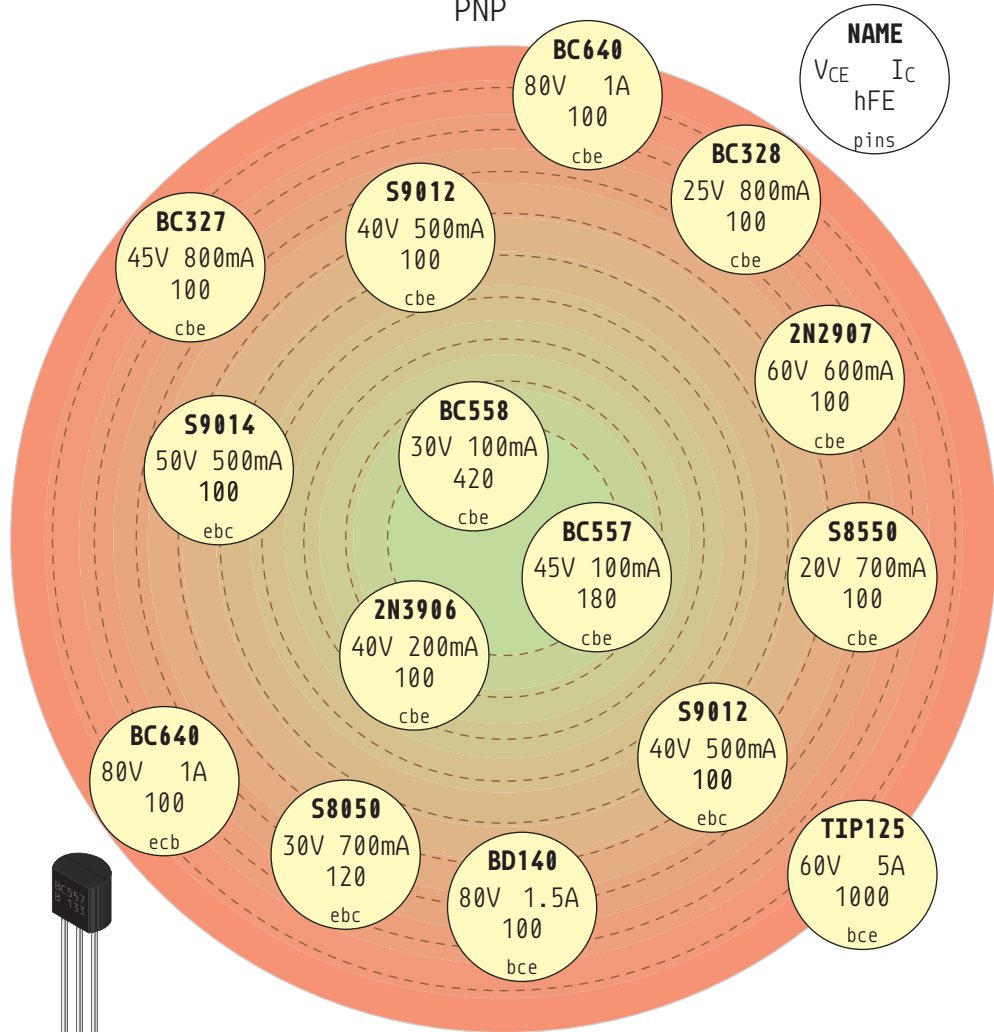




0-1.es/P1

P1

ATmega328P





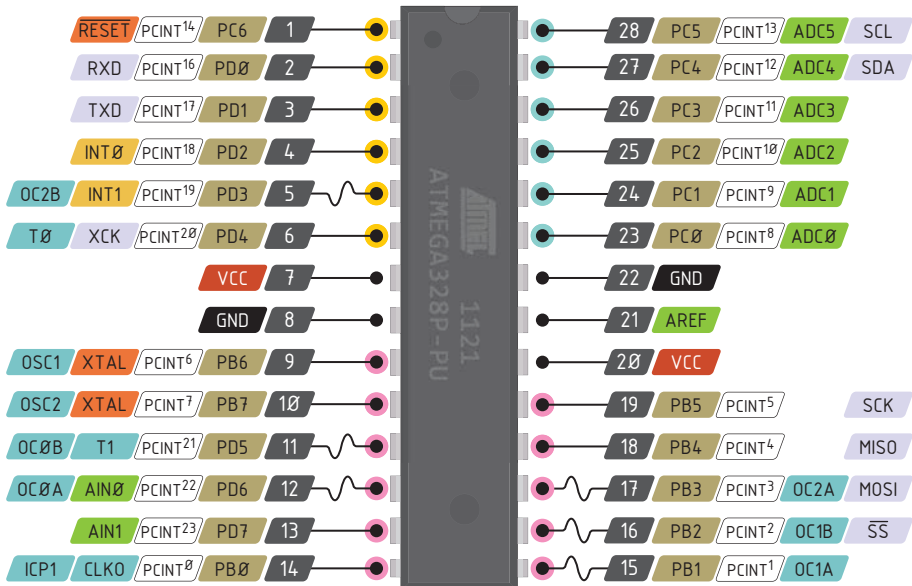




Pinout


 **Absolute** MAX per pin
40mA, 20mA recommended



 **Absolute** MAX per pin 200mA
for the entire package

 The total current of each port
power group **should not exceed** 100mA

-  Power
-  GND
-  Physical PIN
-  Port PIN
-  Analog PIN
-  Serial PIN
-  PIN Function
-  Interrupt PIN
-  Control PIN

 PWM Pin

 Port power group





P2


0-1.es/P2

ATtiny85

Simplified Pinout




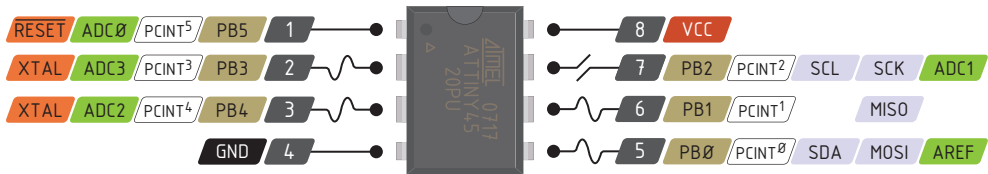Absolute MAX per pin
10mA, 5mA recommended



Absolute MAX per pin 60mA
for the entire package

ICSP Programming

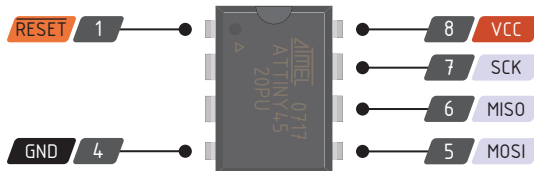

- Power
- GND
- Physical PIN
- Port PIN
- Analog PIN
- Serial PIN
- PIN Function
- Interrupt Pin
- Control PIN

Interrupt Pin

PWM Pin






0-1.es/P3

P3

ATtiny84 Simplified Pinout




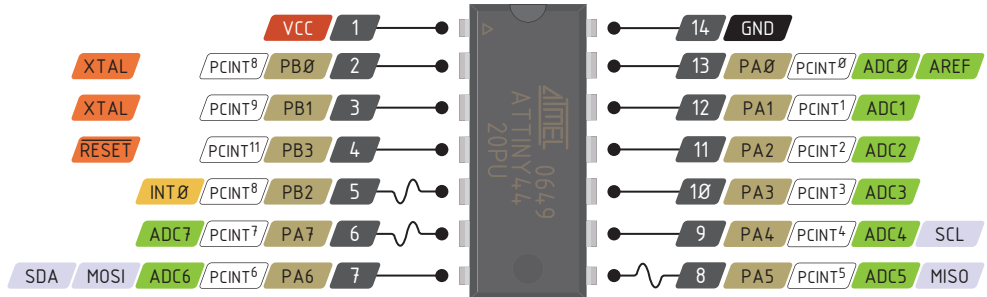Absolute MAX per pin
10mA, 5mA recommended



Absolute MAX per pin 60mA
for the entire package

ICSP Programming

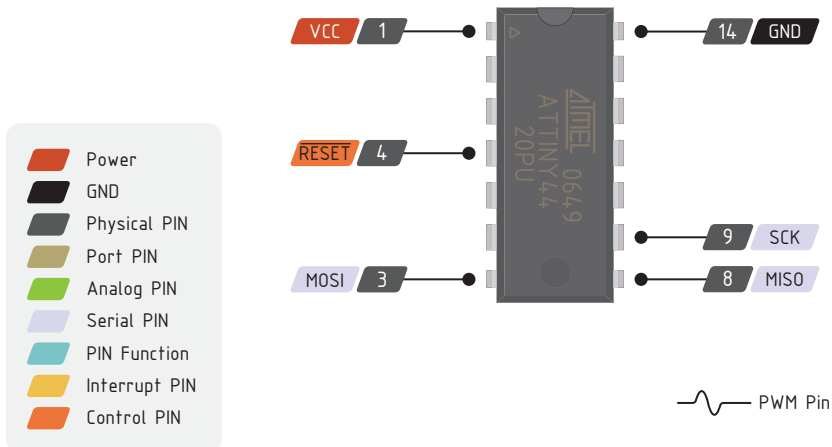



P4


0-1.es/P4

ATtiny2313

Simplified Pinout



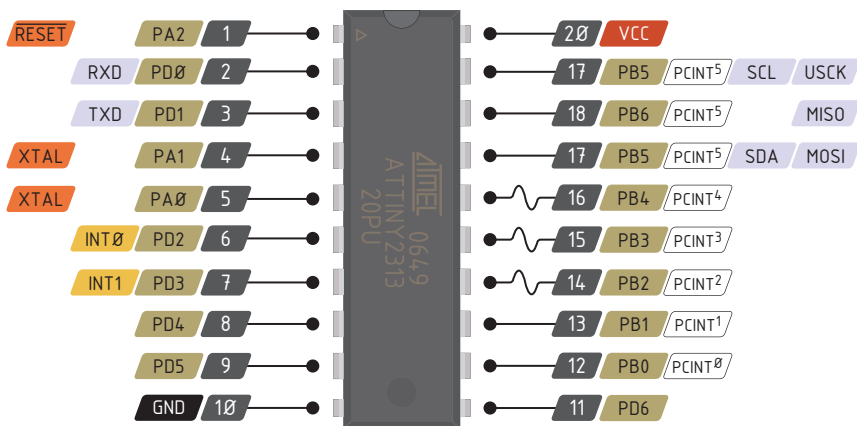Absolute MAX per pin
10mA, 5mA recommended



Absolute MAX per pin 60mA
for the entire package

- Power
- GND
- Physical PIN
- Port PIN
- Analog PIN
- Serial PIN
- PIN Function
- Interrupt PIN
- Control PIN

PWM Pin






0-1.es/P5

P5

ESP8266 Simplified Pinout

ESP-12S

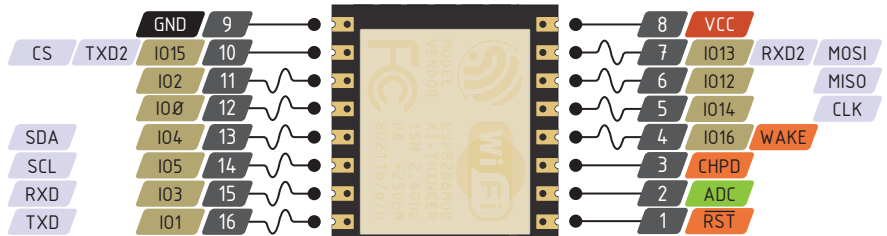


- Power
- GND
- Physical PIN
- Port PIN
- Analog PIN
- Serial PIN
- Control PIN

Absolute MAX per pin
12mA, 6mA recommended

IO15	IO0	IO2	Boot Mode
0V	0V	3.3V	UART Bootloader
0V	3.3V	3.3V	Boot Sketch (SPI Flash)

PWM Pin

ESP-01

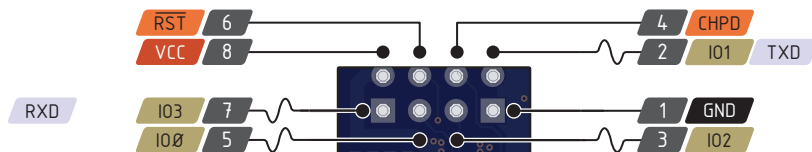

Power **requirements:**
3.3V, $\geq 250\text{mA}$

All ESP8266 IN/OUTs
are **NOT 5V** tolerant!






P5

0-1.es/P5

ESP8266

ESP-12S Minimal Setup

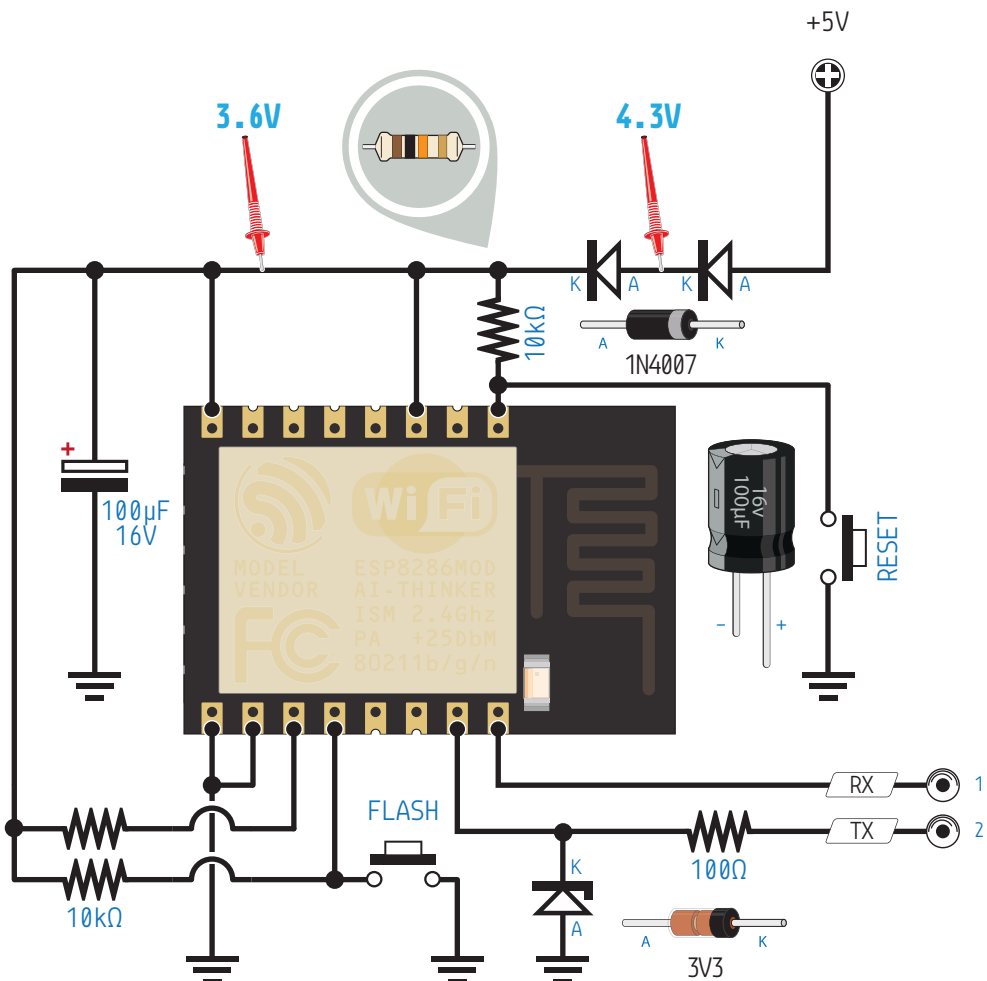

Don't forget to connect all the ground wires together! ⚠






0-1.es/P6

P6

FTDI Pinout

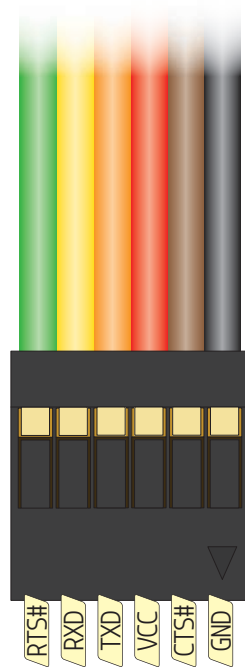

Check the I/O pin voltage before programming the microcontroller!



The FTDI cable is a USB to Serial (TTL level) converter which allows for a simple way to connect TTL interface devices to USB. Normally the I/O pins of FTDI cable are configured to operate at 5V. The FTDI cable uses the RTS signal for hardware reset when programming a microcontroller board.






P7

0-1.es/P7

ICSP Pinout

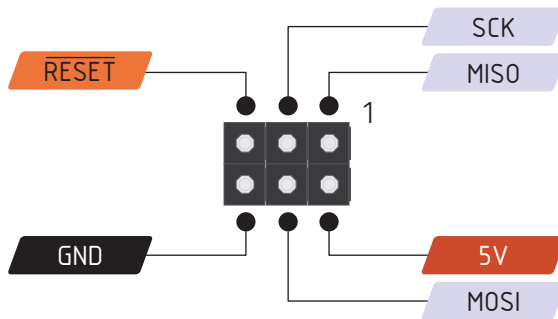

The ICSP header allows the microcontroller to receive the firmware or the bootloader. **ICSP** stands for In Circuit Serial Programming, it is a standard way to program AVR chips. ISCP uses six pins to program the microcontroller:

MISO: (Master In Slave Out): the slave line for sending data to the master.

MOSI: (Master Out Slave In): the master line for sending data to the peripherals.

SCK: (Serial Clock): the clock pulses that synchronize data transmission generated by the master.

RESET: connected to the reset signal of the microcontroller.






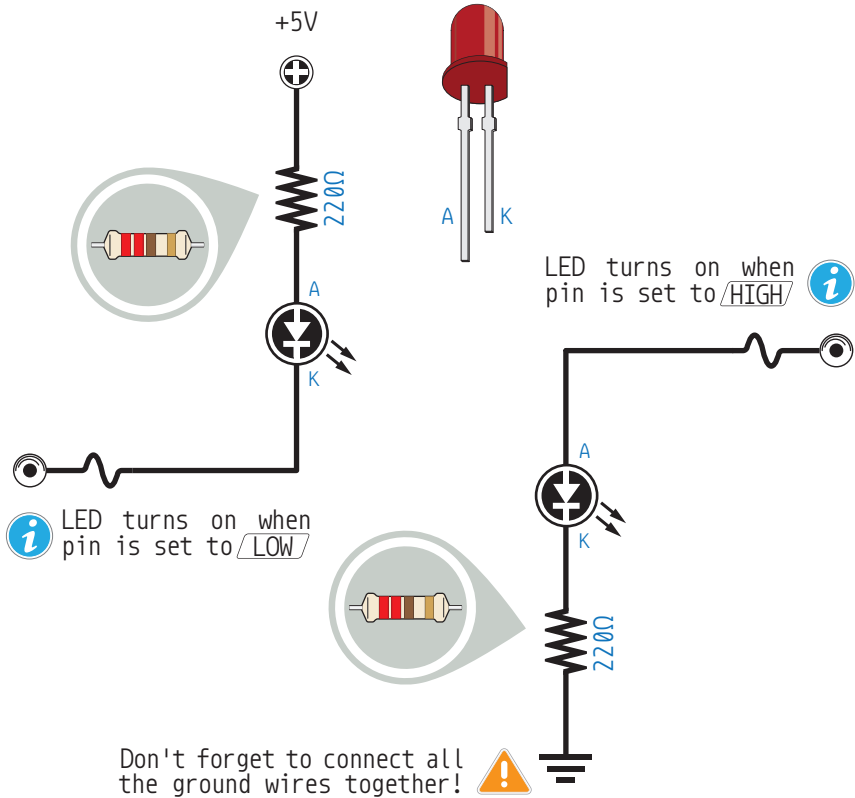
0-1.es/1



LED

Basic Connections

 Reversing the polarity will not damage the LED



LEDs (light-emitting diodes) are components that are polarized and only allow current to flow in one direction. LEDs normally have two terminals: the anode (A) or positive side (the longer lead), and the cathode (K) or negative side (the shorter lead closest to the flat edge of the LED).





1

0-1.es/1

LED Test Code

```
int LEDPin = 13;
```

Assign variable *LEDPin* as pin 13


```
void setup() {  
  pinMode(LEDPin, OUTPUT);  
}
```

Initialize the pin as an OUTPUT

```
void loop() {  
  digitalWrite(LEDPin, HIGH);  
  delay(1000);  
  digitalWrite(LEDPin, LOW);  
  delay(1000);  
}
```

Turn the LED ON
Wait for 1 second
Turn the LED OFF
Wait for 1 second

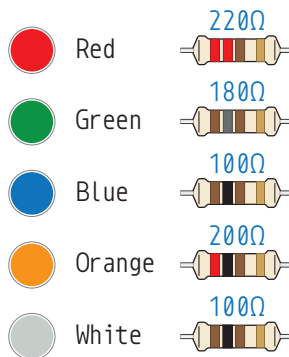Typical LED Current Limiting Resistor Values



Limiting the current that flows through an LED is very important! For this purpose, a current limiting resistor is used in series with the LED. If you connect the LED directly (without a resistor in series) the microcontroller or the LED may suffer damage!






0-1.es/2

2

Alternating LEDs

Basic Connections

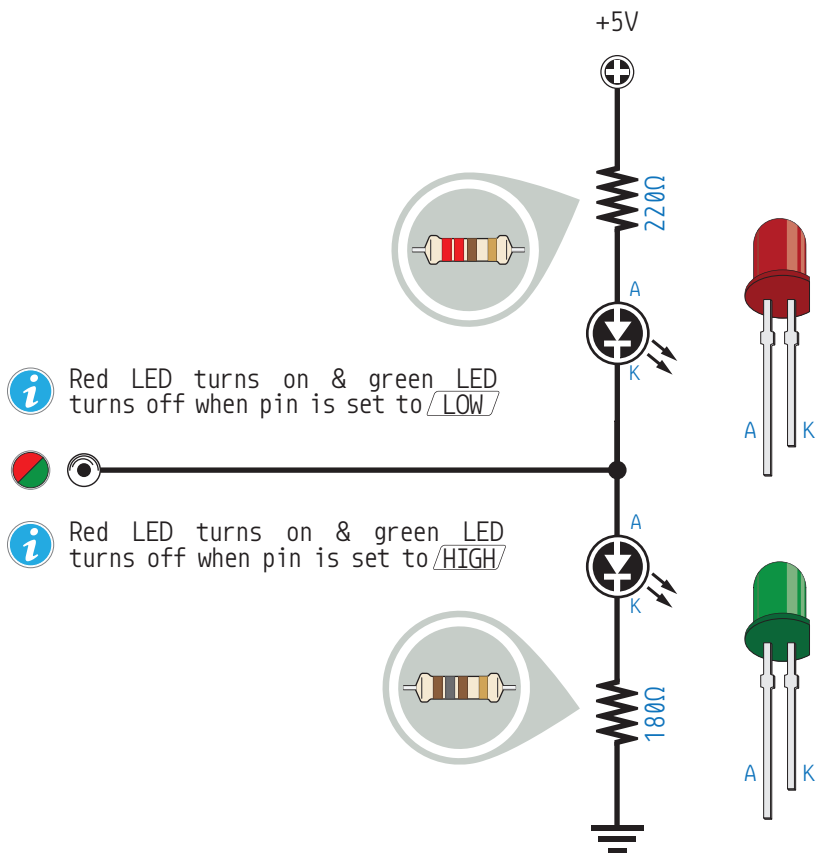




3


0-1.es/3

Bi-Color LED

2-Lead LEDs

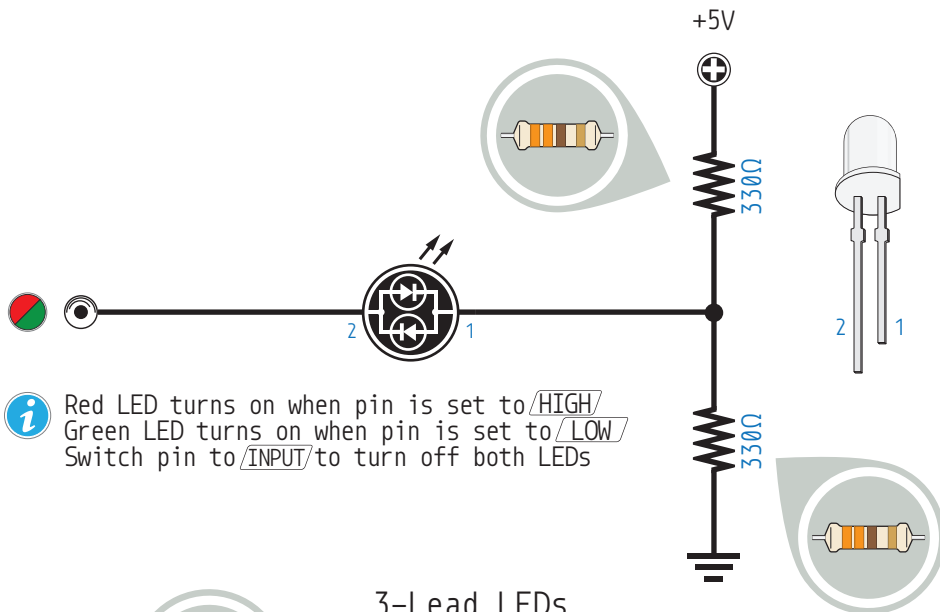

3-Lead LEDs

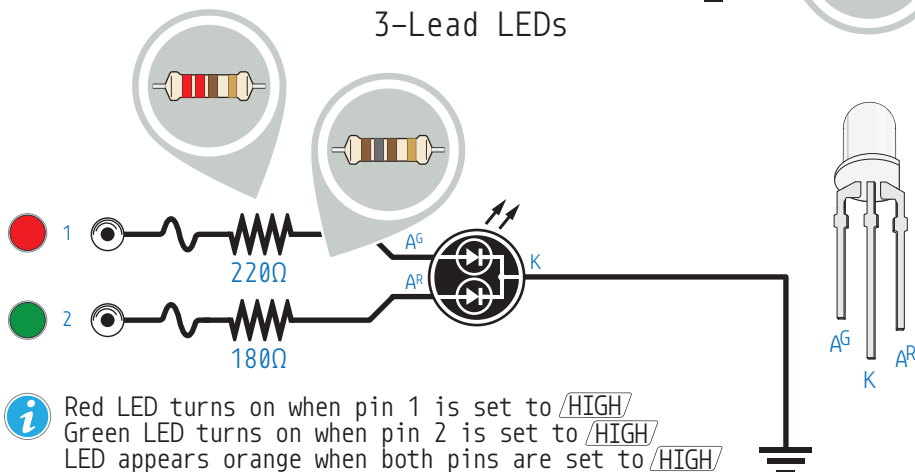




0-1.es/4

4

LED Cluster

Basic Connections

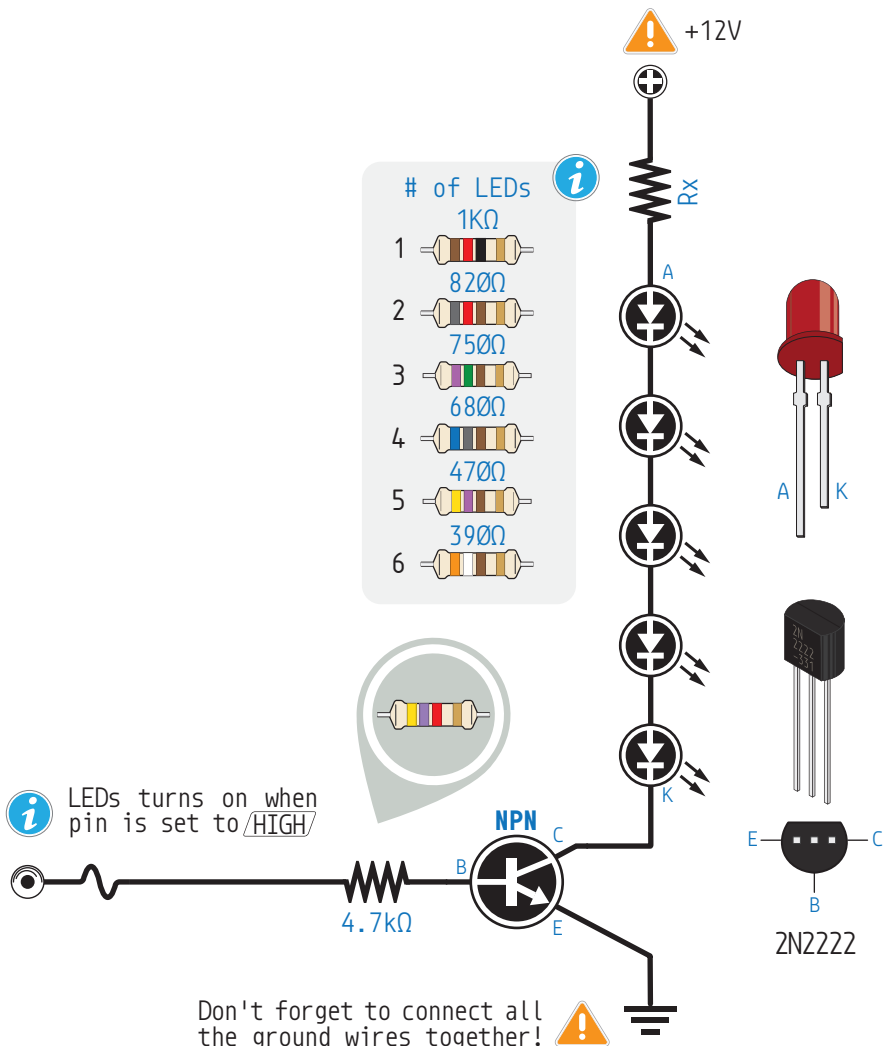




5

0-1.es/5

RGB LED


Common Cathode Configuration

i LED turns on when pin is set to HIGH

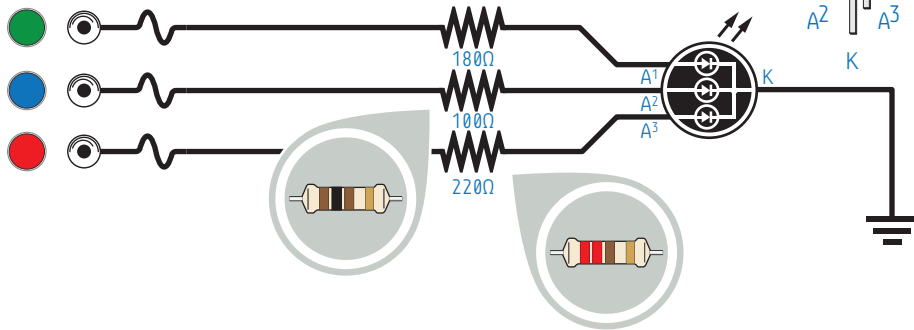

Common Anode Configuration

i LED turns on when pin is set to LOW

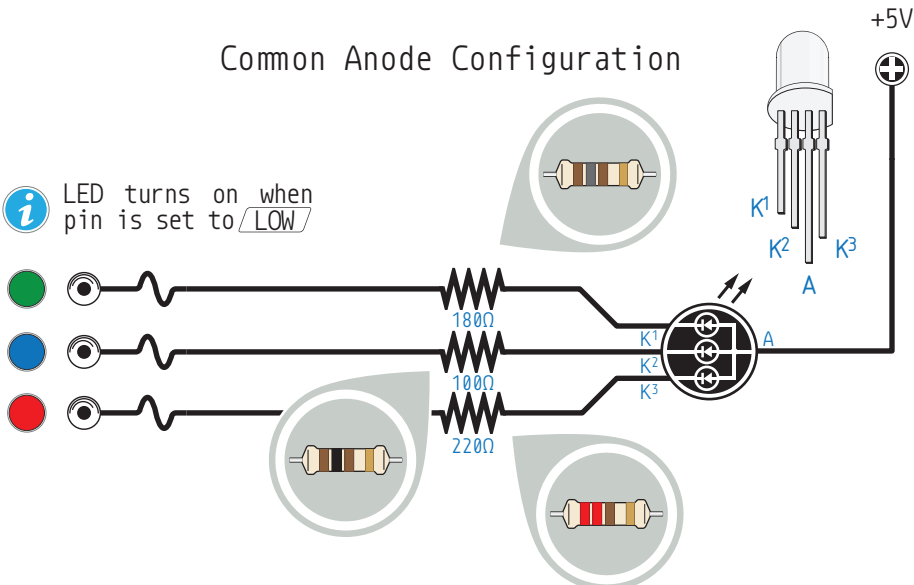




0-1.es/6

6

LED Strip

Basic Connections

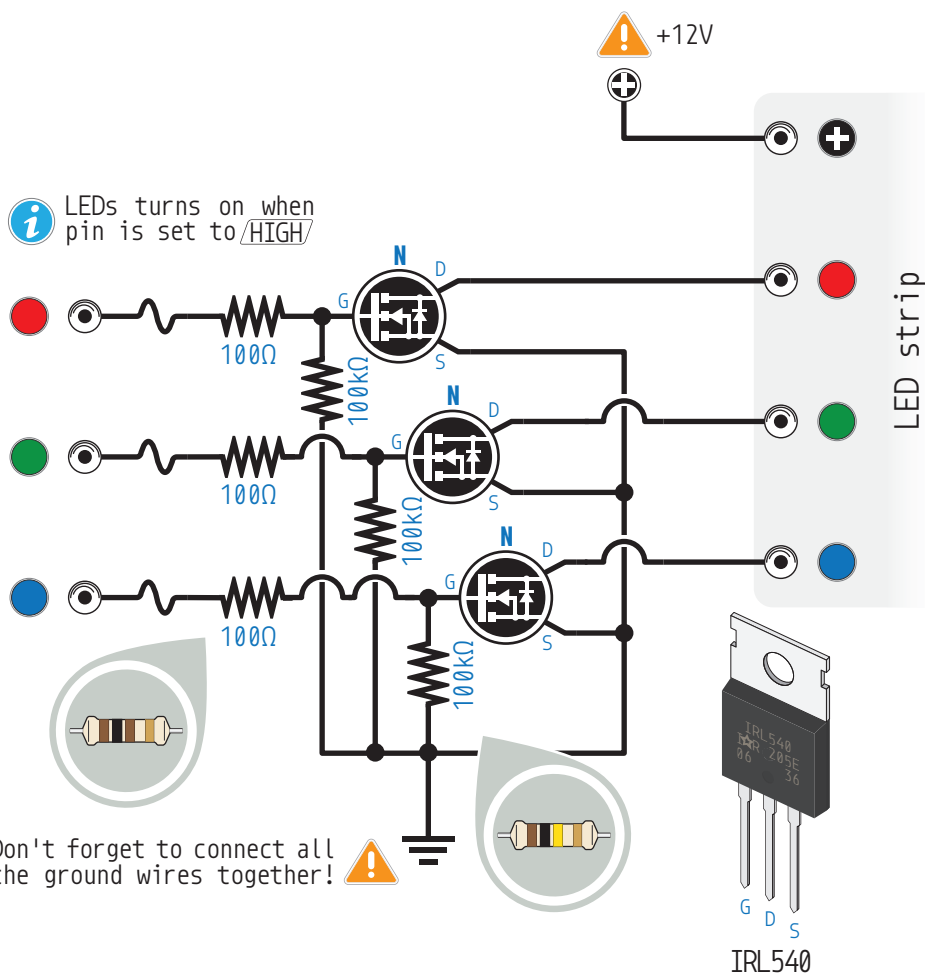

A 1 meter long LED strip can draw nearly 1A when all LEDs are on full brightness. The I/O pins of most microcontroller boards can only supply up to 40mA each, so you will have to help it out with a driver circuit to boost the power. This circuit uses 3 PWM signals from the board and uses them to drive 3 MOSFETs.






7

0-1.es/7

Digitally-Addressable LEDs

Basic Connections

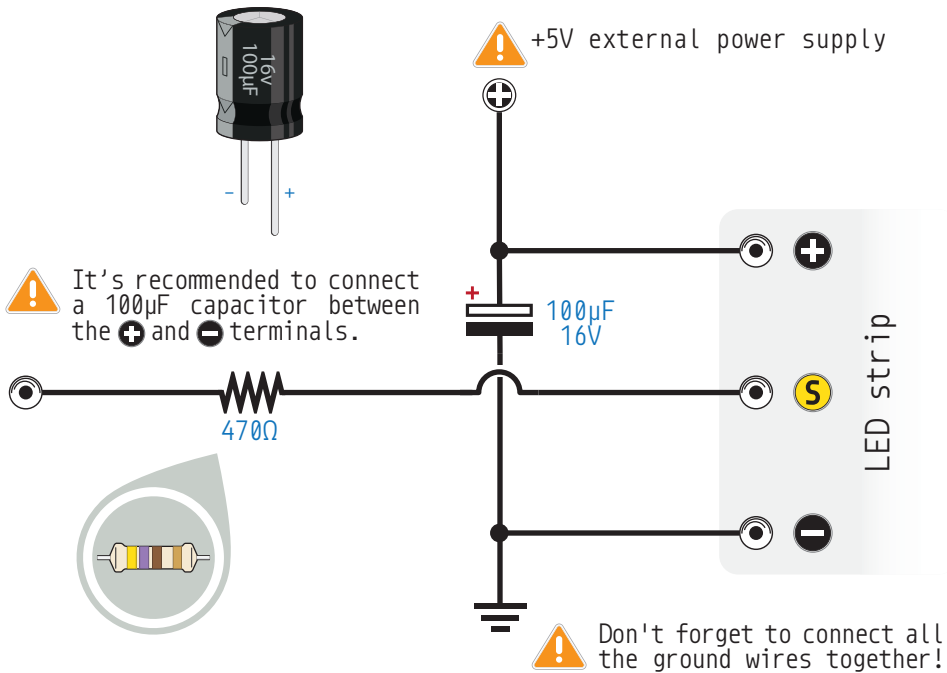

⚠ When connecting digitally-addressable LEDs to any LIVE power source or microcontroller, **ALWAYS CONNECT GROUND (⚡) BEFORE ANYTHING ELSE**. Conversely, disconnect ground last when detaching the LEDs.



This schematic is valid only for RGB color pixels and strips based on the WS2812, WS2811 and SK6812 LED drivers, which use a single-wire control protocol. Do not power the strip directly from the 5V pin of the microcontroller board! Each individual LED draws up to 60mA when set to white at maximum brightness.







0-1.es/8

8

Charlieplexing

Basic Connections

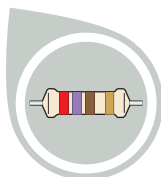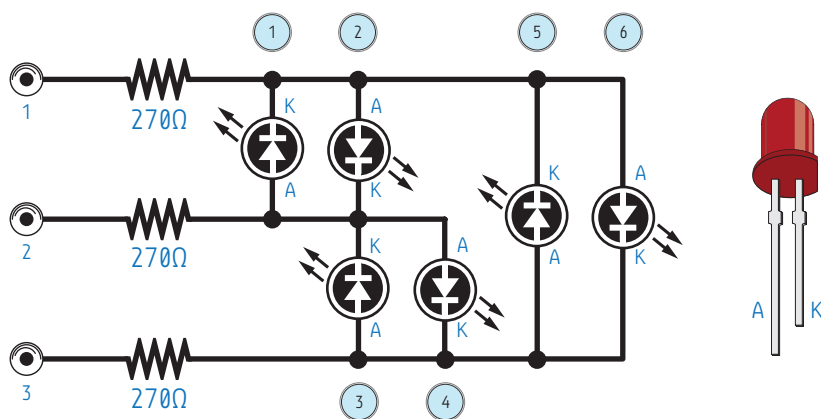

1	2	3		
LOW	HIGH	INPUT		1
HIGH	LOW	INPUT		2
INPUT	LOW	HIGH		3
INPUT	HIGH	LOW		4
LOW	INPUT	HIGH		5
HIGH	INPUT	LOW		6



Charlieplexing is a technique for driving a multiplexed display in which relatively few I/O pins on a microcontroller are used to drive an array of LEDs. Not only does it take advantage of the two states that we normally change, HIGH and LOW, but it also uses a third state by changing between OUTPUT and INPUT modes.







9

0-1.es/9

LED Matrix

Basic Connections

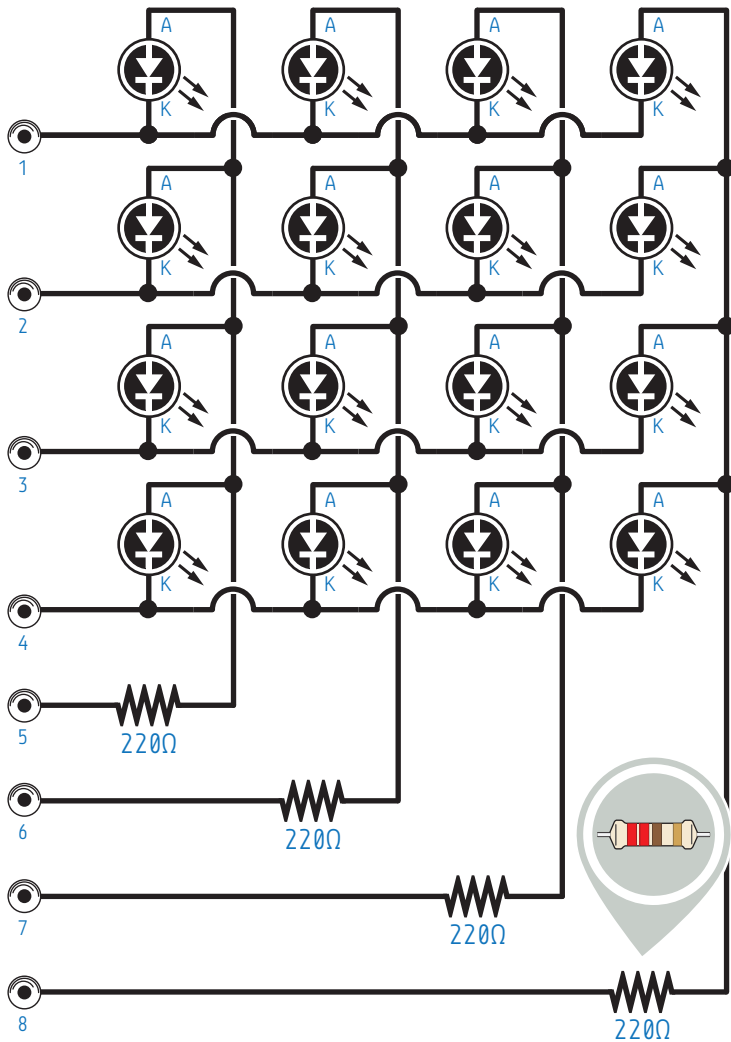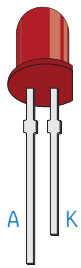




0-1.es/10

10

Multiple LED Clusters

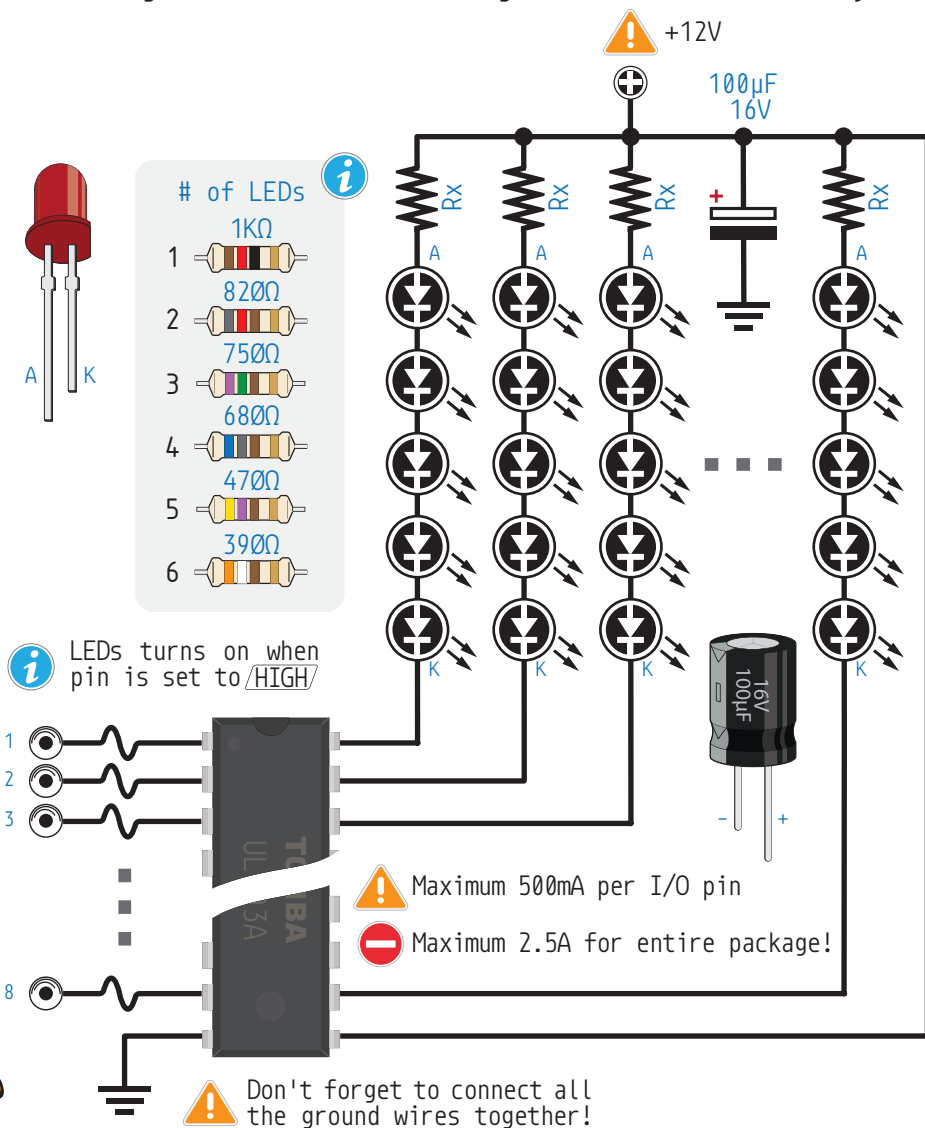Using the ULN2803 Darlington Transistor Array






10


0-1.es/10

ULN2803

Pinout

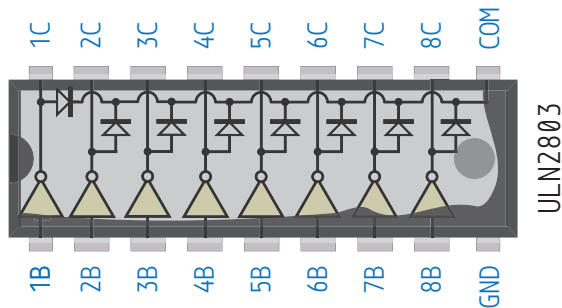

Port Schematic

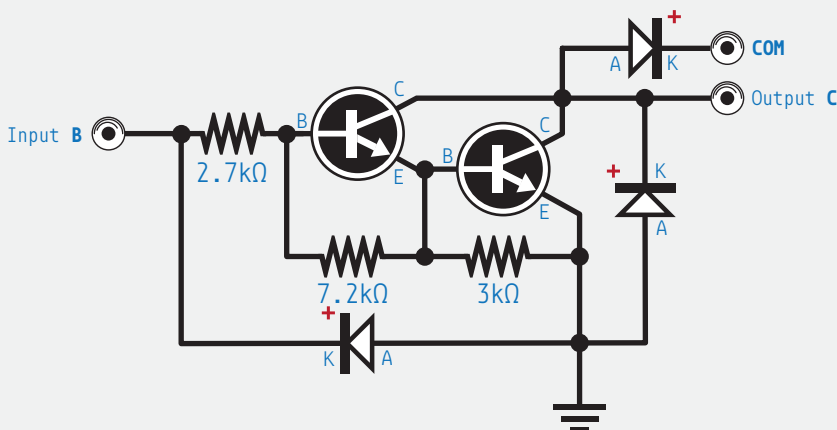

The ULN2803 is an octal Darlington transistor array that delivers up to 500mA of current for each pin and operates at up to 50V. You can drive motors, DC light bulbs, relays, solenoids, etc. The Darlington output pins can even be connected in parallel for higher current applications.







0-1.es/11

11

Decoder/Demultiplexer

Using the 74HC238 Decoder

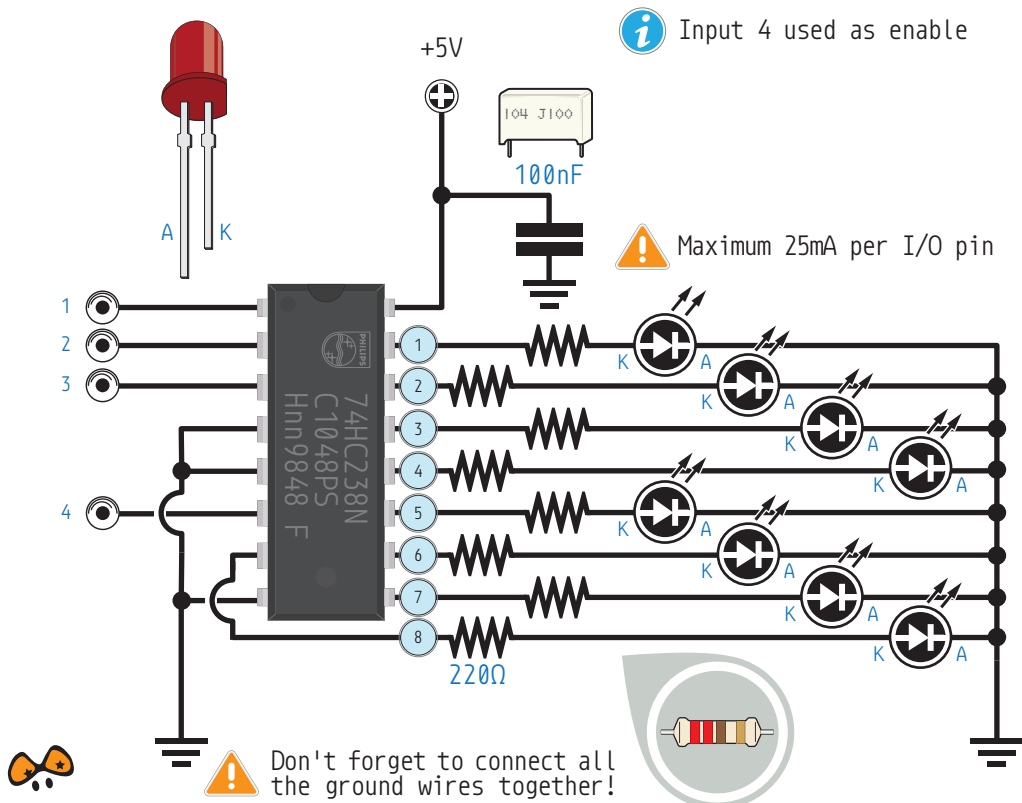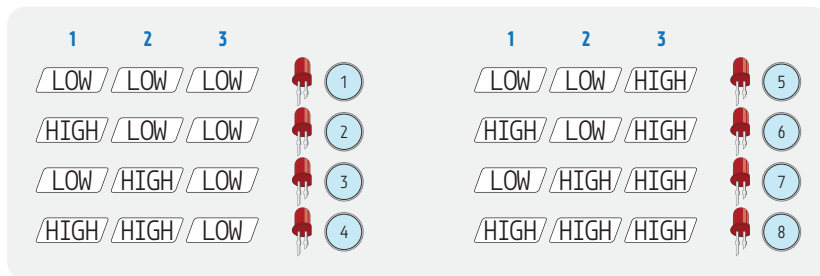



0-1.es/11

Pinout



The 74HC238 is a high speed CMOS 3-to-8 line decoder. It has three binary select inputs (A0, A1, A2) which determine which one of the eight outputs (Y0-Y7) will go high. This chip has three enable inputs (E1, E2, E3). If you leave E3 low, no outputs can be set to high.






0-1.es/12

12

Shift Register

Using the 74HC595 Shift Register

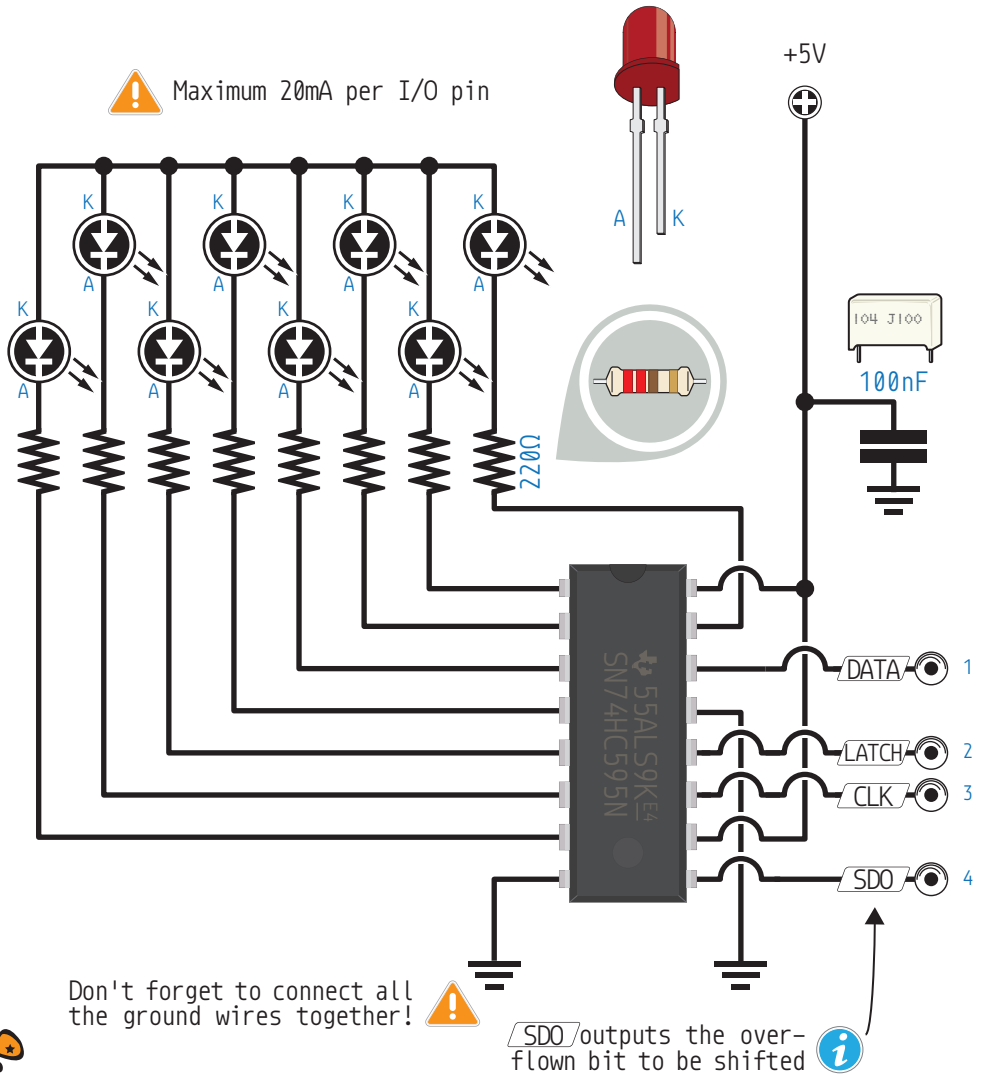




12


0-1.es/12

74HC595

Pinout

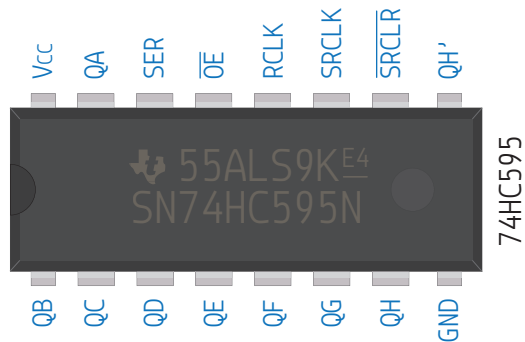

Connecting Multiple 74HC595

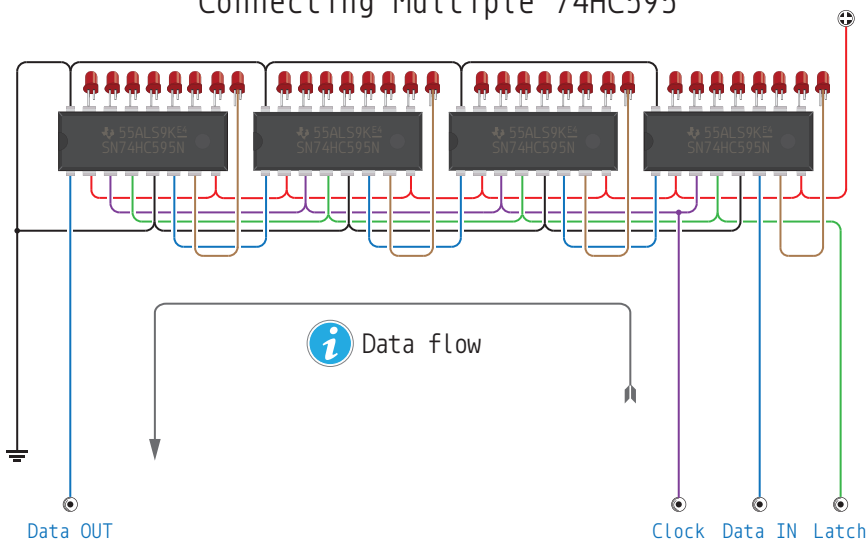

The 74HC595 is an 8-bit shift register. It takes 8 bits from the serial input and outputs them to 8 pins. You can daisy chain them together so it's really easy to control a big number of LEDs or power transistors from only 3 digital microcontroller pins.






0-1.es/13

13

Input Shift Register Via SPI

Using the 74HC165 Shift Register

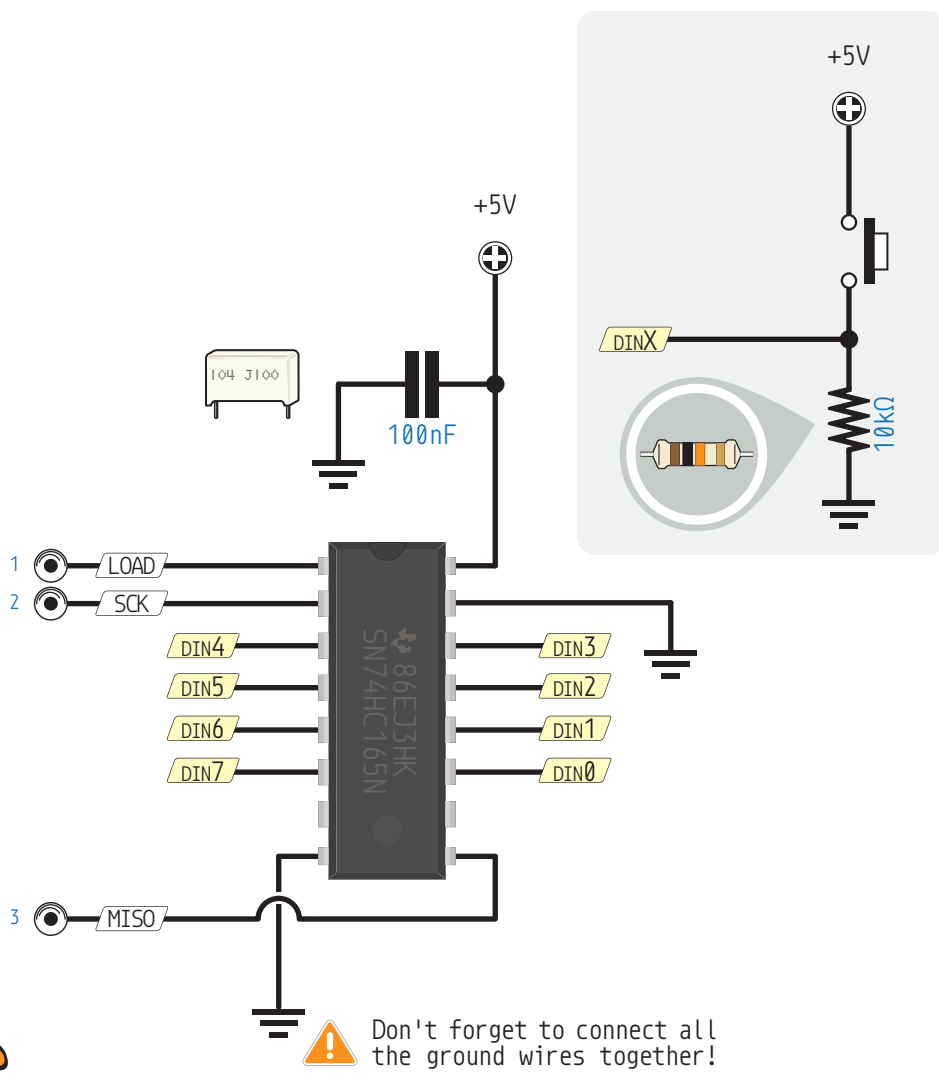




13


0-1.es/13

74HC165

Pinout

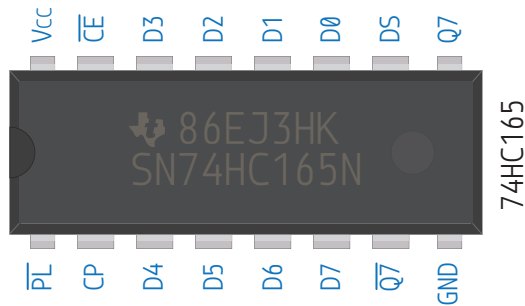

Connecting Multiple 74HC165

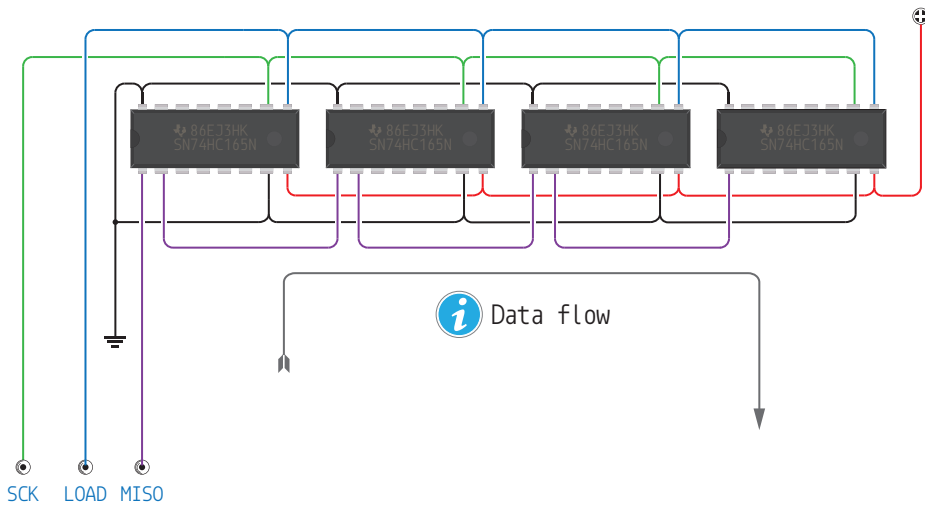

The 74HC165 is an 8-bit parallel-load or serial-in shift registers with complementary serial outputs available from the last stage. You can daisy chain them together so it's really easy to control a big number of LEDs or power transistors from only 3 digital microcontroller pins.






0-1.es/14

14

MAX7219 7-Seg. Display Driver

Connecting a 4-Digit 7-Segment Display

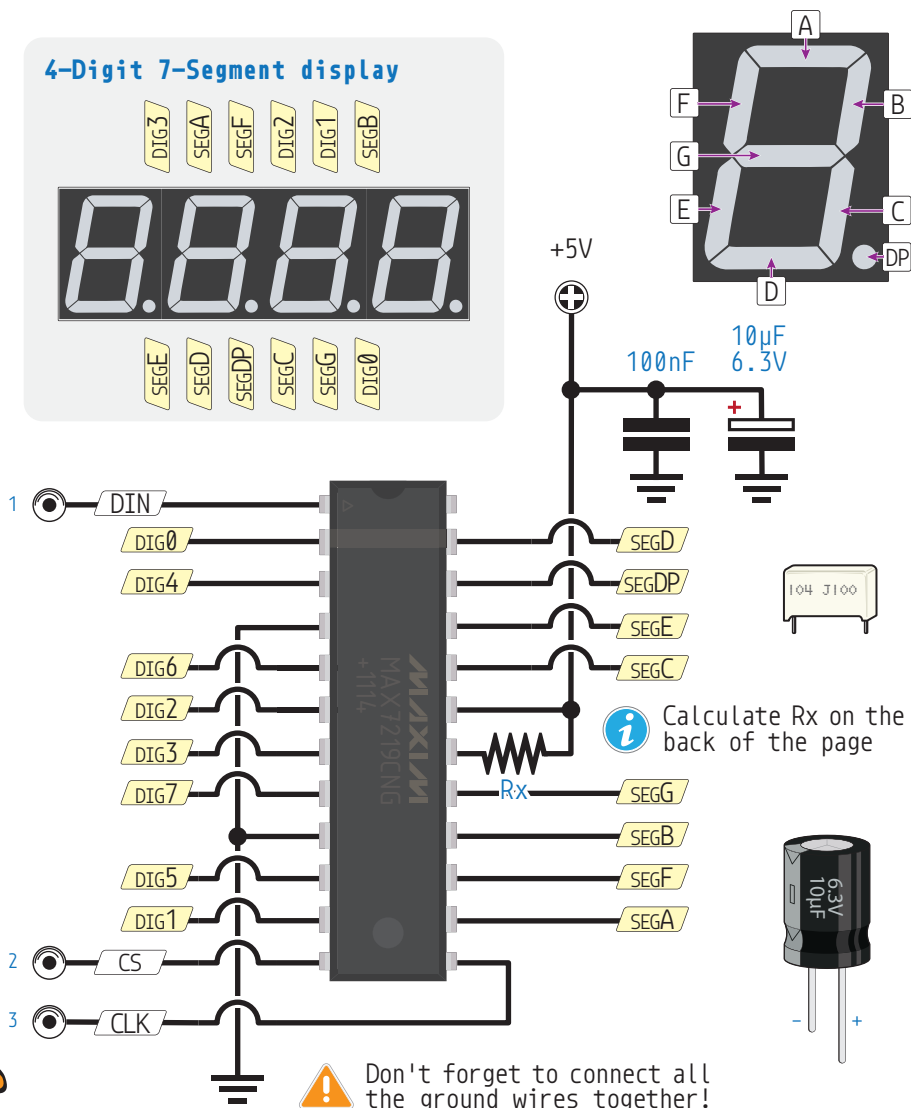




14

0-1.es/14

MAX7219

Pinout

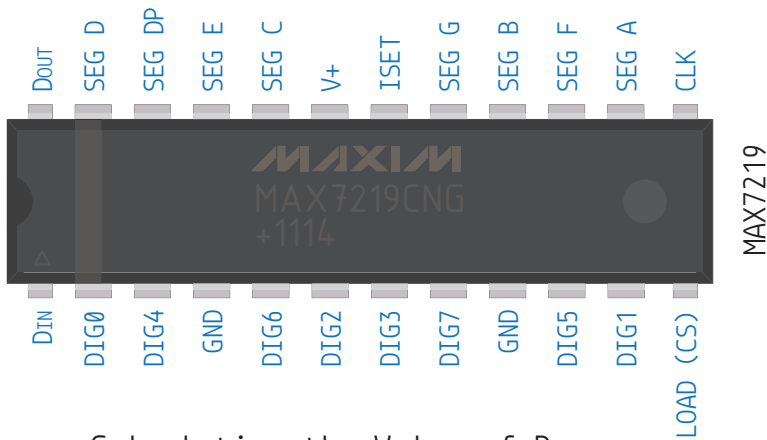

Calculating the Value of Rx

The MAX7219 is a constant-current LED driver. Resistor Rx is used to set the current for the LEDs. You will need to know the voltage and forward current for your LED display or matrix and match the value on the table below. E.g., if you have a 2V, 20mA LED, your resistor value must be 28kΩ.

I _{SEG} (mA)	V _{LED} (V)				
	1.5	2.0	2.5	3.0	3.5
40	12.2	11.8	11.0	10.6	9.69
30	17.8	17.1	15.8	15.0	14.0
20	29.8	28.0	25.9	24.5	22.6
10	66.7	63.7	59.3	55.4	51.2

 Values in kΩ



The MAX7219 is a powerful serial input/output common-cathode display driver that interfaces microcontrollers with 7-segment numeric LED displays of up to 8 digits. It has a built-in BCD decoder and brightness control. You could also use it to drive individual LEDs, Bar-graphs LEDs, or 8×8 LED matrix displays.





0-1.es/15

15

LEDM88G 8x8 LED Matrix

Using the MAX7219 LED Display Driver



Use a common-cathode LED matrix

Pin 16



SEG G

SEG F

DIG 1

SEG DP


DIG 3

SEG E

SEG C

DIG 0

Pin 9

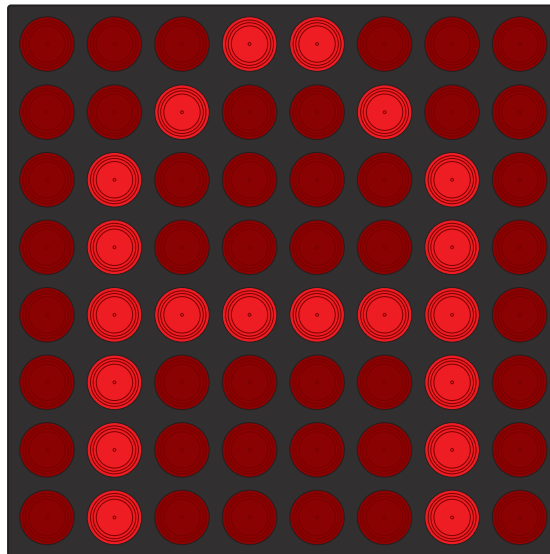

Pin 1

DIG 4

DIG 6

SEG A

SEG B

DIG 7

SEG D

DIG 5

DIG 2



Pin 1 is the first pin starting from the left if you orient the device so that the part number is facing towards you







15

0-1.es/15

LEDM88G 8x8 LED Matrix Schematic

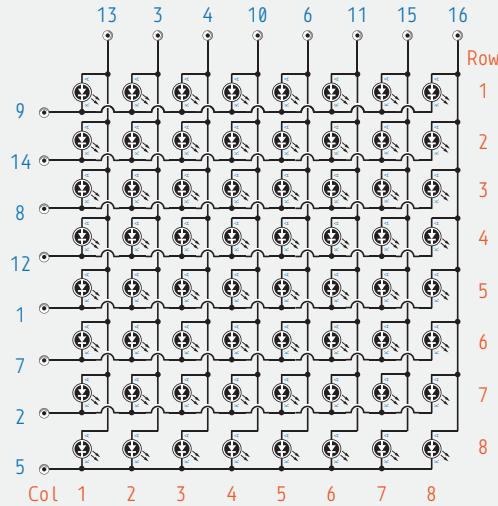

Connecting Multiple MAX7219

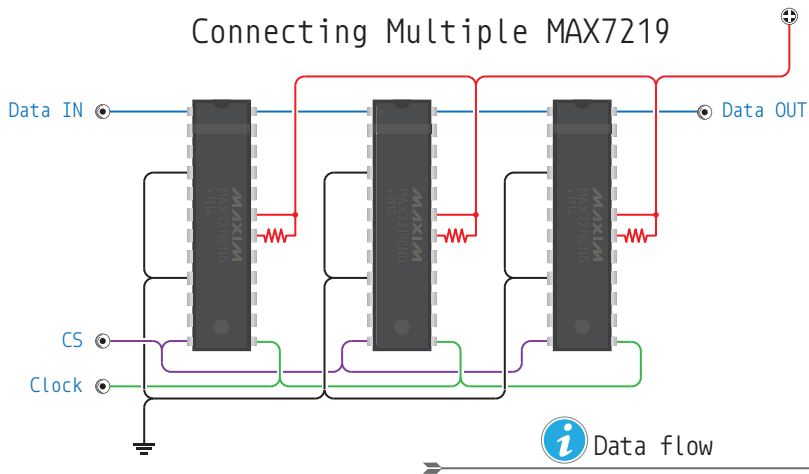

Using one MAX7219 you can drive up to 64 LEDs using only 4 wires to interface with a microcontroller. This powerful LED driver is designed to be daisy-chained so you can connect multiple 64-pixel displays together (like those scrolling signs you see in shop windows).






0-1.es/16

16

TLC5940 LED Driver

Basic Connections

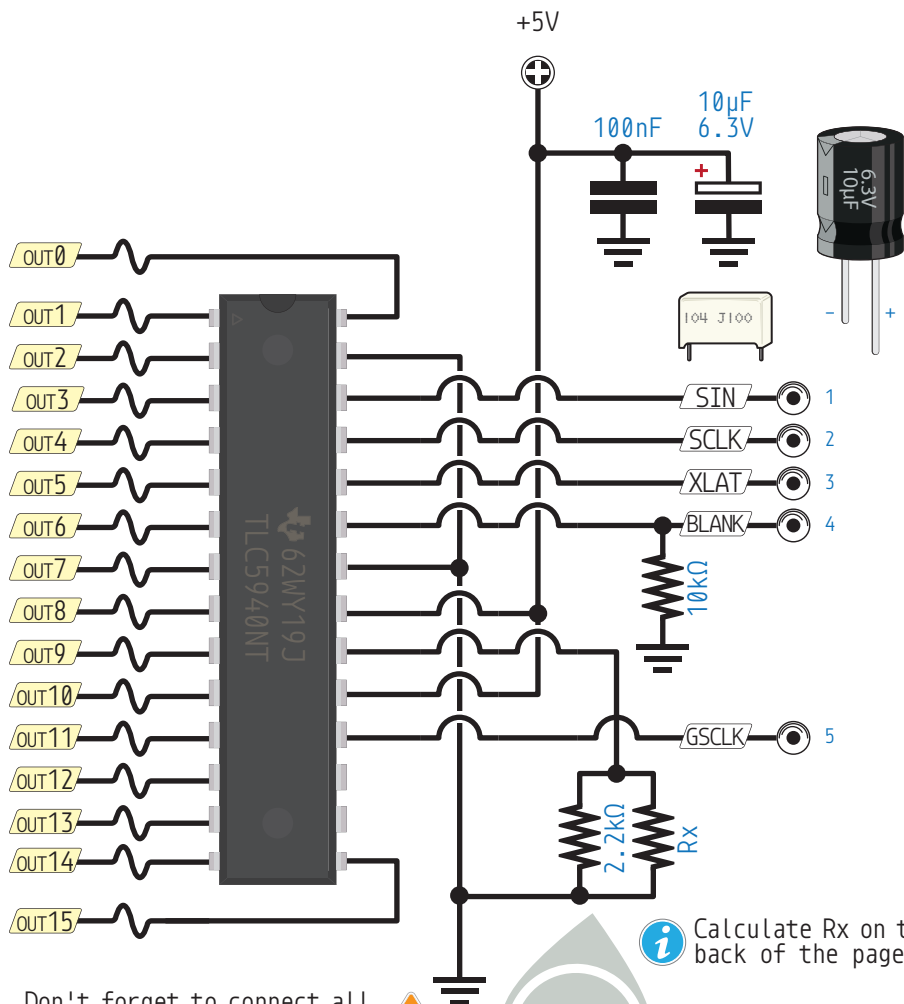




16

0-1.es/16

TLC5940

Pinout

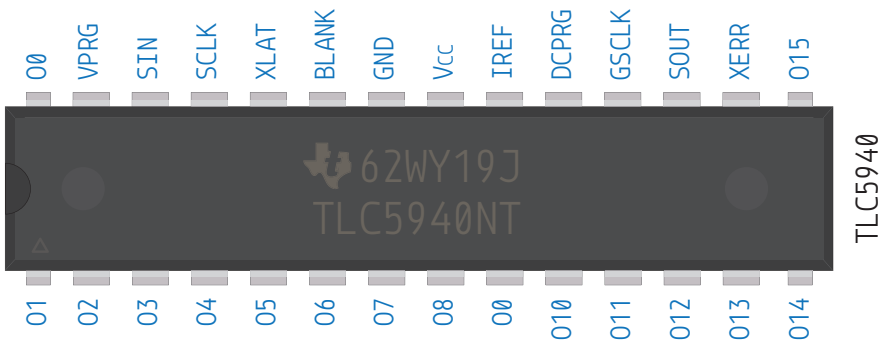

Calculating the value of Rx

The TLC5940 is a constant-current LED driver. The value of Rx has to be calculated according to the output current that is best suited for your application. If you want to connect components that draw 18mA of current use Ohm's law to calculate the resistor value as shown below.

$$R_x = V / I$$
$$R_x = 39.06V / 0.018A$$
$$R_x = 2.170 \approx \mathbf{2.2k\Omega}$$



The number 39.06 comes from the on-chip 1.24V voltage reference multiplied by a gain of 31.5, therefore $1.24 \times 31.5 = 39.06V$



The TLC5940 is a 16-channel, constant-current sink LED driver. Each channel has an individually adjustable 4096-step grayscale PWM brightness control, 6 bit current limit control (0-63), and a daisy chainable serial interface. Use this schematic to increase the number of PWM pins available to your microcontroller.






0-1.es/16

16

TLC5940 LED Driver


Connecting LEDs

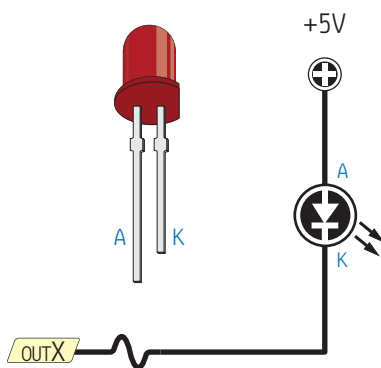

i You can connect outputs in parallel to sink different current levels

Paralleled outputs	LED current range (mA)	Number of LEDs per chip
1	0-80	16
2	0-160	8
3	0-240	5
6	0-480	2
8	0-640	2
16	0-1280	1

Connecting Servos

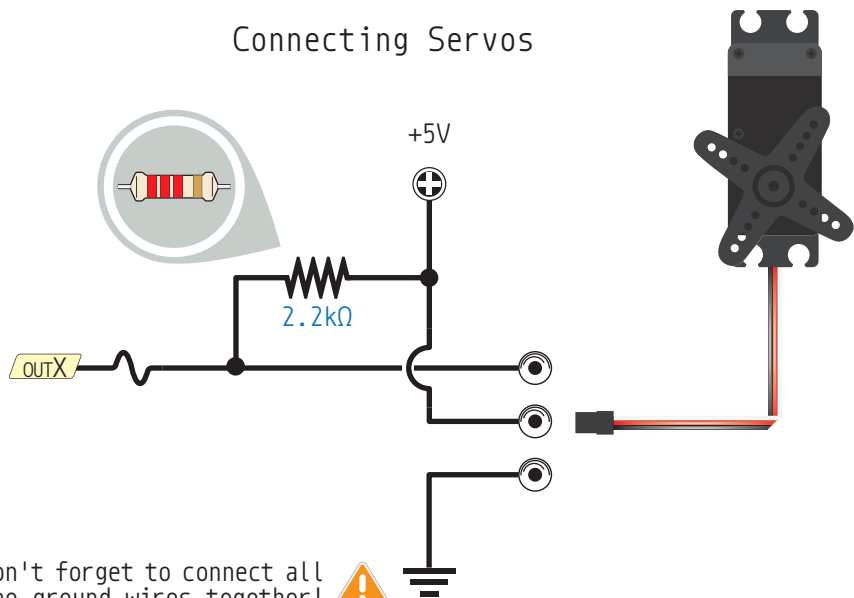


Don't forget to connect all the ground wires together! **!**




0-1.es/16

TLC5940 LED Driver

Connecting High-Power LEDs

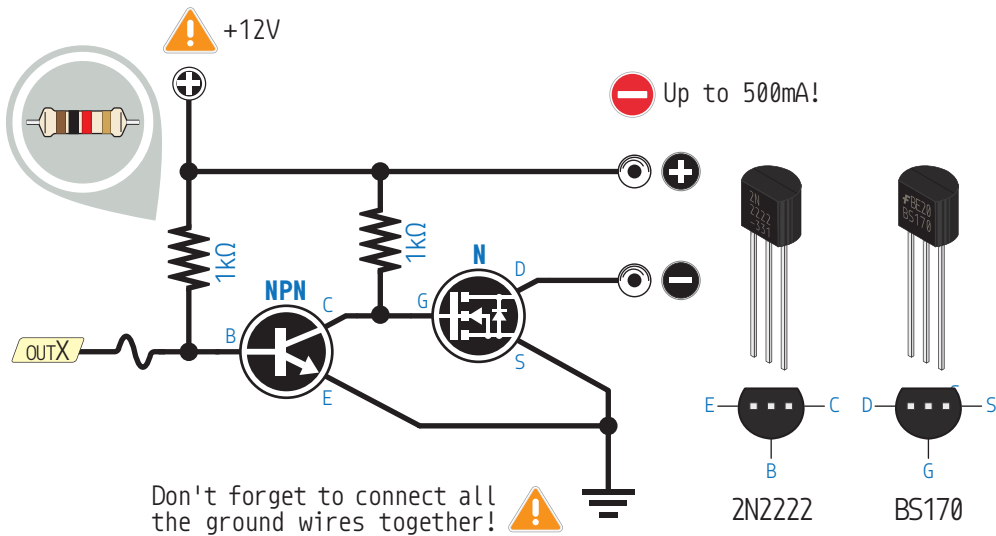

Connecting Multiple TLC5940

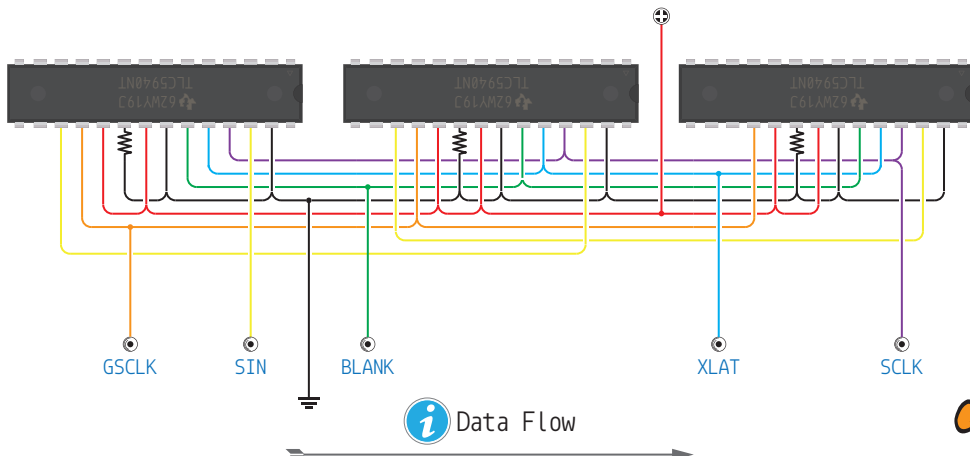



Common-Cathode Connections








18

0-1.es/18

4-Digit 7-Segment Display

Basic Connections

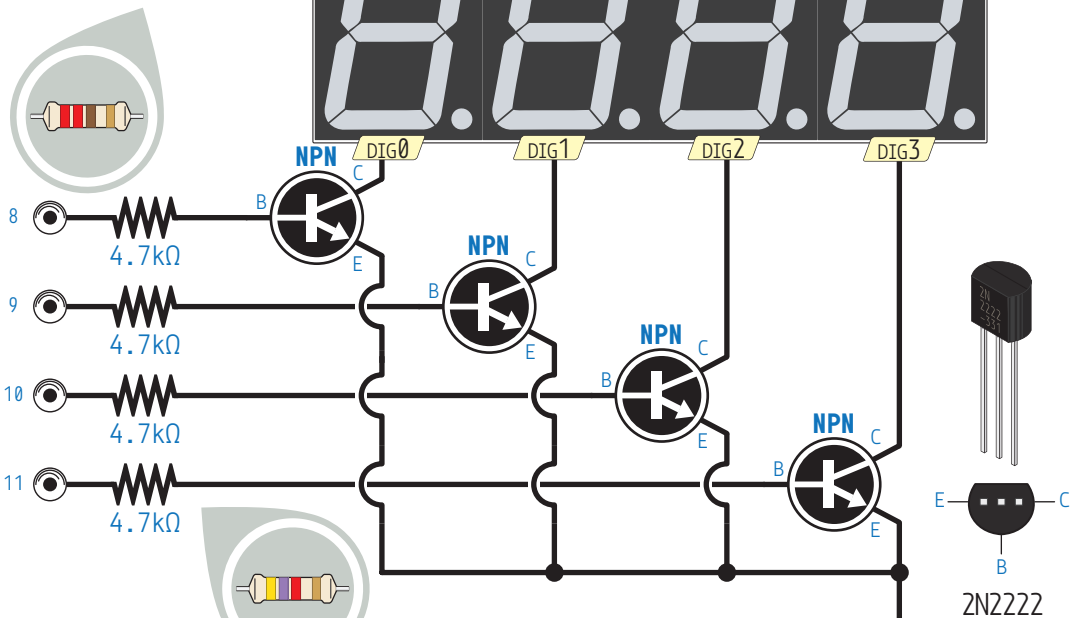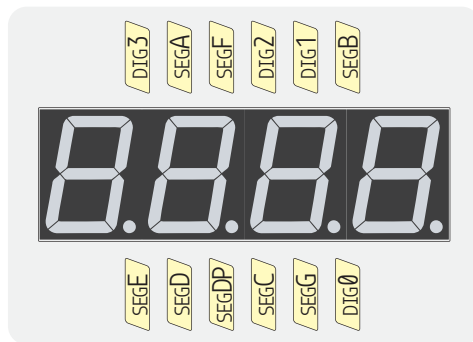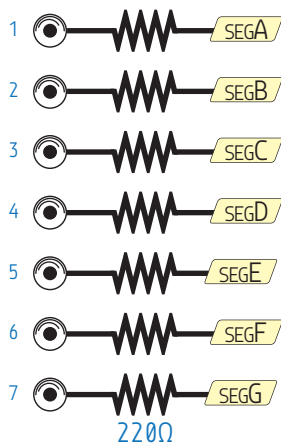

Don't forget to connect all the ground wires together!






0-1.es/19

19

I/O Expander

Using the MCP23017 I/O Expander

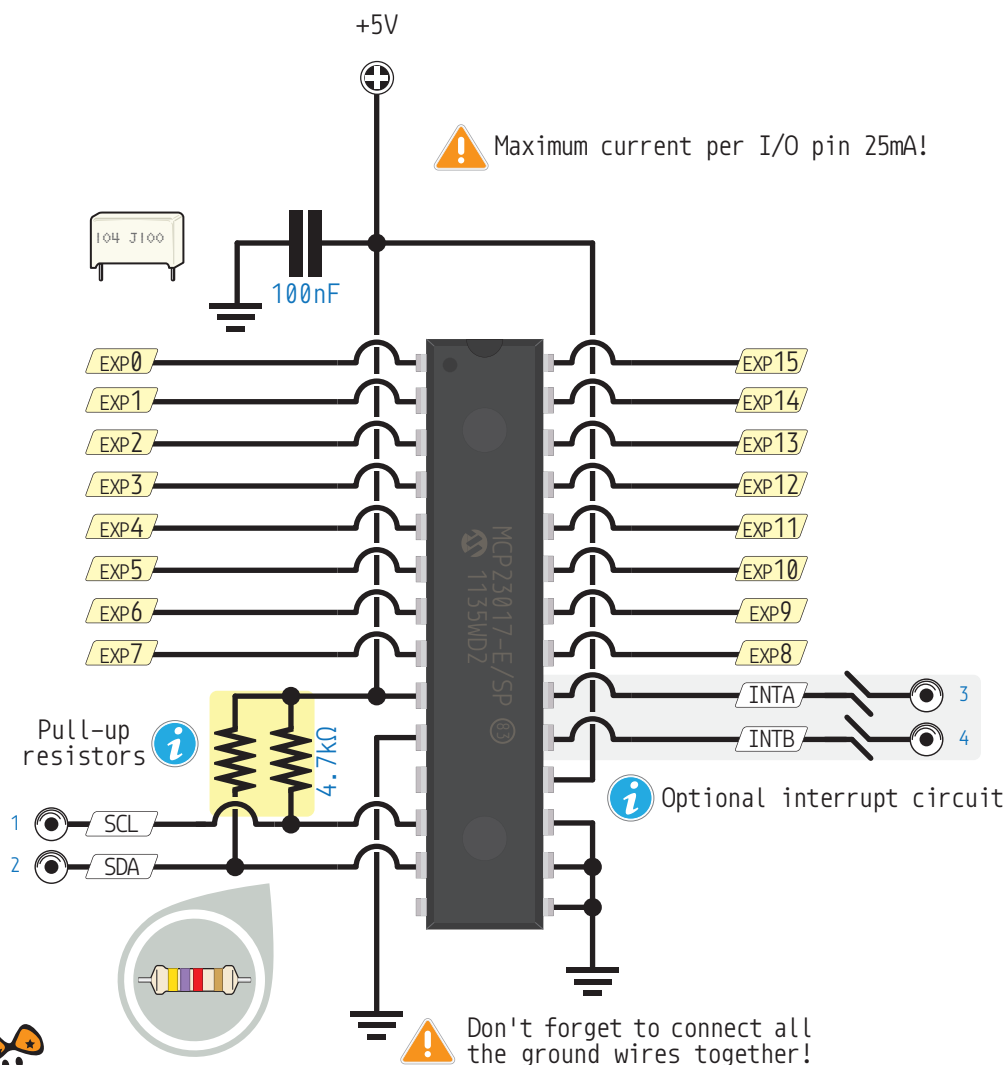




19


0-1.es/19

MCP23017


Pinout

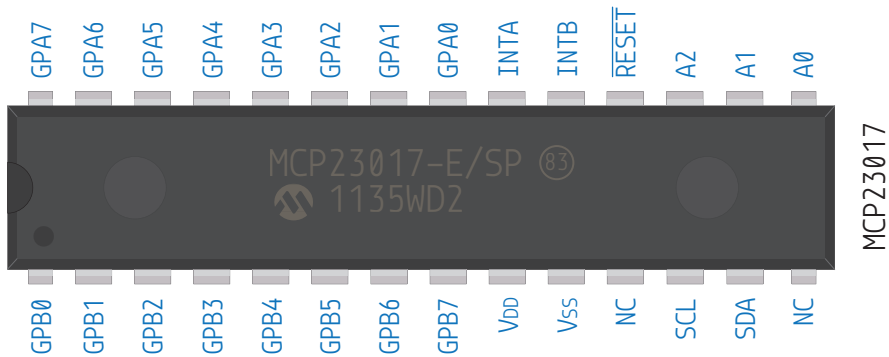

Connecting an LED

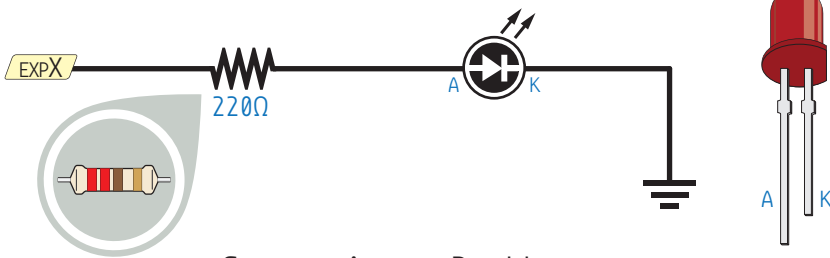

Connecting a Pushbutton

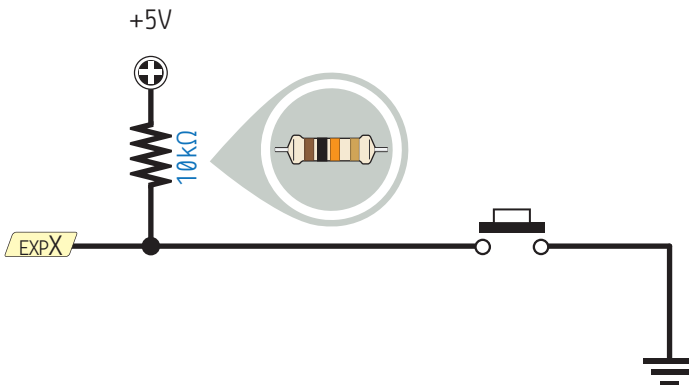



Using the 4051 Mux/Demux






20


0-1.es/20

4051

Pinout

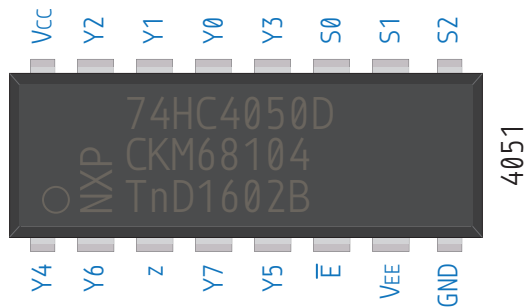

Doubling the Number of Ports

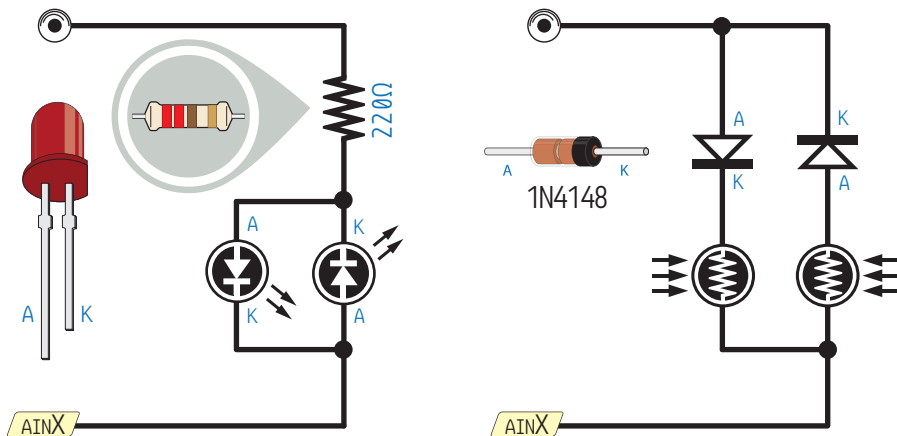

The 4051 is a single-pole octal-throw analog switch suitable for use in analog or digital 8:1 multiplexer/demultiplexer applications. The switch features three digital select inputs, eight independent inputs/outputs and common input/output.






0-1.es/21

21

DC Light Bulb

Low-Power Load

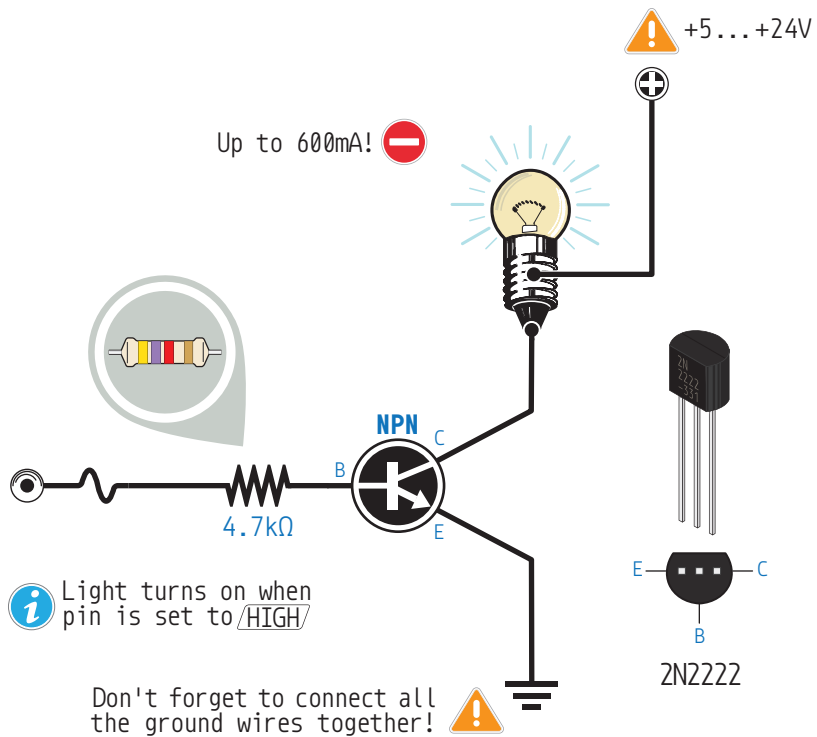

Microcontrollers can only output a very small amount of current from their output pins. These pins are meant to send control signals, not to act as power supplies. The most common way to control a direct current device from a microcontroller is to use a transistor.





22

0-1.es/22

DC Light Bulb

High-Power Load




Don't forget to attach a heat sink to the MOSFET if are connecting a high-power load!

Up to 28A!



Light turns on when pin is set to HIGH

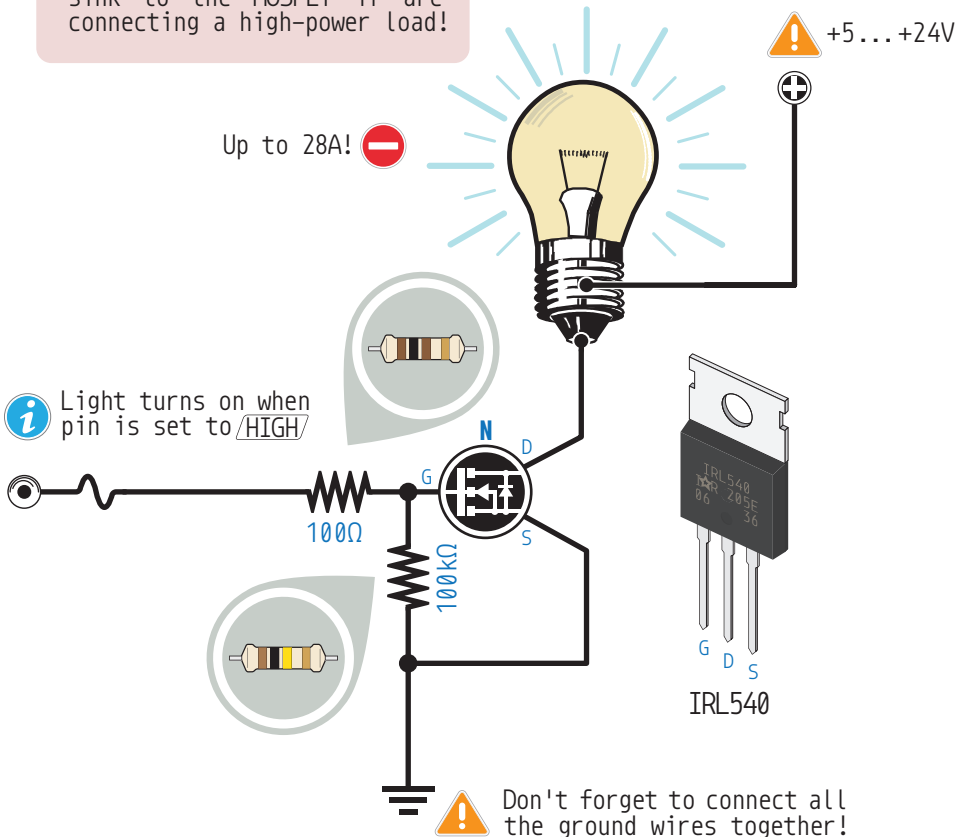

The 2N2222 transistor is rated at 800mA maximum, but you should leave a good safety margin. Many electronics projects designed for switching high-current DC loads use MOSFETs. If your lamp is greater than 2W, you need a MOSFET. The IRL540 can deliver its specified 28A continuous current at 5V.






0-1.es/23

23

DC Motor Basic Connections

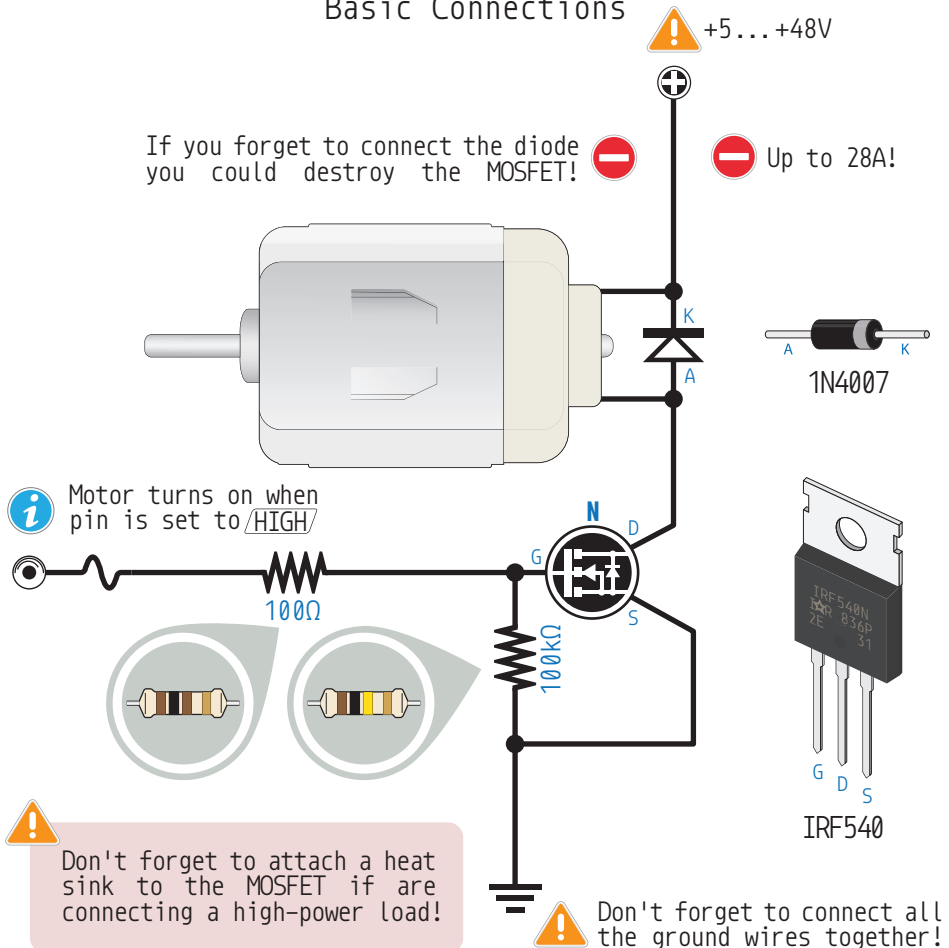

DC motors can create harmful voltage spikes due to their inductive nature. In this schematic the capacitor used for filtering the noise caused by the motor and the diode is used to protect the power supply from reverse voltage caused by the motor acting like an inductor.






24

0-1.es/24

Solenoid Basic Connections

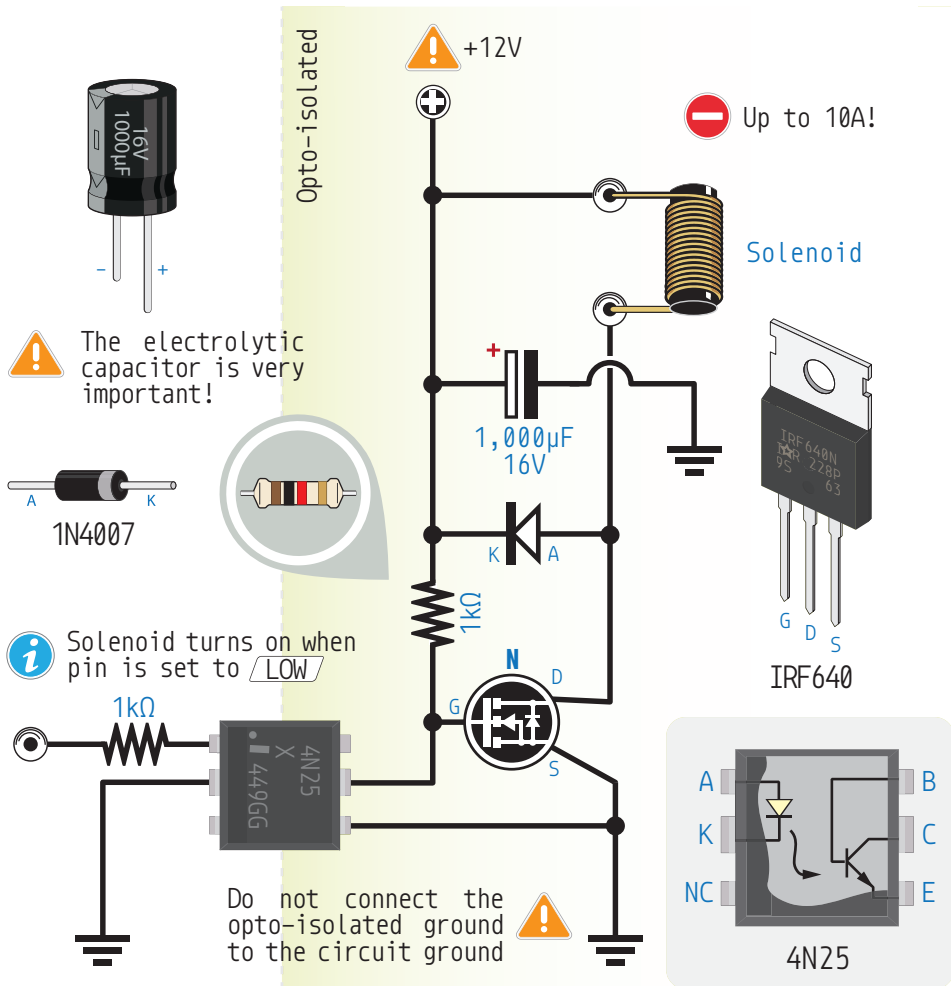

It's very important to use a large electrolytic capacitor in this circuit. The capacitor is used for supplying the current required by solenoid when the circuit is activated.






0-1.es/25

25

Relay

Basic Connections

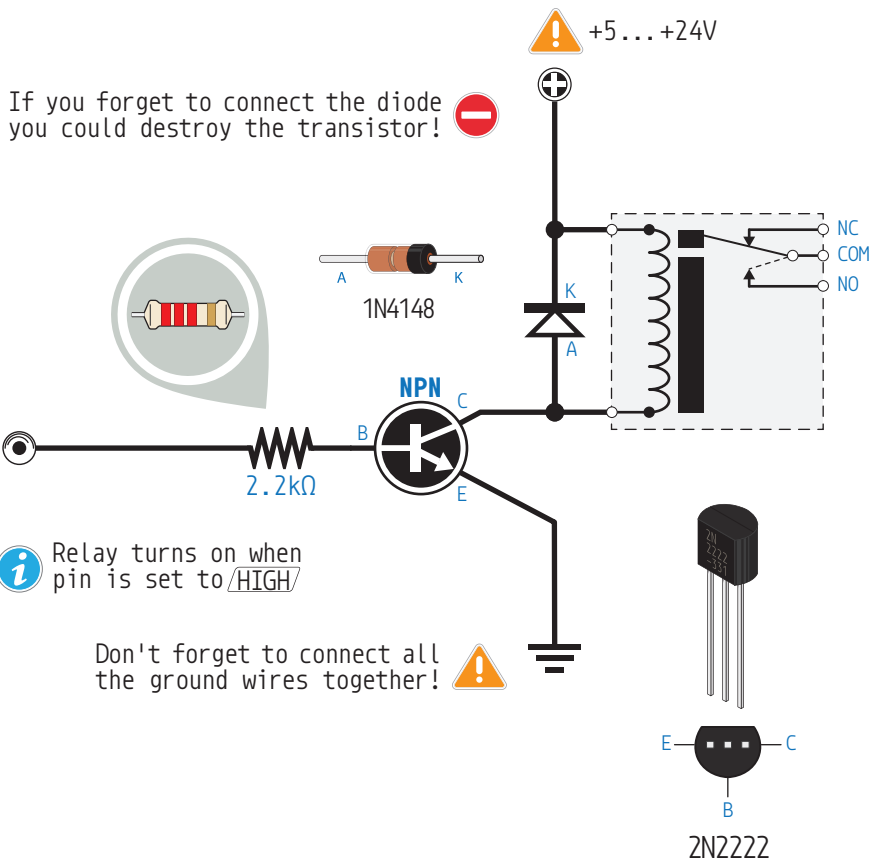

Relays have two types of contacts: NO and NC. NO stands for "Normally Open", whereas NC stands for "Normally Closed". When the relay is turned off, NO contacts are open and NC contacts are closed. On the other hand, when the relay is turned on, NO contacts are closed and NC contacts are open.





25

0-1.es/25

Relay Test Code

```
int relayPin = 9;
```

Assign variable *relayPin* as pin 9


```
void setup() {  
    pinMode(relayPin, OUTPUT);  
}
```

Initialize the pin as an OUTPUT

```
void loop() {  
    digitalWrite(relayPin, HIGH);  
    delay(3000);  
    digitalWrite(relayPin, LOW);  
    delay(3000);  
}
```

Turn the relay ON
Wait for 3 seconds
Turn the relay OFF
Wait for 3 seconds

Status LED for the Relay

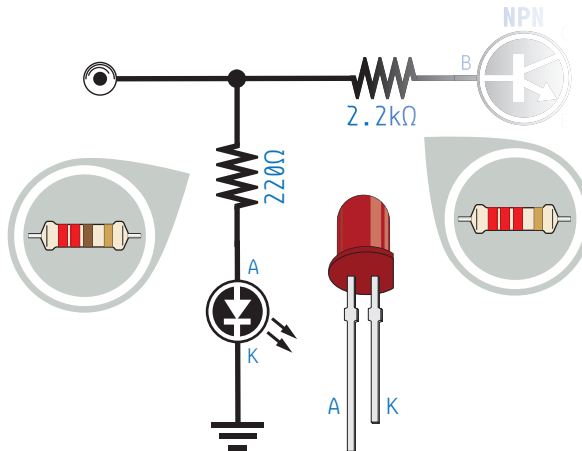

Relays offer complete isolation between the control circuit and the load. They can switch AC and DC and they can be very reliable and robust. Compared to transistors, relays are very slow. Relays are ON-OFF devices, whereas transistors can have their voltage drop varied.






0-1.es/26

26

Opto-Isolated Relay

Basic Connections

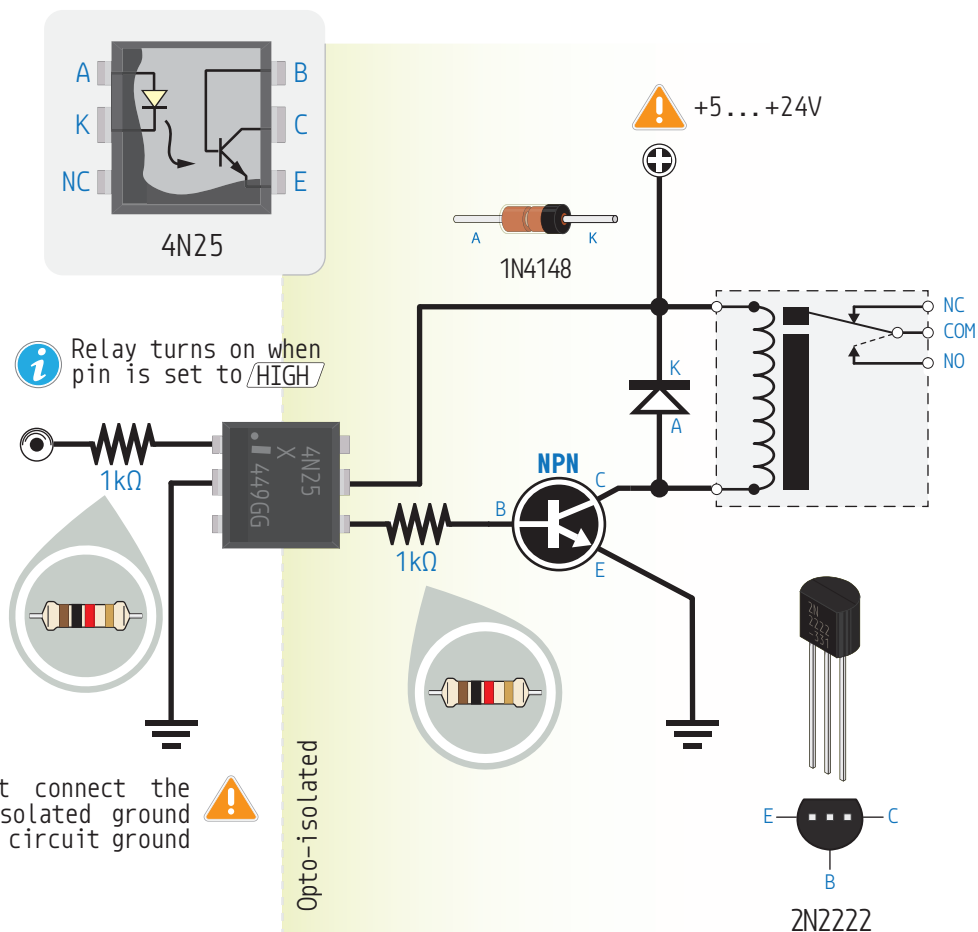

The purpose of an optocoupler is to isolate two parts of a circuit. Typical examples are industrial units with lots of interferences which affect the signals in the wires. If these interferences are not isolated, they can affect the correct functioning of the unit and cause errors.






27

0-1.es/27

Logic-Level MOSFET

Basic Connections

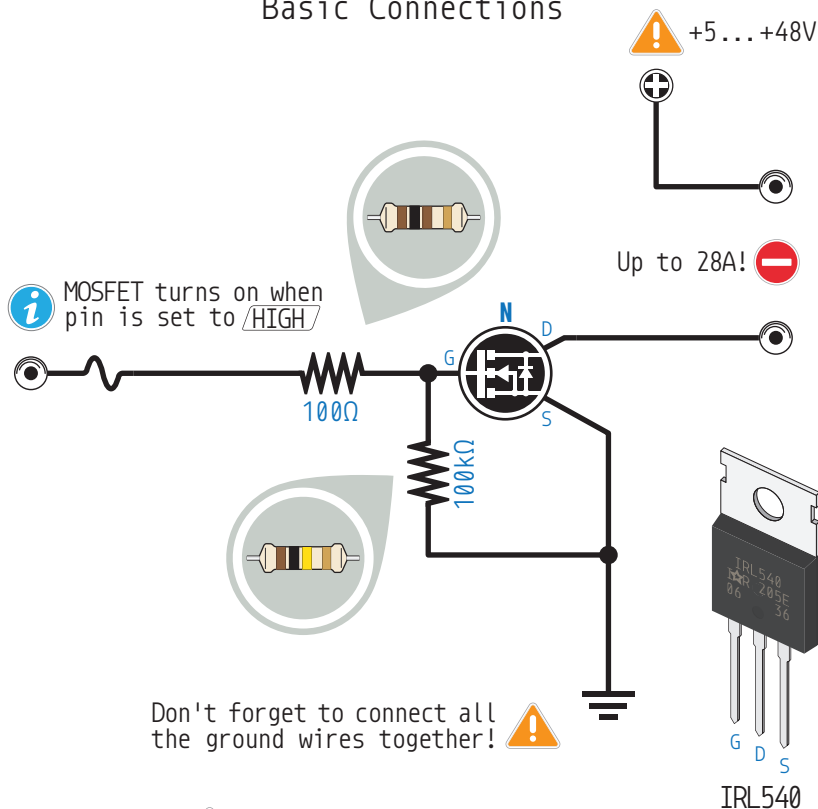

Don't forget to attach a heat sink to the MOSFET if are connecting a high-power load!



If you need to switch high-current and/or high-voltage loads with a microcontroller board, you need to use a MOSFET. This circuit is recommended only for switching purposes or in low frequency applications. The IRL540 can deliver its specified 28A continuous current at 5V.






0-1.es/28

28

Non-Logic-Level MOSFET

Using the 4N25 Optocoupler

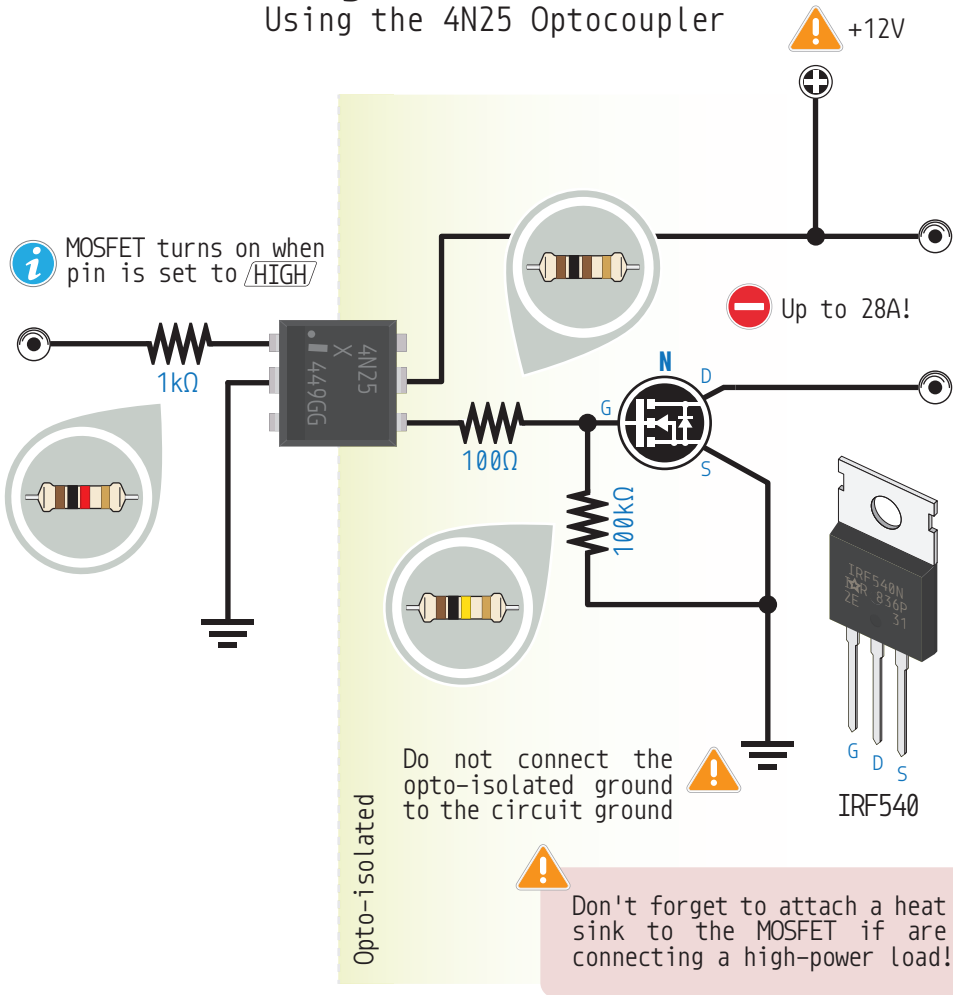

Use this circuit if you have a power FET (like the IRF series) and need some galvanic separation from your microcontroller circuit. This circuit is recommended only for switching purposes or in low frequency applications. The IRF540 can deliver its specified 28A of continuous current at 10V.






29

0-1.es/29

Servo

Basic Connections

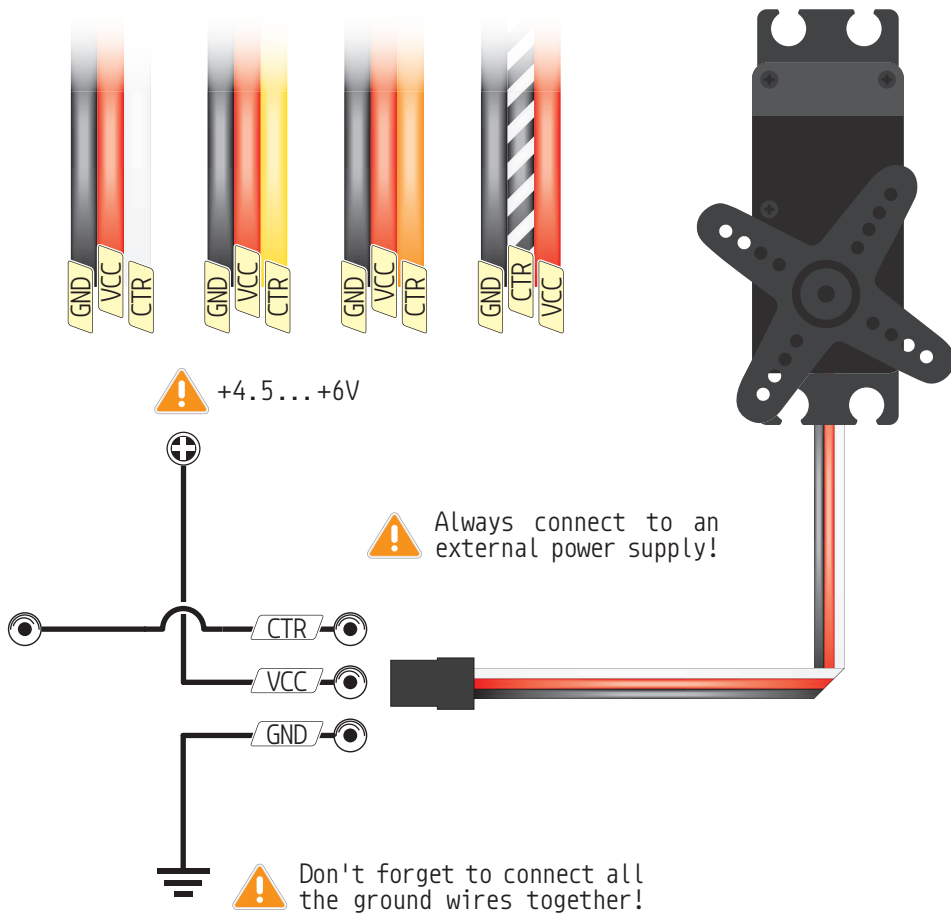

Standard servos are designed to receive electronic signals that tell them what position to hold. They are used, for example, to control the position of flaps, rudders and steering. Continuous rotation servos on the other hand turn at certain speed and direction. They are useful for driving wheels and pulleys.






0-1.es/30


30

Magnetic Buzzer

Basic Connections

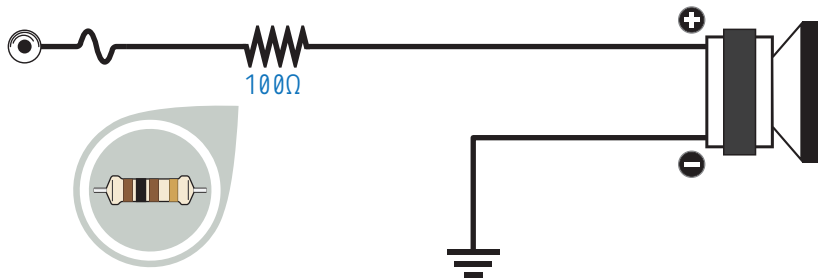

With External Power Supply

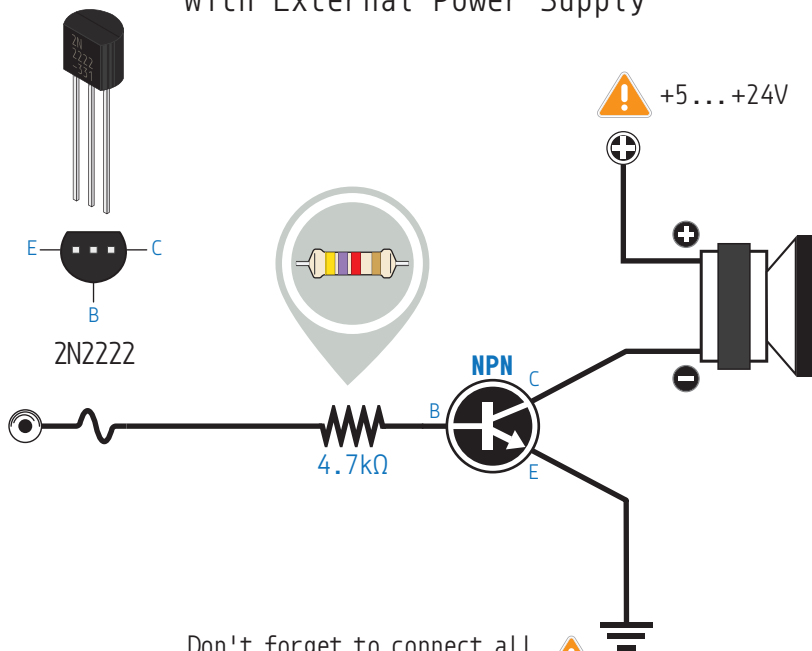

Don't forget to connect all the ground wires together! 






31

0-1.es/31


Piezo Buzzer

Basic Connections

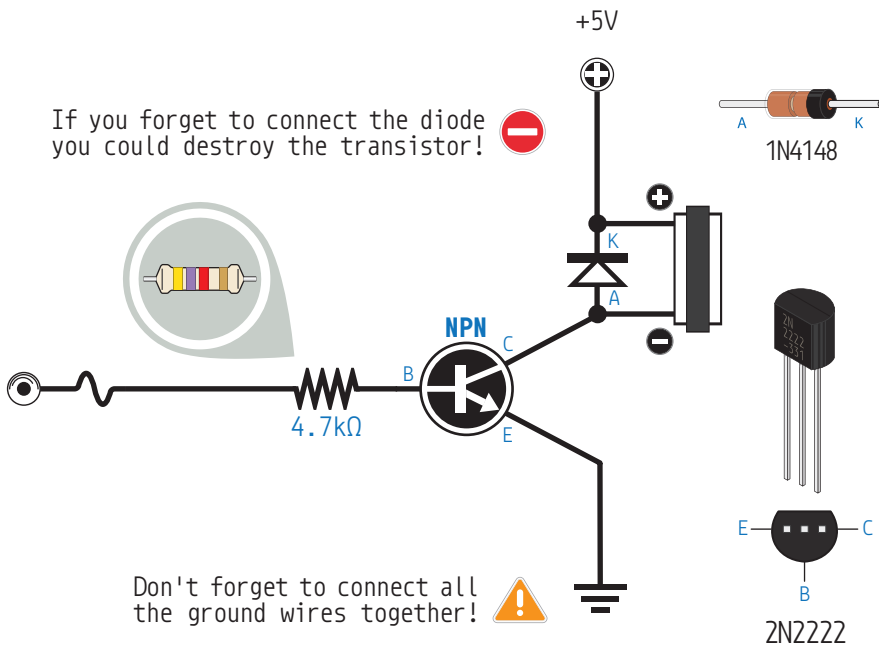If you forget to connect the diode you could destroy the transistor!



Note Frequency (Hz)

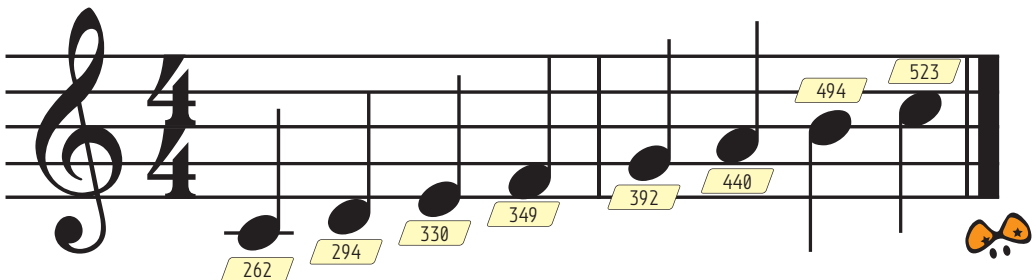




0-1.es/32

32

IR Detector

Basic Connections

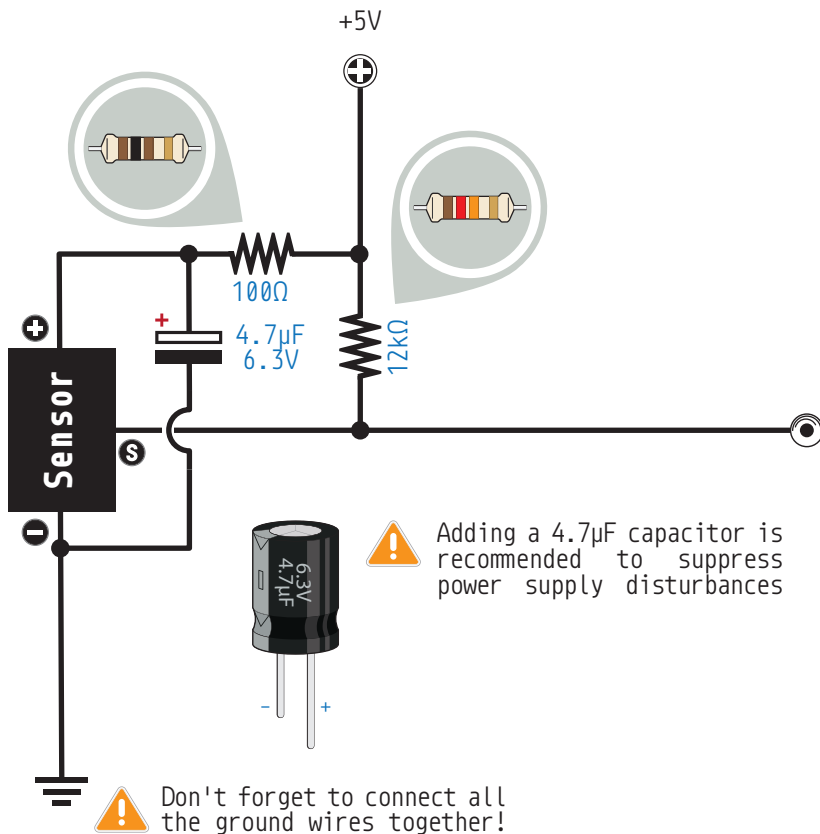

IR detectors are tiny microchips with a photocell that are tuned to detect infrared light. They are almost always used for remote control detection. IR detectors are digital out, either they detect a signal over a carrier (usually 38kHz) and output LOW (0V) or they do not detect anything and output HIGH (5V).





32

0-1.es/32


IR Detector

Common IR Detectors


TSOP4836
SFH5110




TSOP1836
NJL61H380

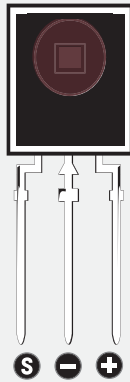

IS1U60

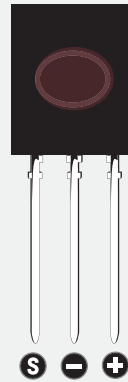

TSOP1736
SFH506
TFMS5360

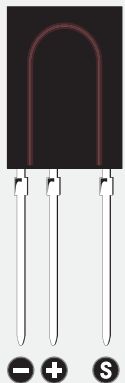

SFH505A



PIC12043S






0-1.es/33

33

IR Emitter

Basic Connections

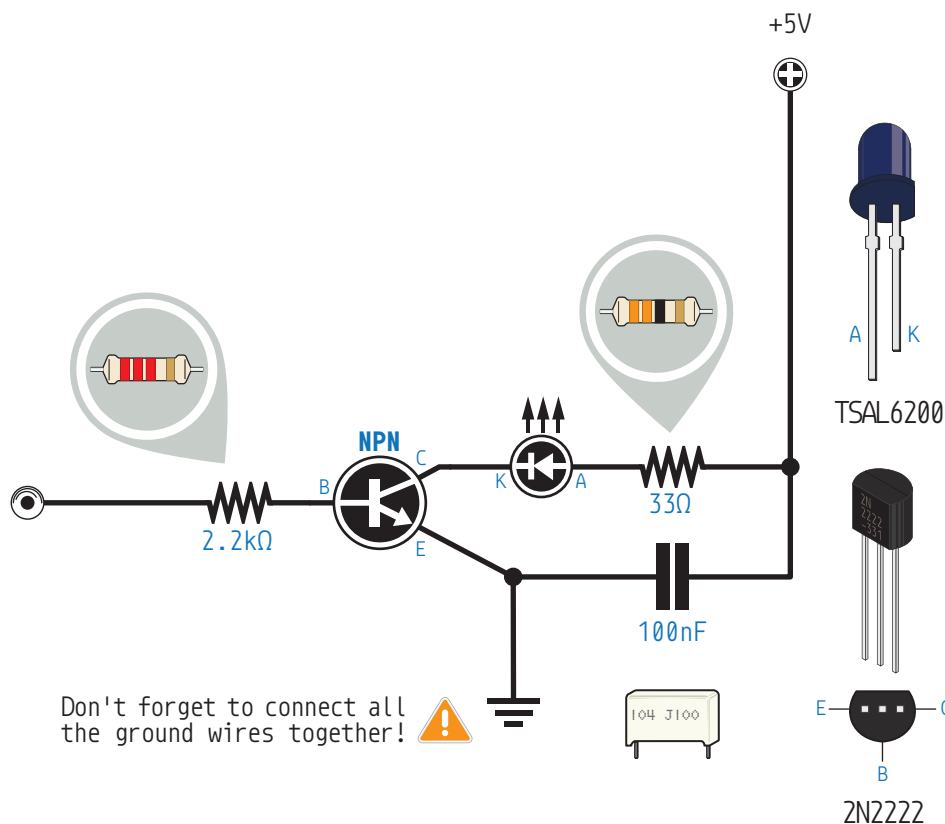

IR (infrared) communication is a popular, inexpensive, and easy to use wireless communication technology. IR light is very similar to visible light, except that it has a slightly longer wavelength. This means IR is undetectable to the human eye, making it perfect for wireless communication.






34

0-1.es/34

Constant-Current IR Emitter

Basic Connections

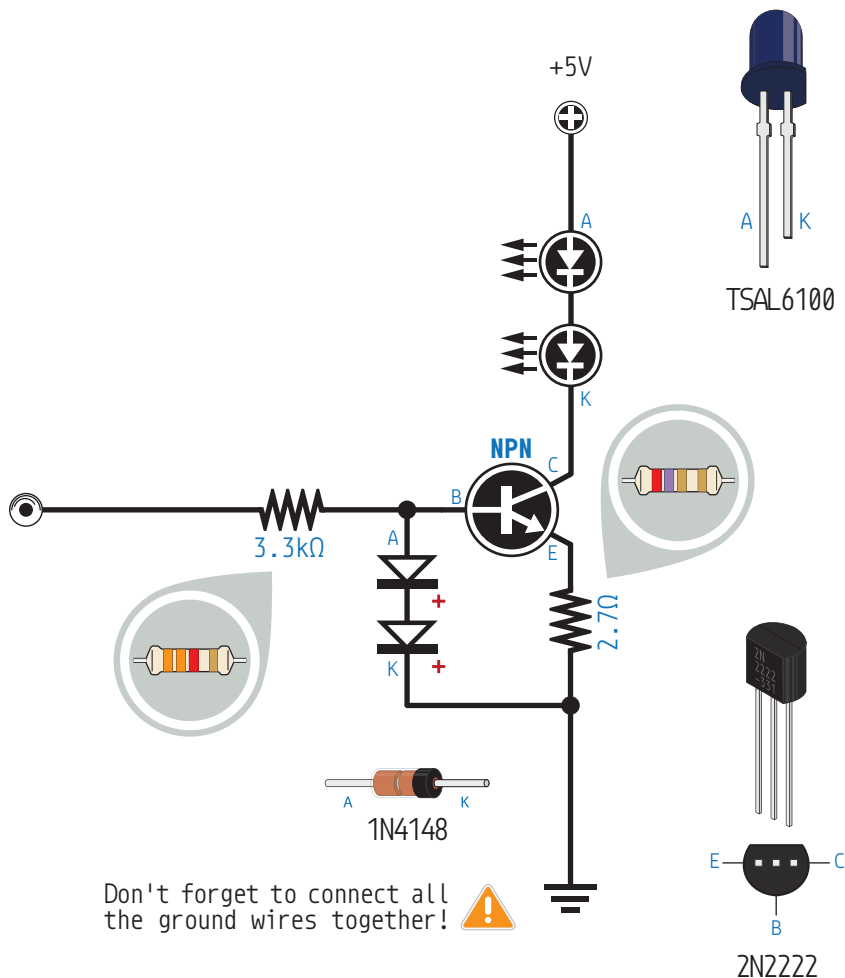




0-1.es/35

35

HD44780-Based LCD

Basic Connections

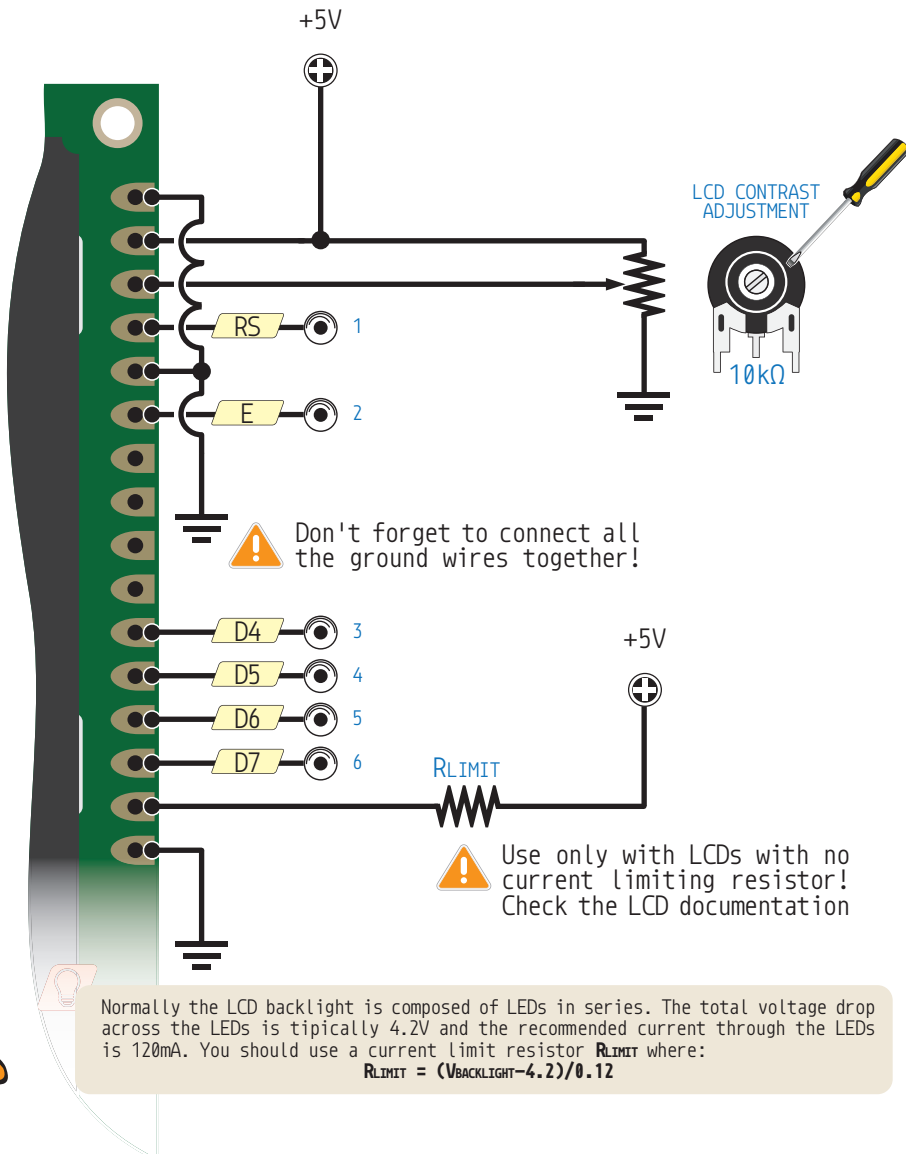




35

0-1.es/35


HD44780-Based LCD

Pinout

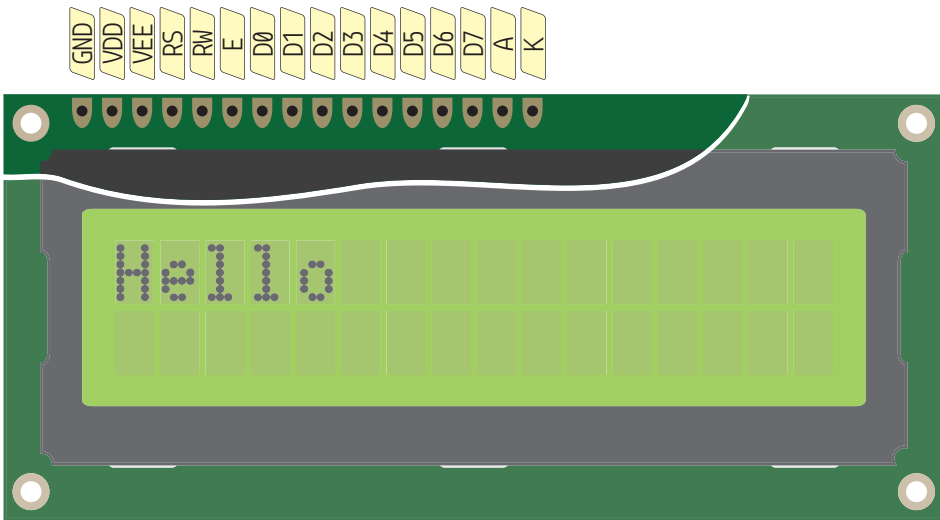

LCD Backlight Control

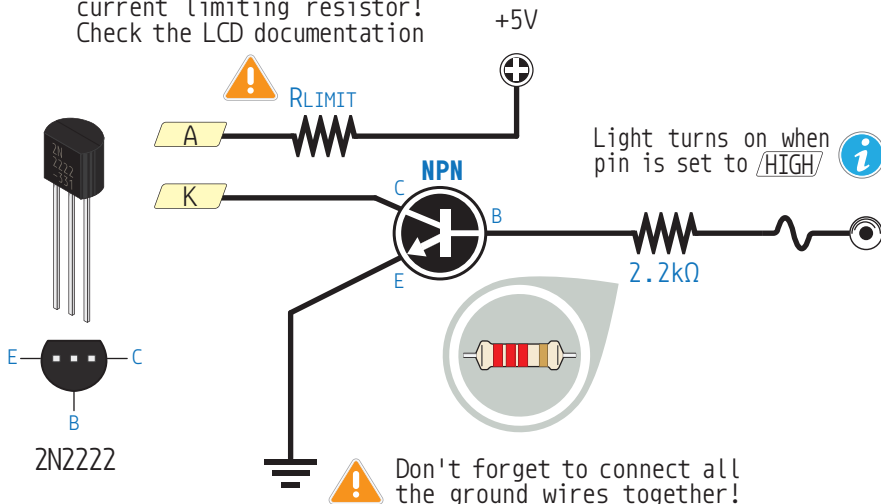Use only with LCDs with no
current limiting resistor!
Check the LCD documentation






0-1.es/36

36

HD44780-Based LCD Via I²C

Using the PCF8574 I/O Expander

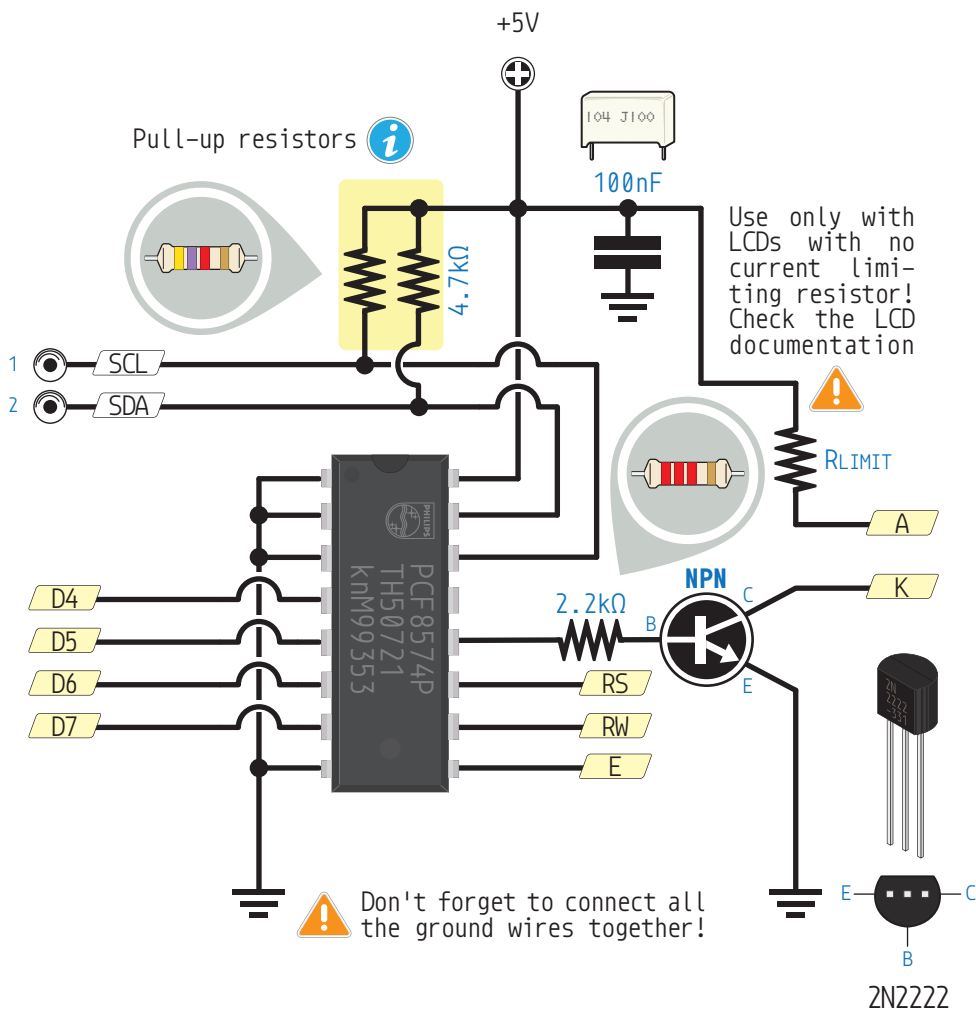




36

0-1.es/36

PCF8574

Pinout

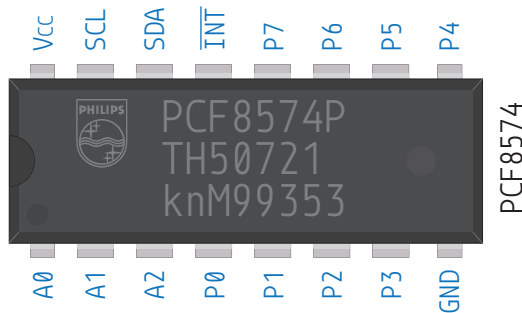

I²C Pull-Up Resistors

I²C is a popular communication protocol in embedded systems. When interfacing with the slave device a pull-up resistor is needed on each bi-directional line. This is just two wires, called **SCL** and **SDA**. **SCL** is the clock line that is used to synchronize all data transfers over the I²C bus. **SDA** is the data line. The **SCL** and **SDA** lines are connected to all devices on the I²C bus. There needs to be a third wire which is just the ground. Both **SCL** and **SDA** lines are “open drain” drivers. What this means is that the chip can drive its output low, but it cannot drive it high. For the line to be able to go high you must provide pull-up resistors to the 5V supply. There should be a resistor from the **SCL** line to the 5V line and another from the **SDA** line to the 5V line. **You only need one set of pull-up resistors** for the whole I²C bus, not for each device.






0-1.es/37

37

Nokia 5110 LCD

Basic Connections

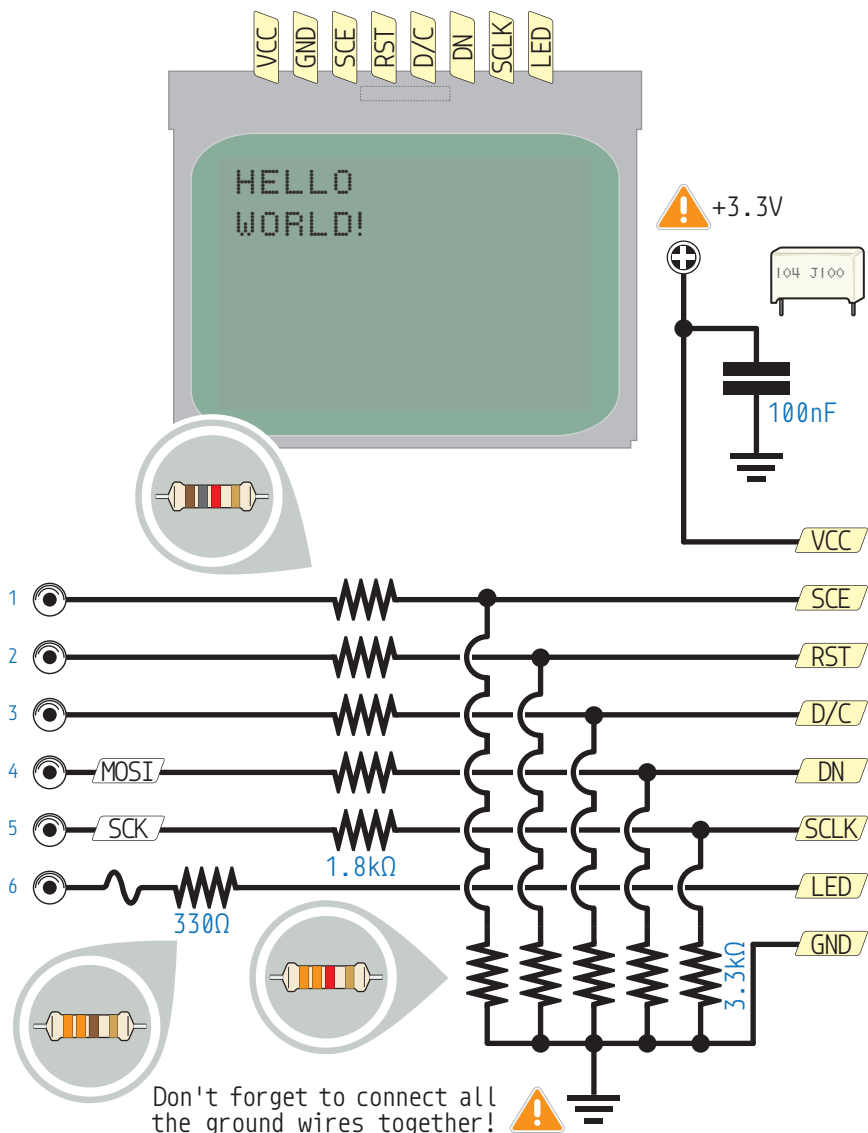




38

0-1.es/38

OLED LCD

Basic Connections

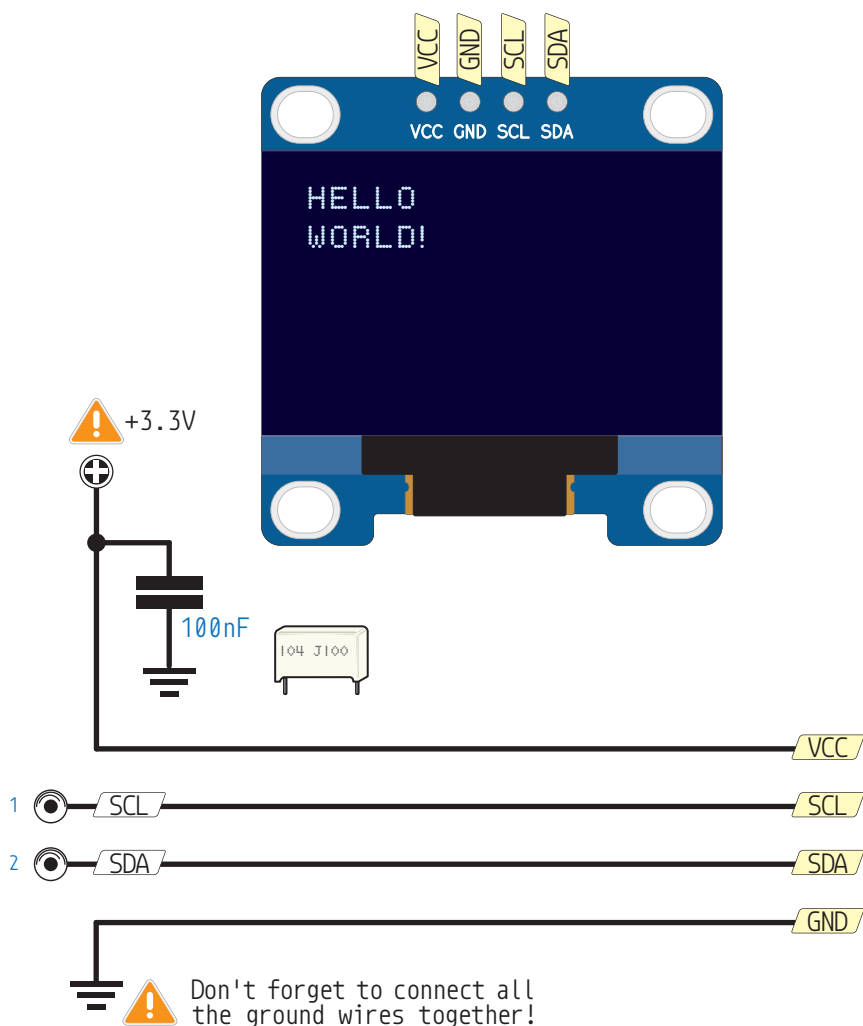




0-1.es/39

39

UC1701 128x64 LCD

Basic Connections

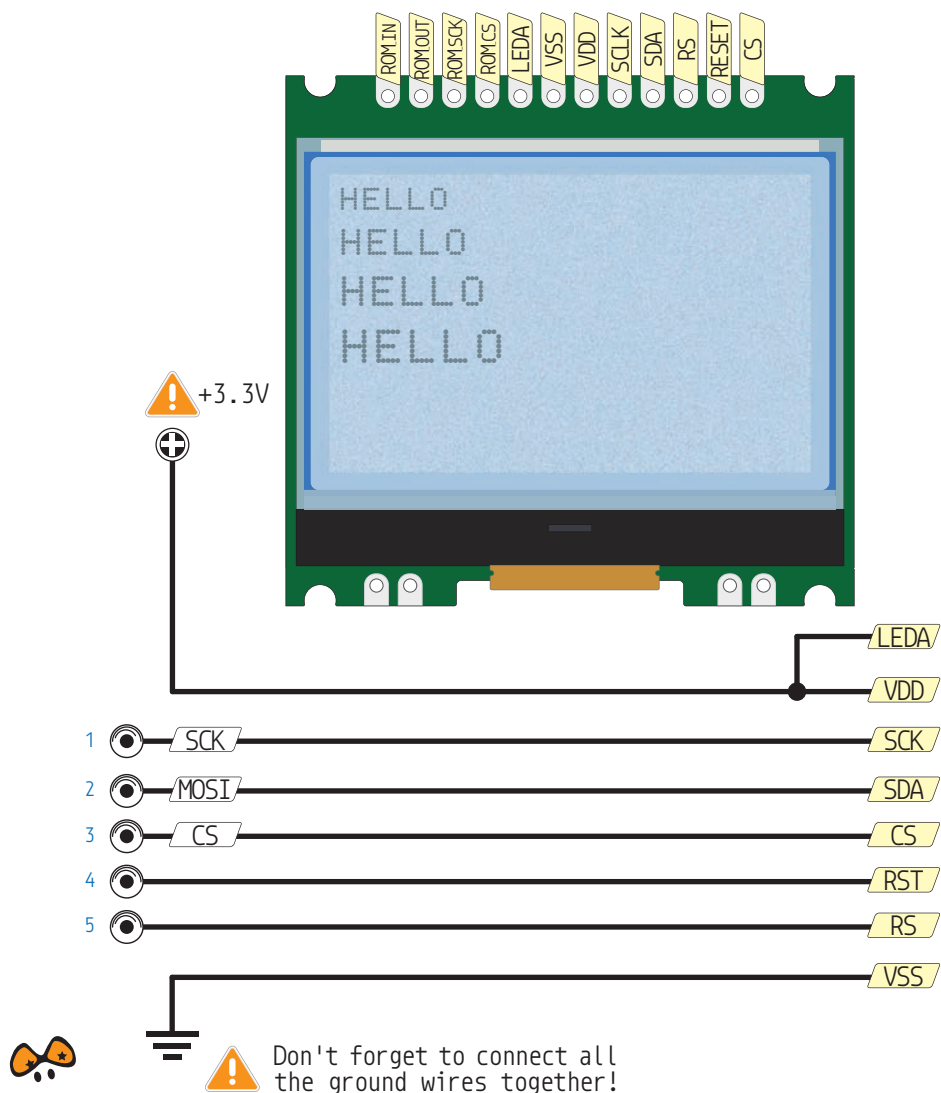




40

0-1.es/40

ST7032i LCD

Basic Connections

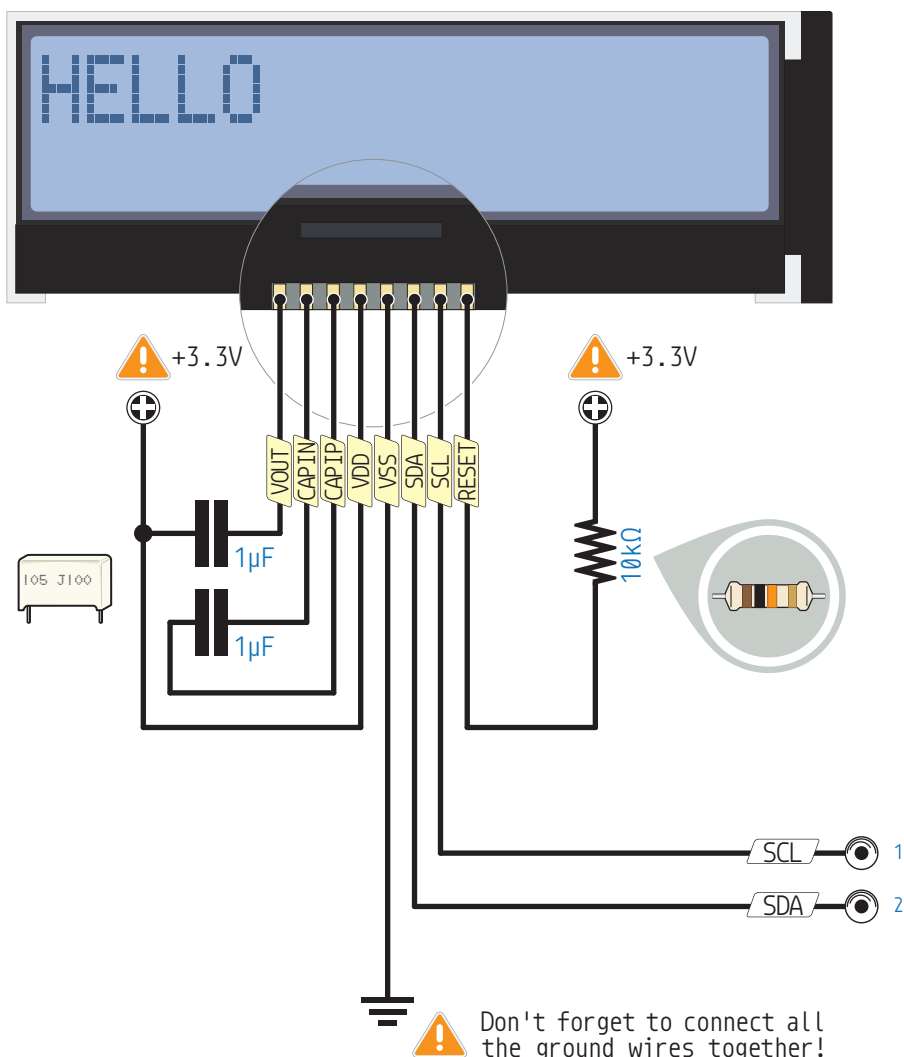




0-1.es/41

41

DS Touchscreen

Basic Connections

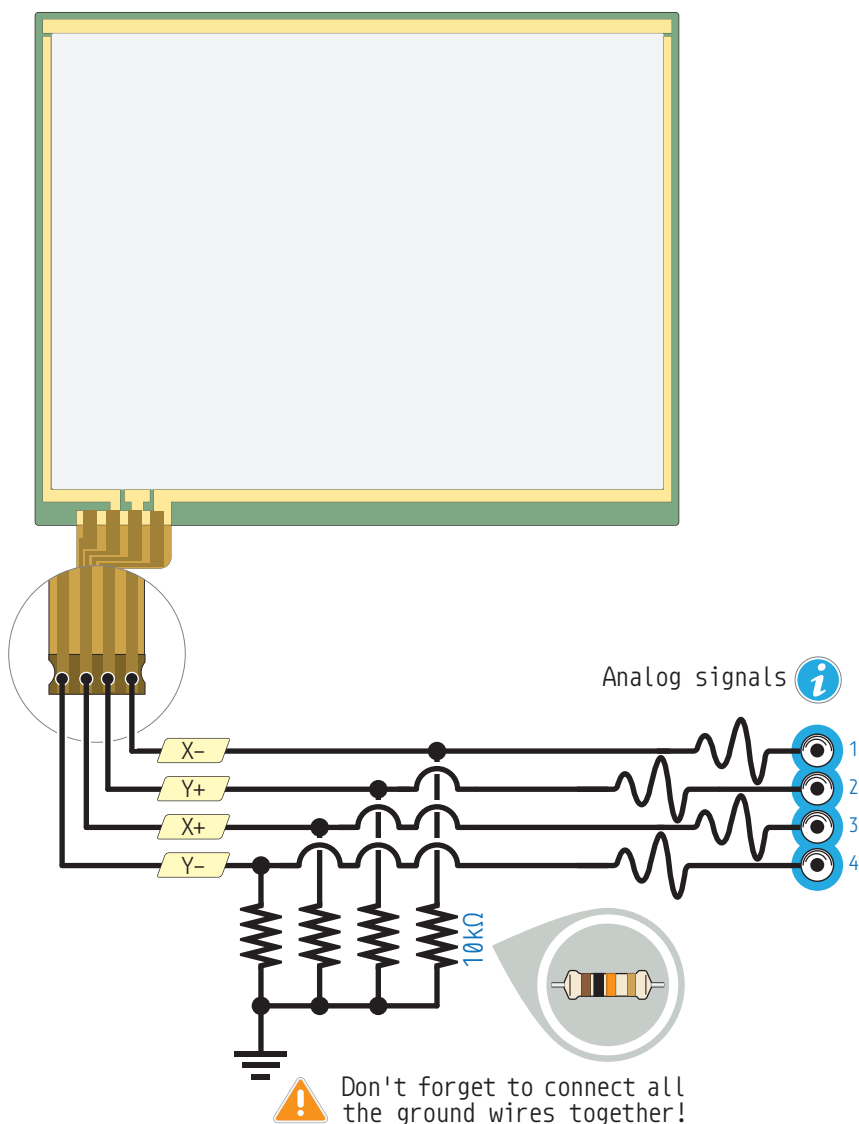




42

0-1.es/42

Simple Touch Sensor

Basic Connections

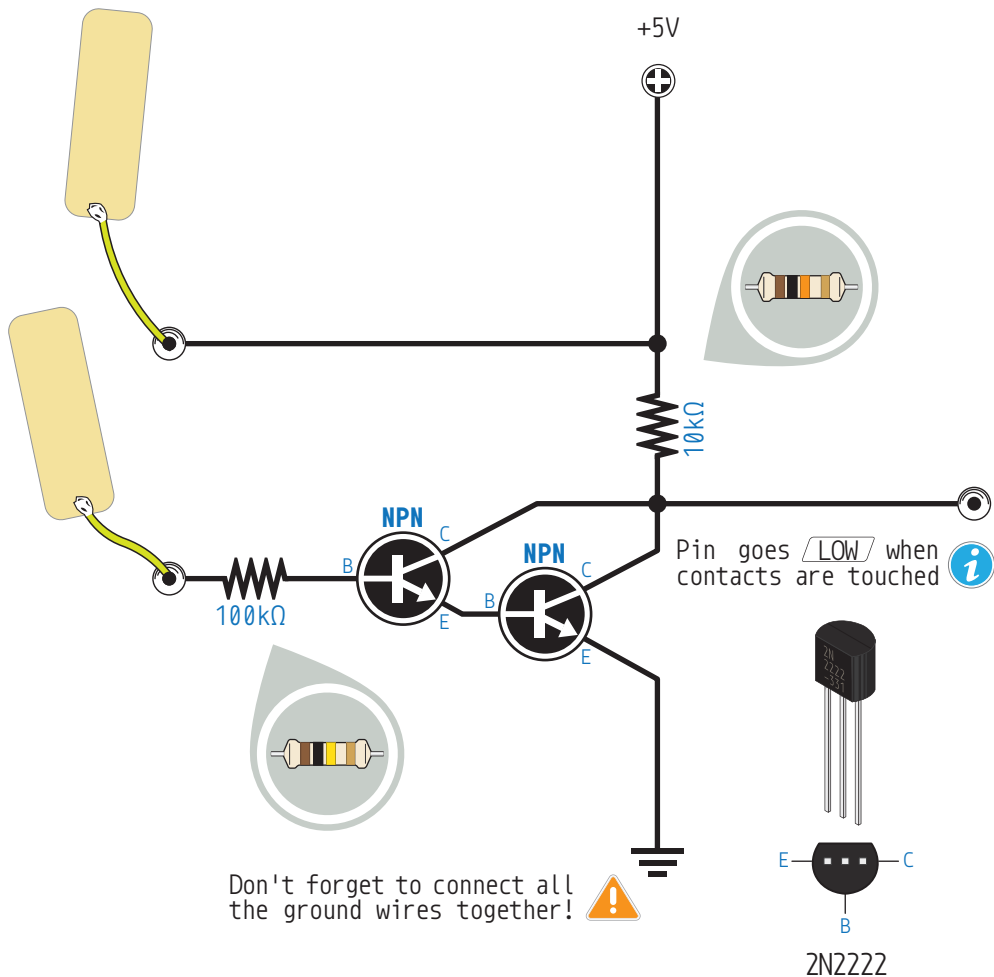

This simple touch sensor is based on a Darlington configuration of transistors. They behave like a single transistor with a very high current gain, making it sensitive enough to respond to the small current passing through your body when you touch the metallic plates, activating the circuit.








0-1.es/43

43

Pushbutton

Basic Connections

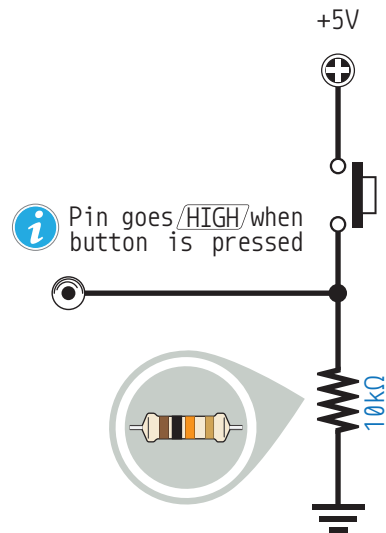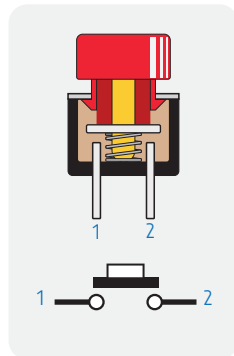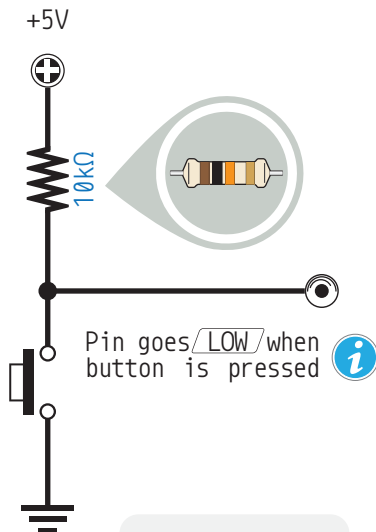

Don't forget to connect all the ground wires together!



Pushbuttons or switches connect two points in a circuit when you press them. If you don't use the pull-up or pull-down resistor, the input pin is "floating" and will randomly return either HIGH or LOW values. Don't forget to connect all the ground wires together!





43

0-1.es/43

Pushbutton

Test Code

```
int LEDPin = 13;  
int SWITCHPin = 4;  
int val;
```

Assign variable *LEDPin* as pin 13
Assign variable *SWITCHPin* as pin 4
Variable for reading the pin status

```
void setup() {  
  pinMode(LEDPin, OUTPUT);  
  pinMode(BUTTONPin, INPUT);  
}
```

Initialize the pin as an *OUTPUT*
Initialize the pin as an *INPUT*

```
void loop() {  
  val = digitalRead(SWITCHPin);  
  if (val == LOW) {  
    digitalWrite(LEDPin, HIGH);  
  }  
  if (val == HIGH) {  
    digitalWrite(LEDPin, LOW);  
  }  
}
```

Read input value and store it in *val*
Check if the button is pressed
Turn LED on

Check if the button is not pressed
Turn LED off

Using Internal Pull-Up Resistors



Don't forget to connect all the ground wires together!






0-1.es/44

44

Pushbutton to 12V

Basic Connections

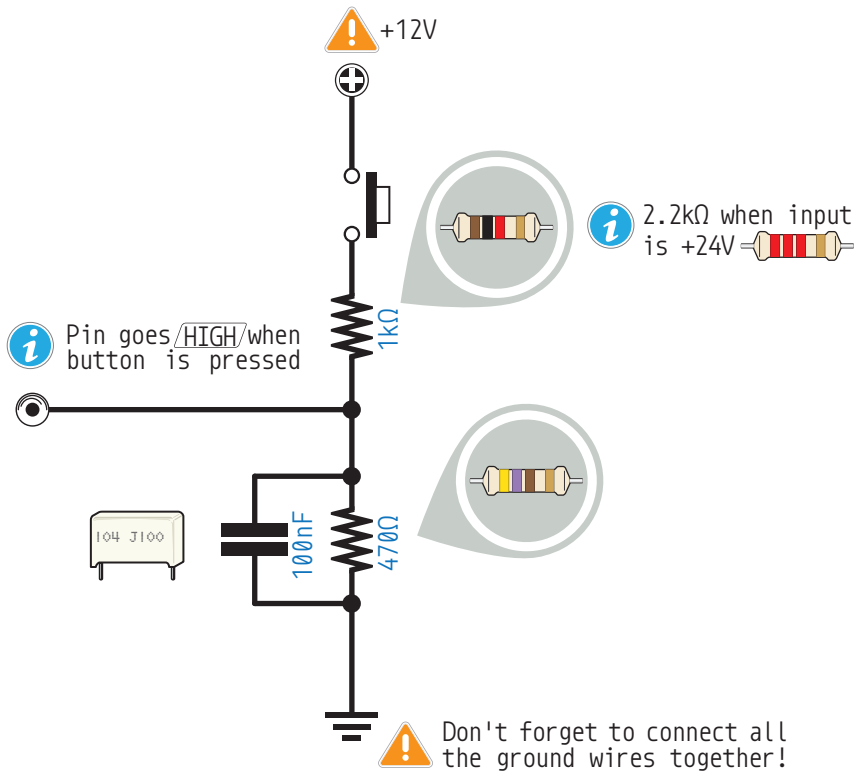

12V signals are often found in many electronic systems and appliances, as signal voltage swings of 12V are advantageous to increase noise immunity. Electronic noise captured by the input wiring will be reduced by about 2/3 thanks to the resistor divider. Noise can be further reduced by the 100nF capacitor.







45


0-1.es/45

Toggle Switch

Basic Connections

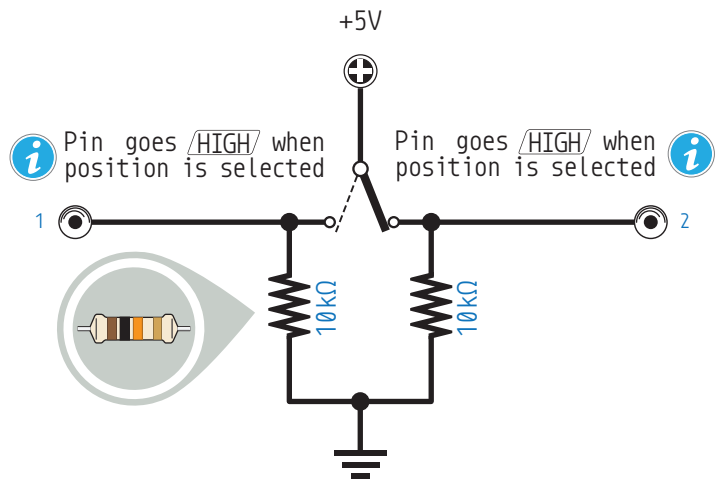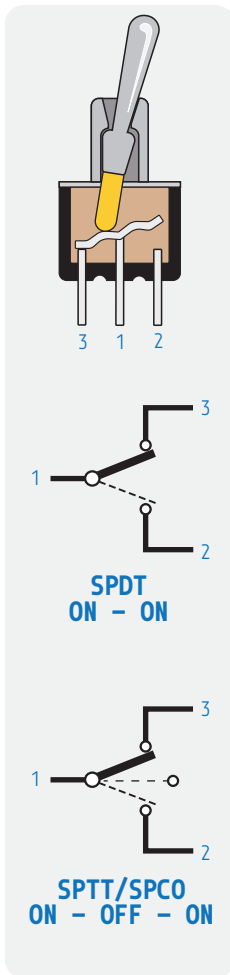

Using One Analog Input

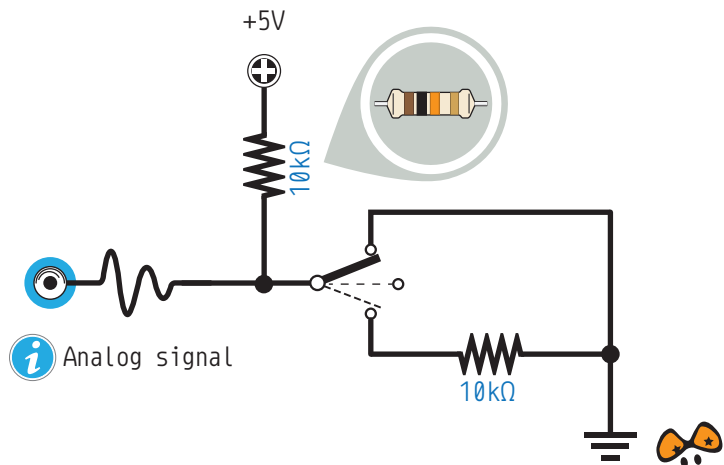




0-1.es/46

46

Multiple Pushbuttons

Basic Connections

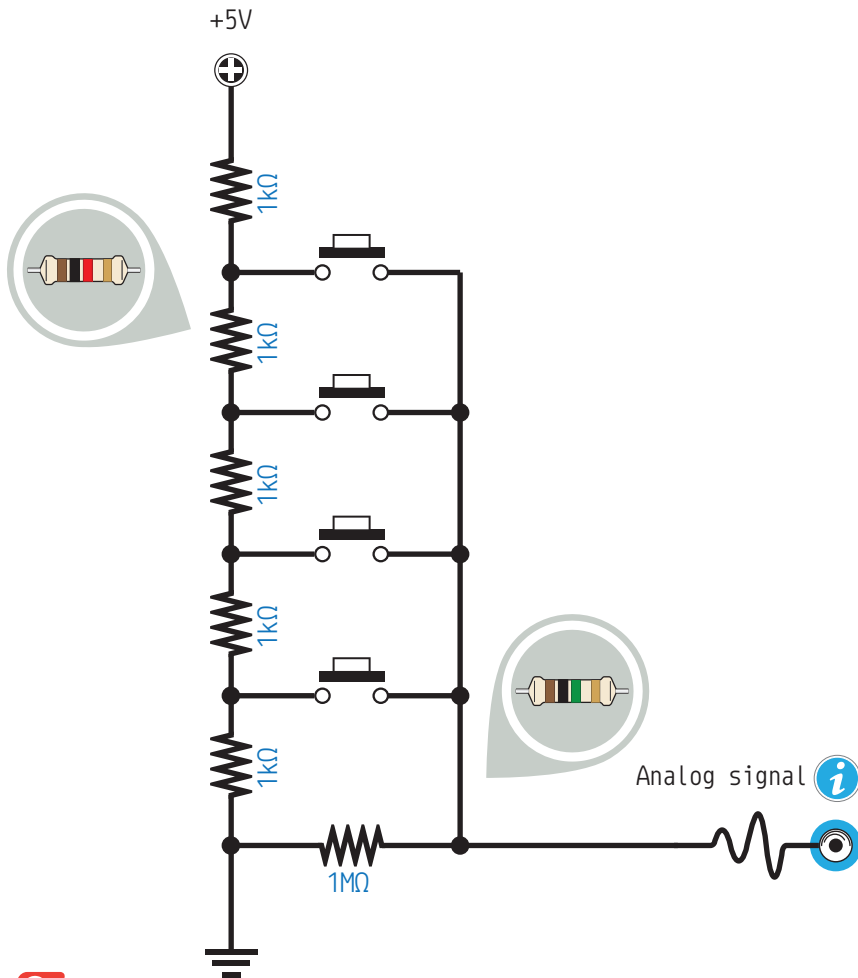

This circuit cannot handle simultaneous button presses. In order to do that, you could use resistors with values at 2x increments with respect to the previous one (e.g., $1\text{k}\Omega$, $2\text{k}\Omega$, $4\text{k}\Omega$, $8\text{k}\Omega$). Hence by checking the voltage value, you should be able to tell which buttons are pressed simultaneously.






47


0-1.es/47

Rotary Encoder

Using Internal Pull-Up Resistors

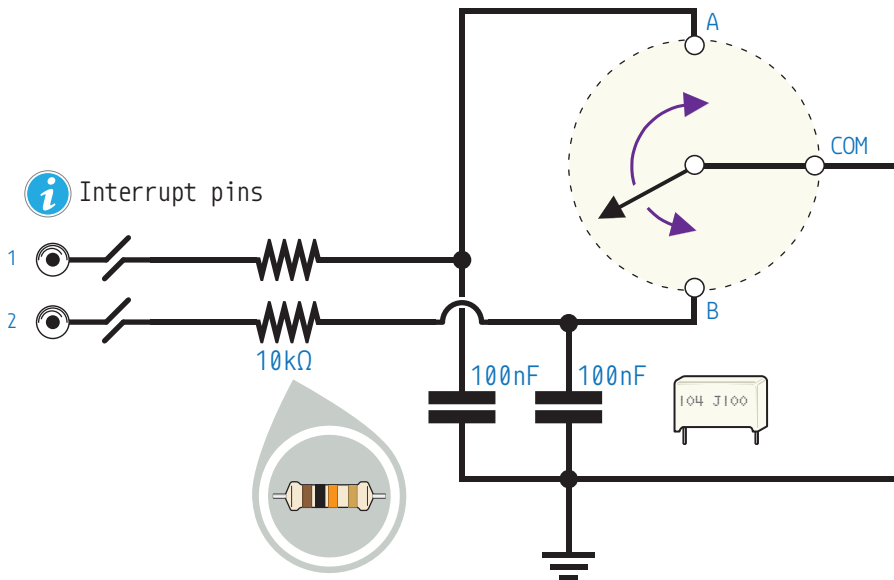

How Rotary Encoders Work

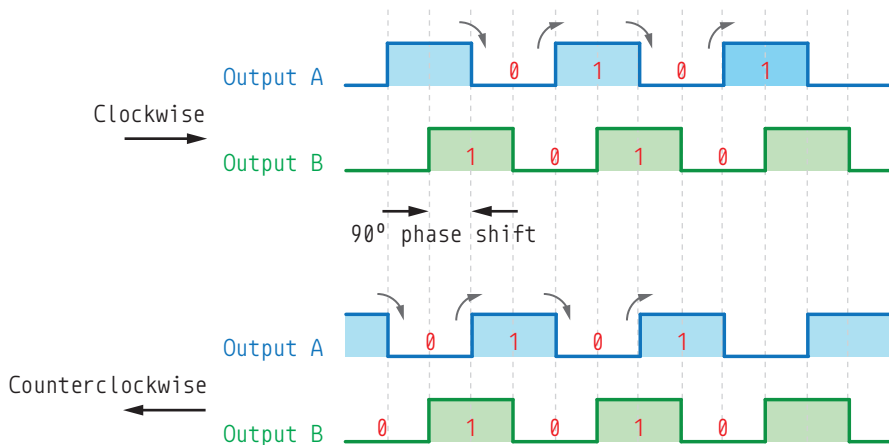




0-1.es/48


48

Rotary Encoder

Basic Connections

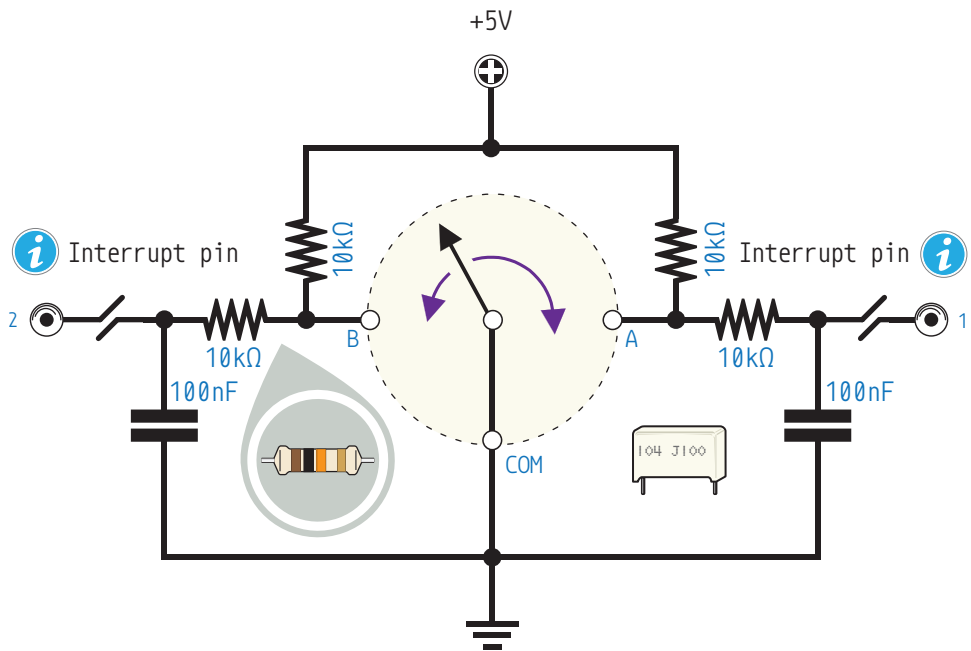

Inside a Rotary Encoder

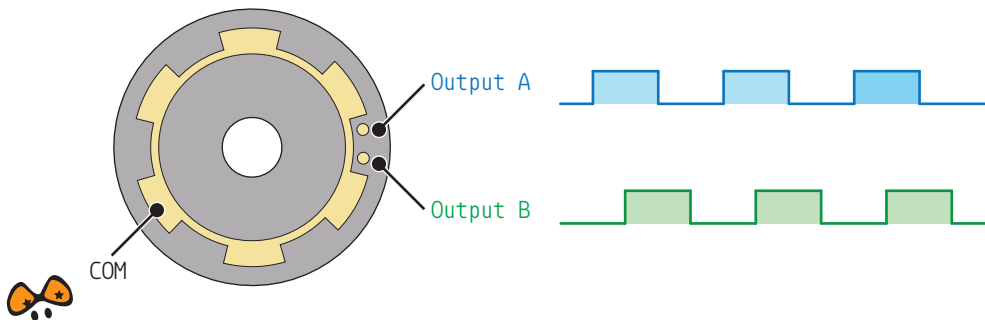




49

0-1.es/49

Simple Debouncing Circuit

Basic Connections


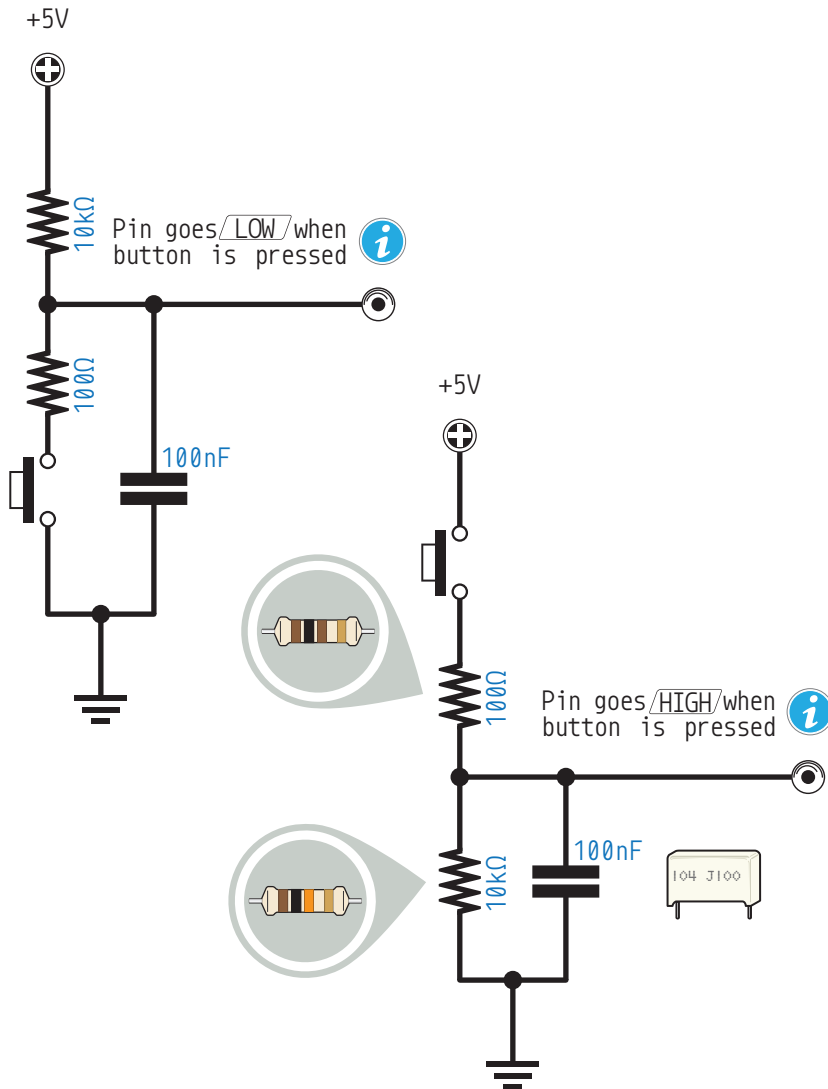




Debouncing

Theory

Contact bounce is a common problem associated with mechanical switches and relays. Switch and relay contacts are made up of spring metals which are forced to contact each other by an actuator. While they collide with each other there is a possibility of rebounding for some time before they make a stable contact. As a result of this effect there will be ON/OFF transitions generated as the contacts rapidly open and close. Contact bounce is an **undesired behavior** which generates multiple transitions for a single user input.

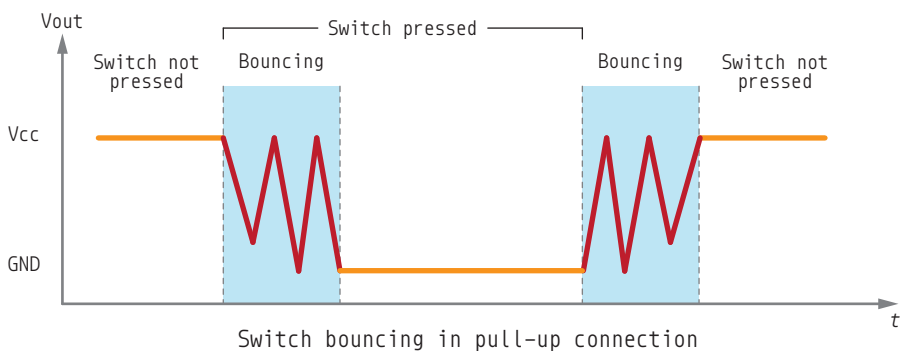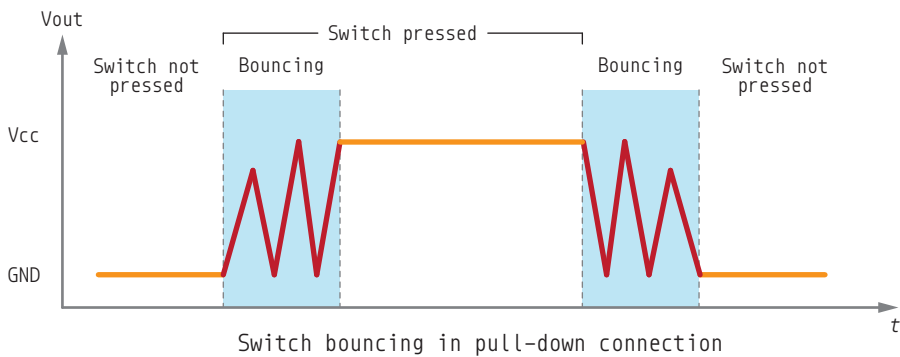




51

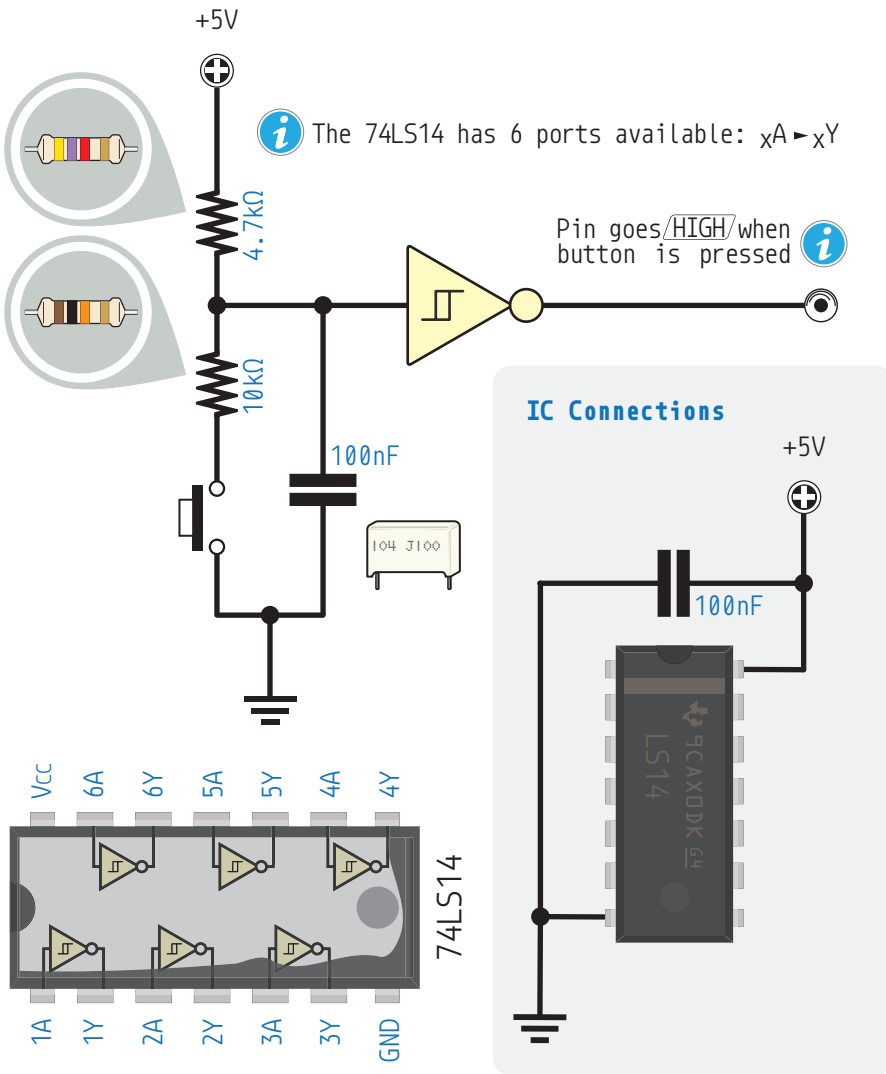0-1.es/51

Debouncing

Using the 74LS14 Schmitt Trigger Inverter






0-1.es/52

52

Rotary Encoder Debouncing

Using the 74LS14 & the 74LS74

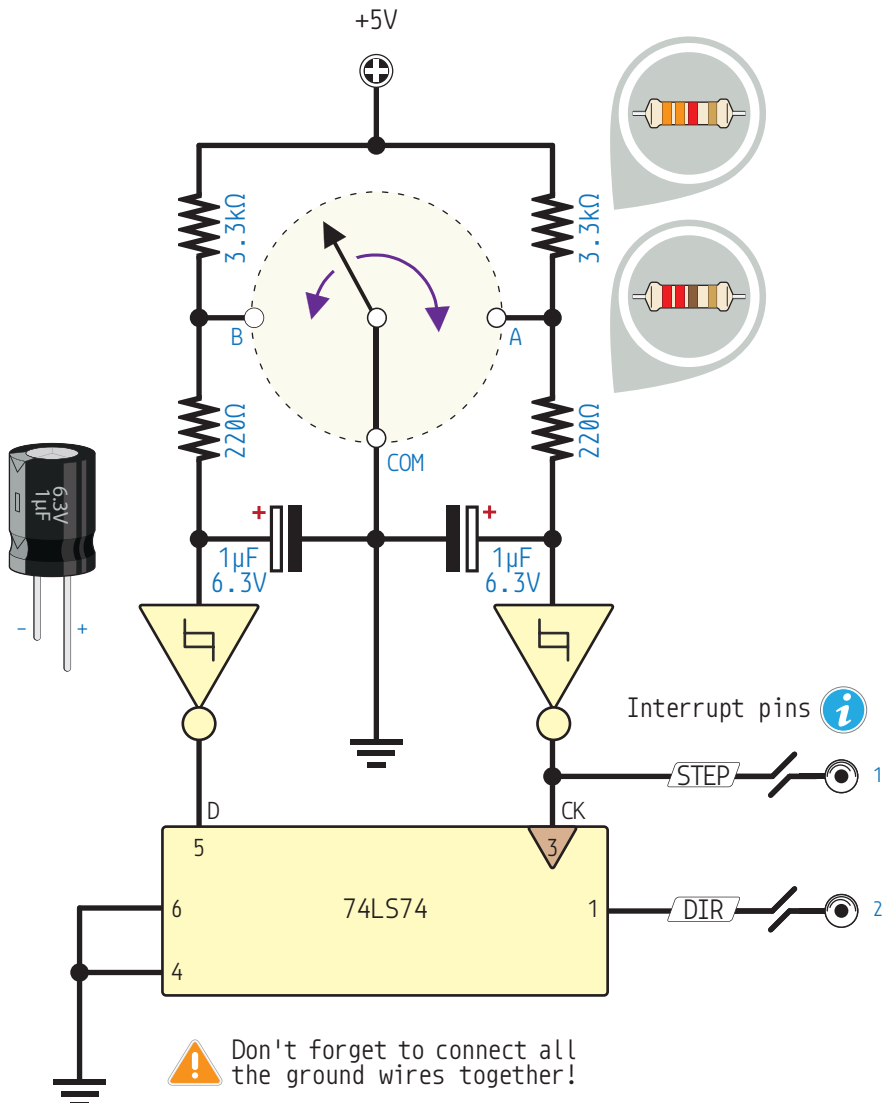







52

0-1.es/52

74LS14 & 74LS74

Pinout

74LS14 & 74LS74 Connections

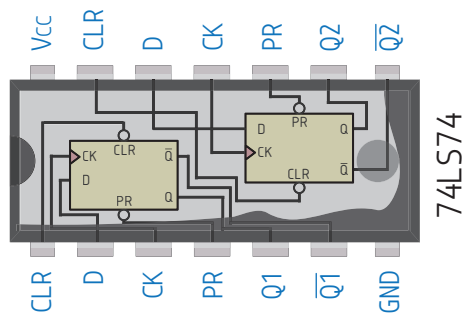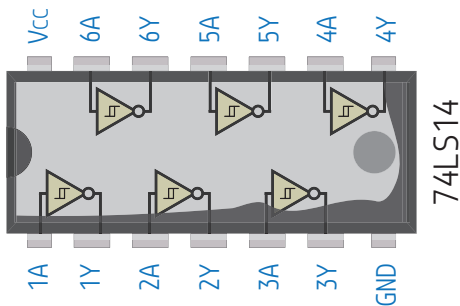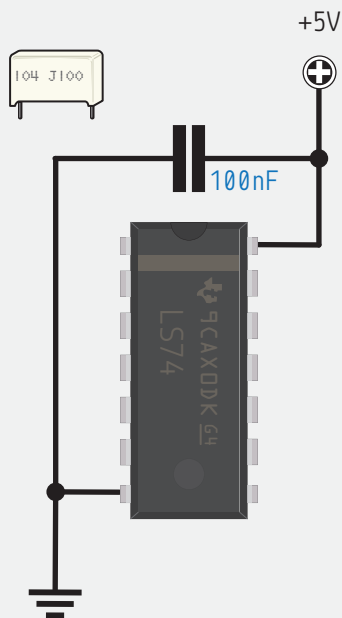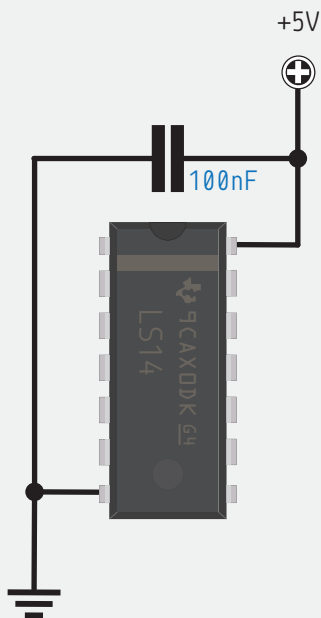






53

0-1.es/53

Keypad

Pinout

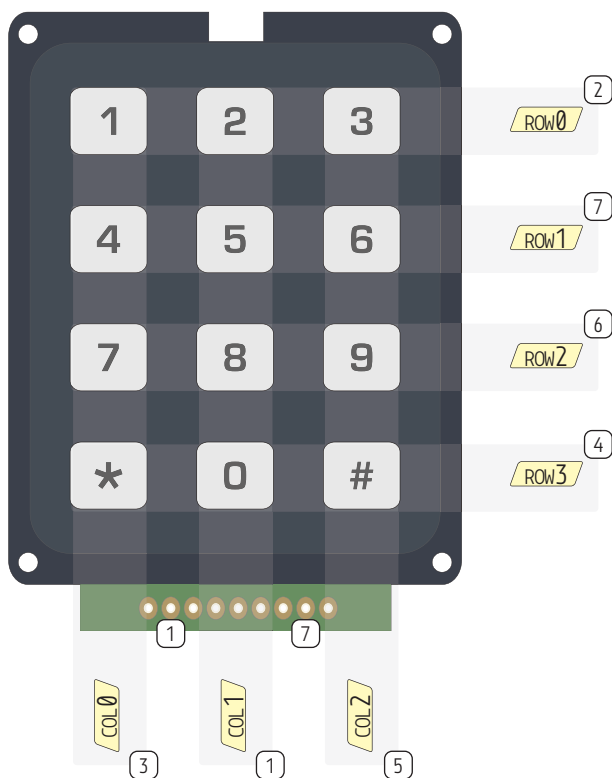

Keypads are ubiquitous in many electronic appliances and are used as input devices. Note that computer and calculator keypads have a different key arrangement compared to telephones, locks or ATMs.






0-1.es/54

54

Membrane Keypad

Pinout

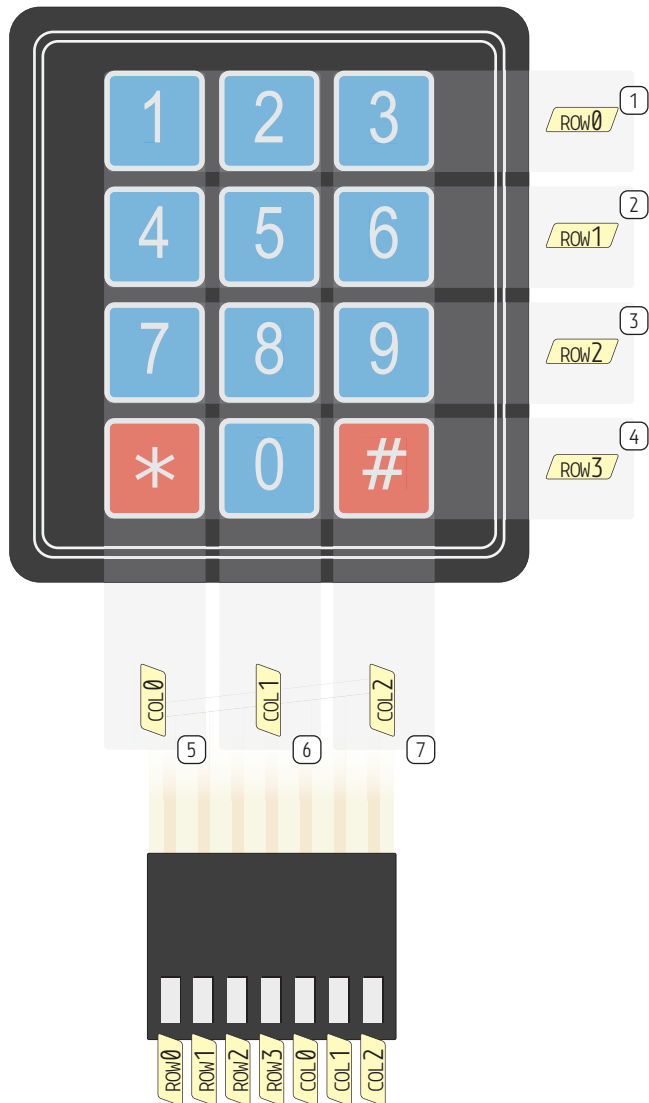




54

0-1.es/54

Keypad With 1 Analog Pin

Basic Connections

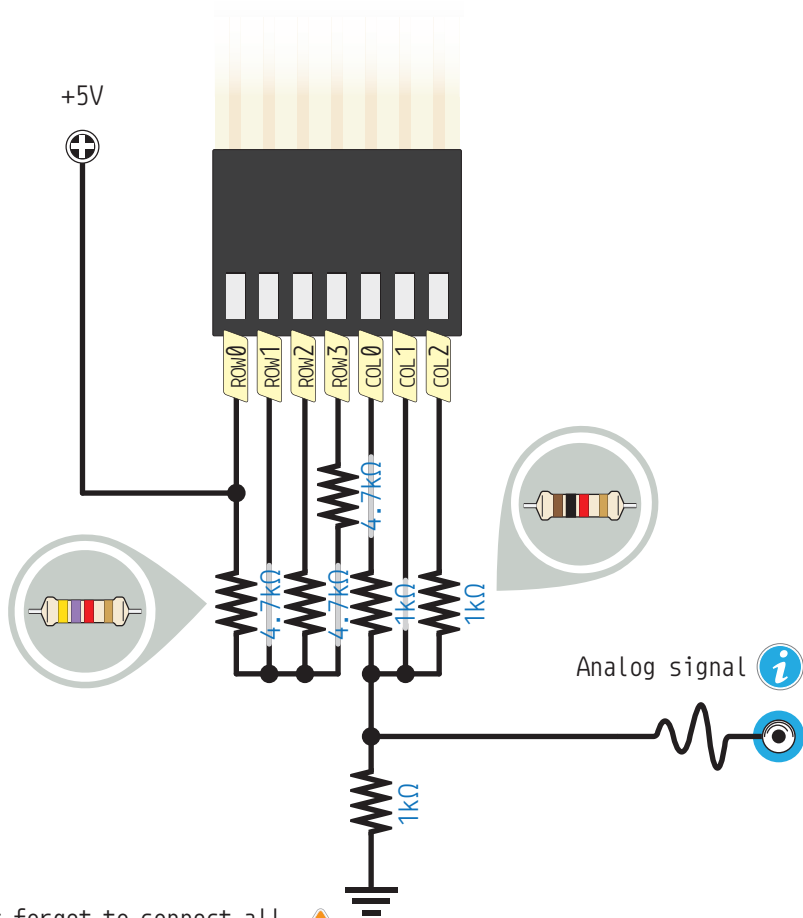

Don't forget to connect all the ground wires together! ⚠️







0-1.es/55

55

Thumbwheel Switch

Basic Connections

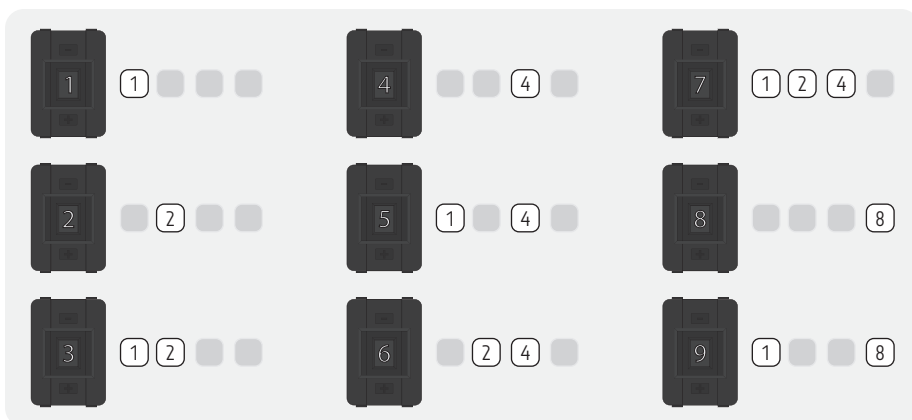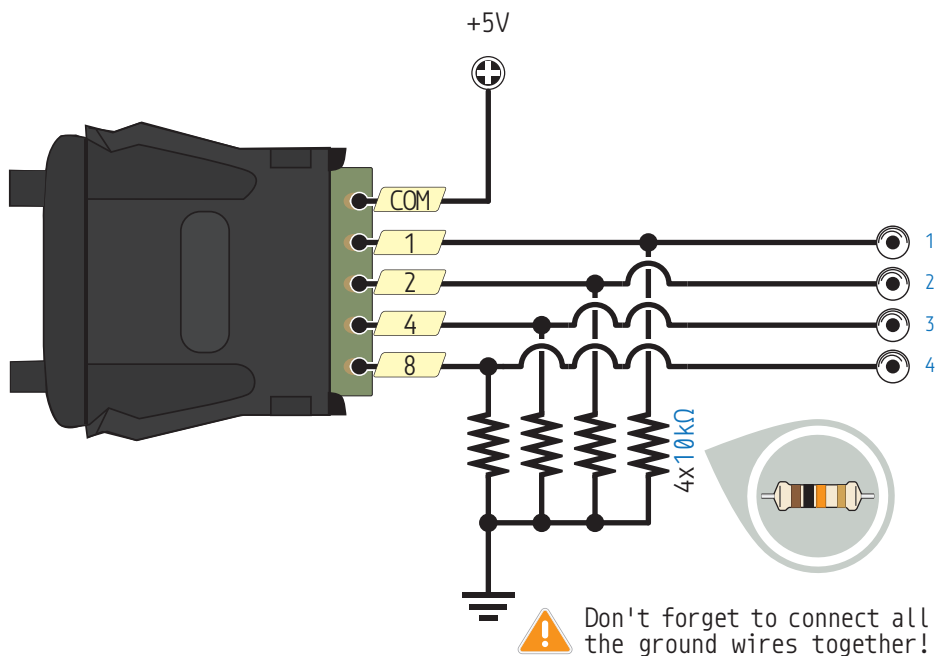





56

0-1.es/56

Rotary Switch

Basic Connections

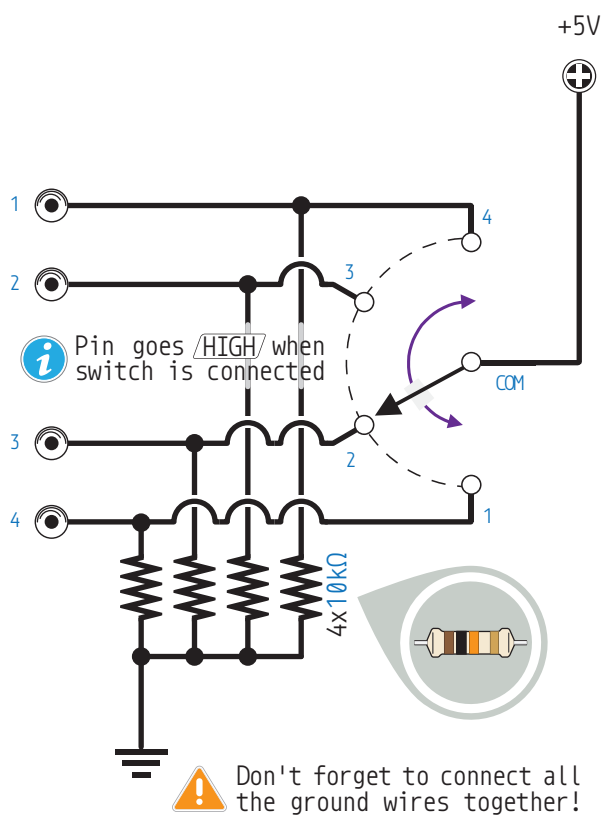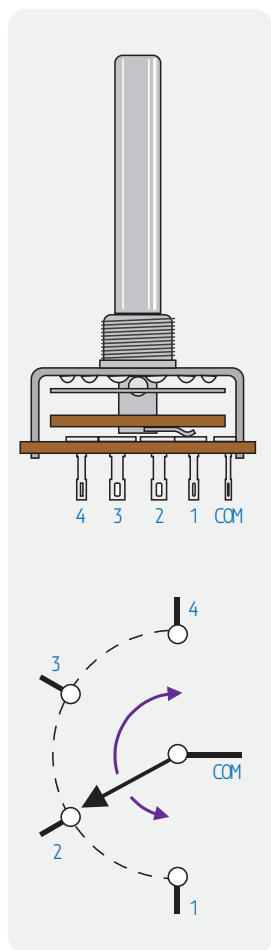

Rotary switches are switches that have fixed angular positions that click in place when the connection is established by rotating the shaft. You could build this circuit using just one analog pin as in the **Multiple Pushbuttons** sheet by replacing the pushbuttons in that circuit with a rotary switch.






0-1.es/57

57

PS/2 Keyboard

Basic Connections

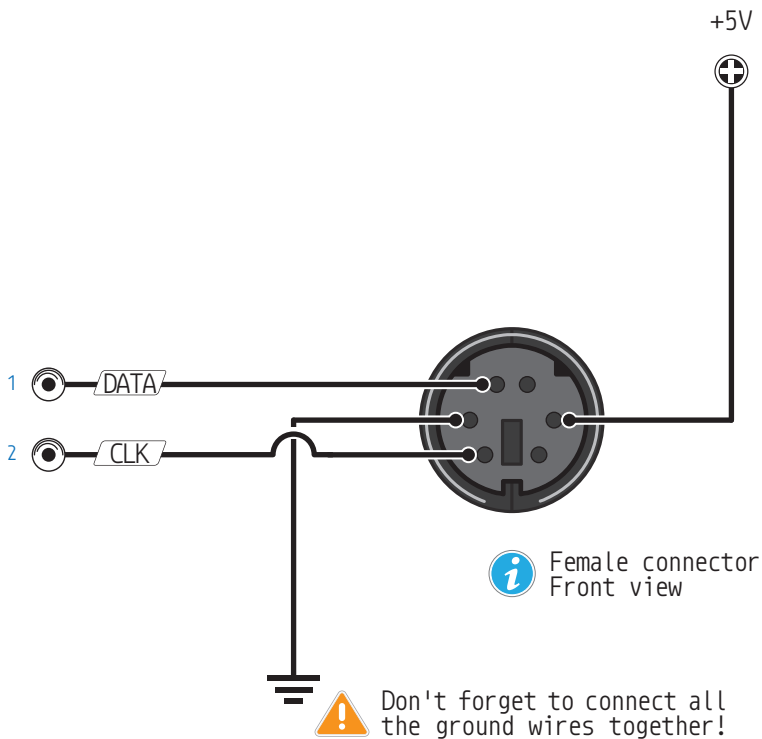

PS/2 is a simple synchronous serial protocol that uses only two wires for communication. Due to its simplicity, PS/2 keyboards are widely used with simple microcontroller boards. PS/2 keyboards can send the equivalent ASCII value of the key that has been pressed.







58

0-1.es/58

Trimmer

Basic Connections

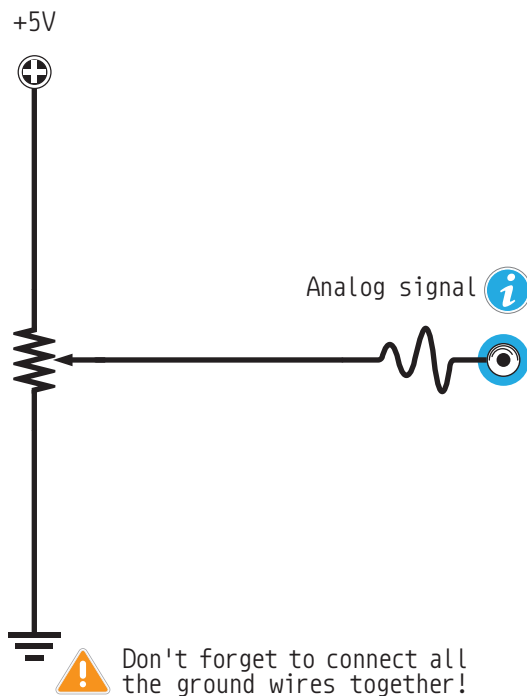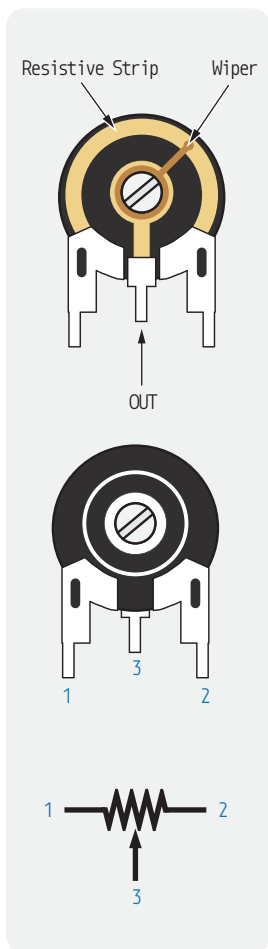

Trimmers are manually-adjustable, variable resistors with three terminals. Two terminals are connected to a resistive element and the third terminal is connected to an adjustable wiper. In this circuit, the position of the wiper determines the output voltage.







0-1.es/59

59

Photoresistor (LDR)

Basic Connections

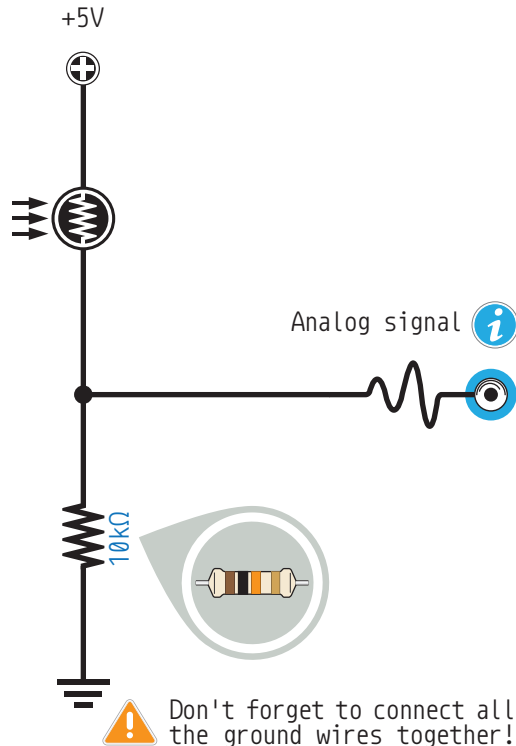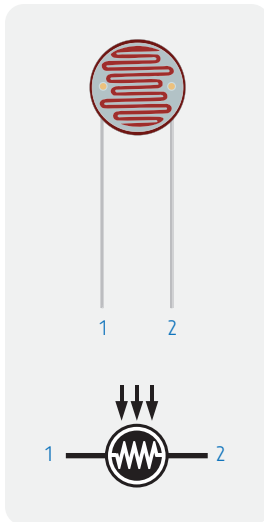

Photoresistors or photocells are light-controlled variable resistors. The resistance of a photoresistor decreases with increasing incident light intensity. Photoresistors can be applied in light-sensitive detector circuits and light-activated switching circuits.






60

0-1.es/60

Phototransistor

Basic Connections

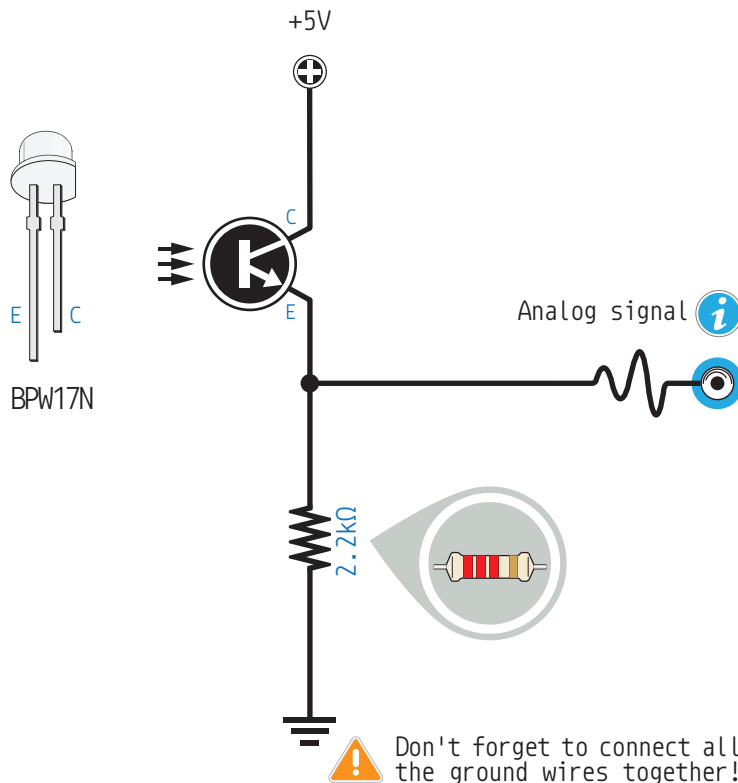

Phototransistors are light-sensitive transistors. Light reaches the the base-collector junction, where electrons are generated, and the current is amplified by the current gain. Phototransistors are faster than photoresistors and slower than photodiodes, but they are less sensitive to temperature.






0-1.es/61

61

Opto-Isolated DC Input

Using the 4N25 Optocoupler

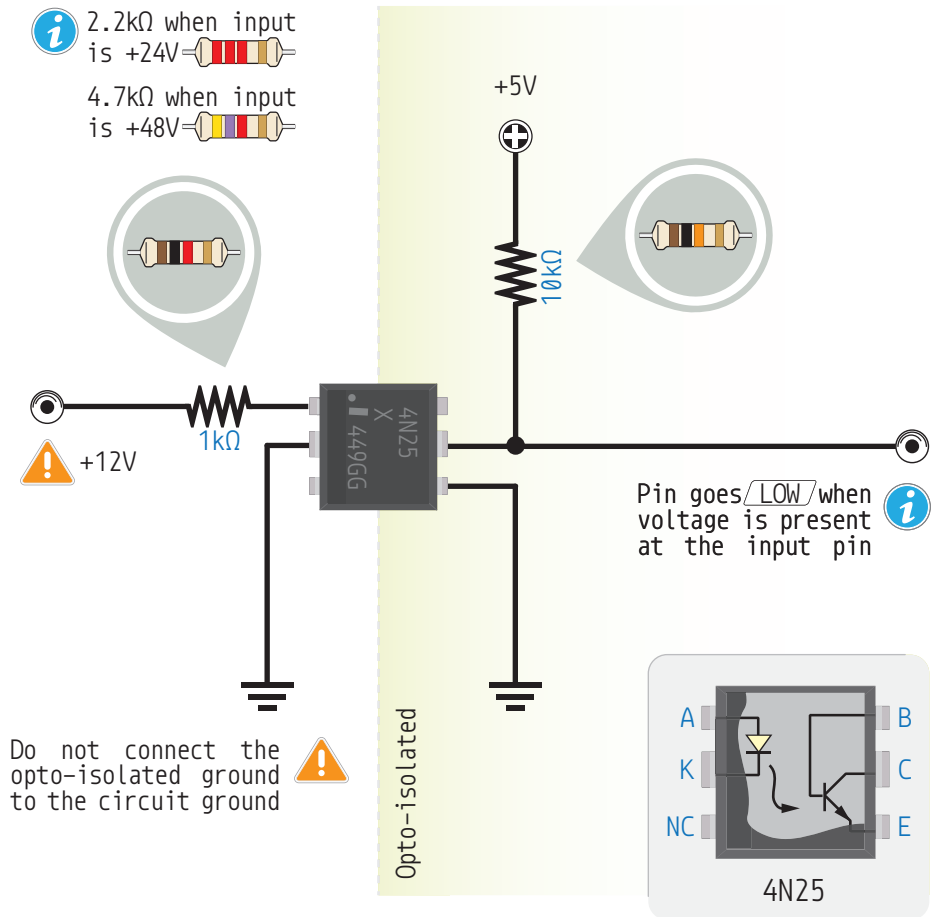




62

0-1.es/62

Opto-Isolated AC Input

Using the 4N25 Optocoupler

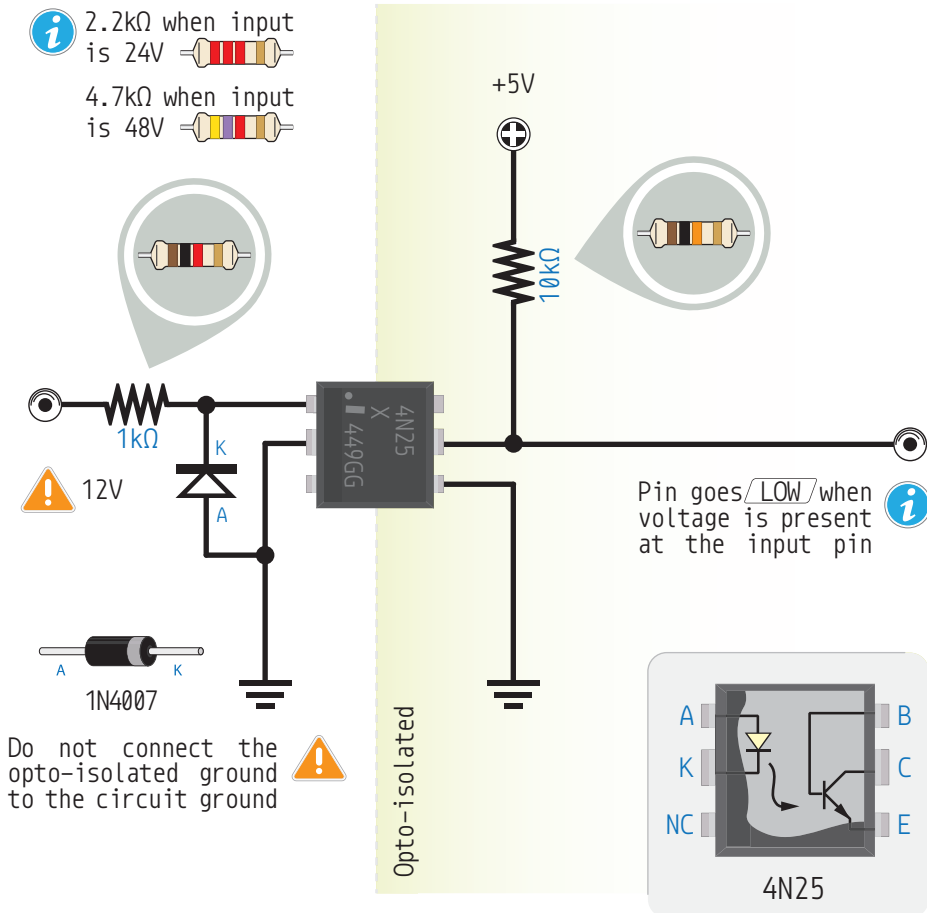




0-1.es/63


63

SPST CMOS Analog Switch

Using the 4066 Quad Bilateral Switch

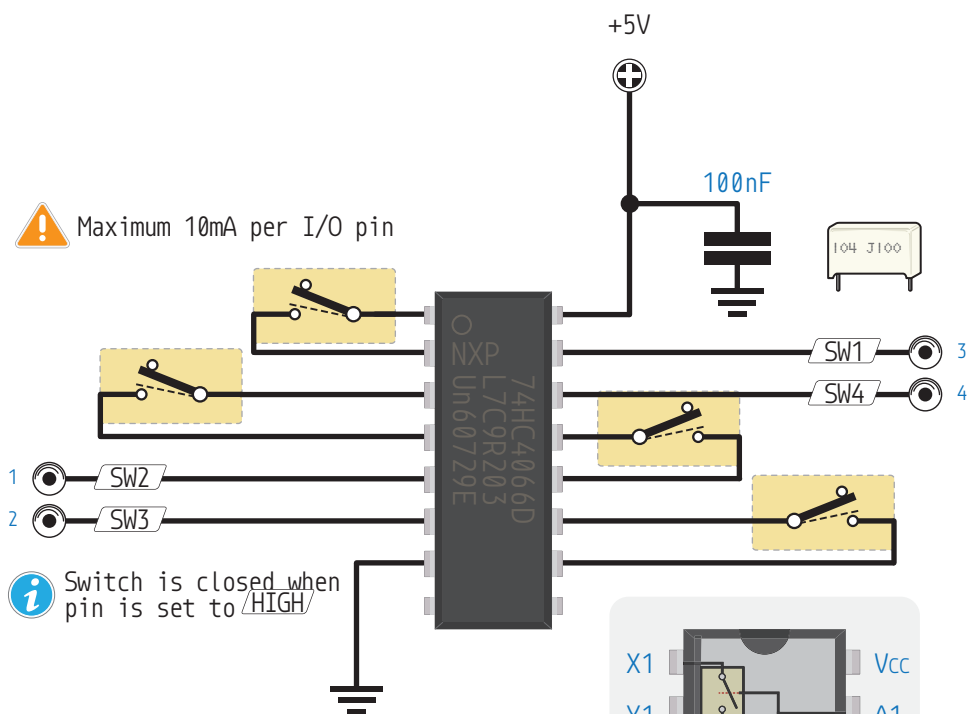

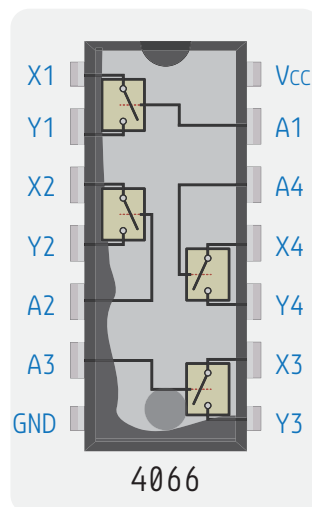Don't forget to connect all the ground wires together! !






64

0-1.es/64

AC Current Sensor

Basic Connections

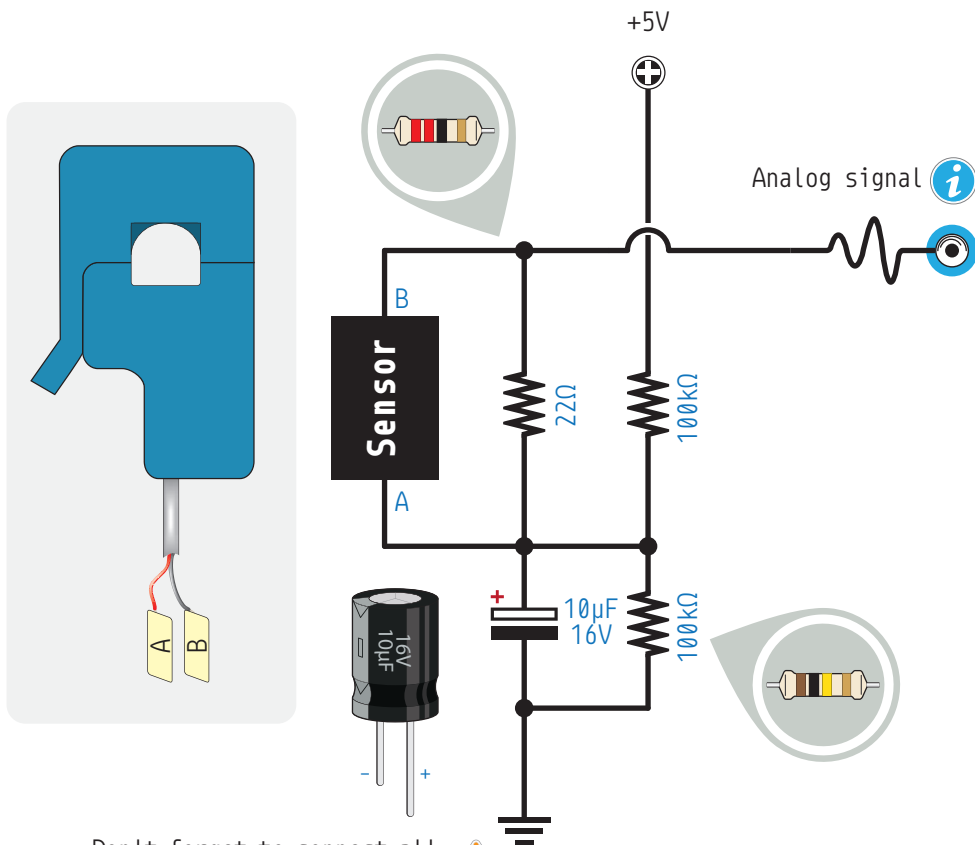

Don't forget to connect all the ground wires together! 



These non-invasive current sensing probes are an affordable solution for measuring high AC current. They are also called CT (current transformer) sensors because they act like current transformers, delivering a fraction of the current measured through magnetic induction.






0-1.es/65

65

LM34/LM35 Temperature Sensor

Basic Connections

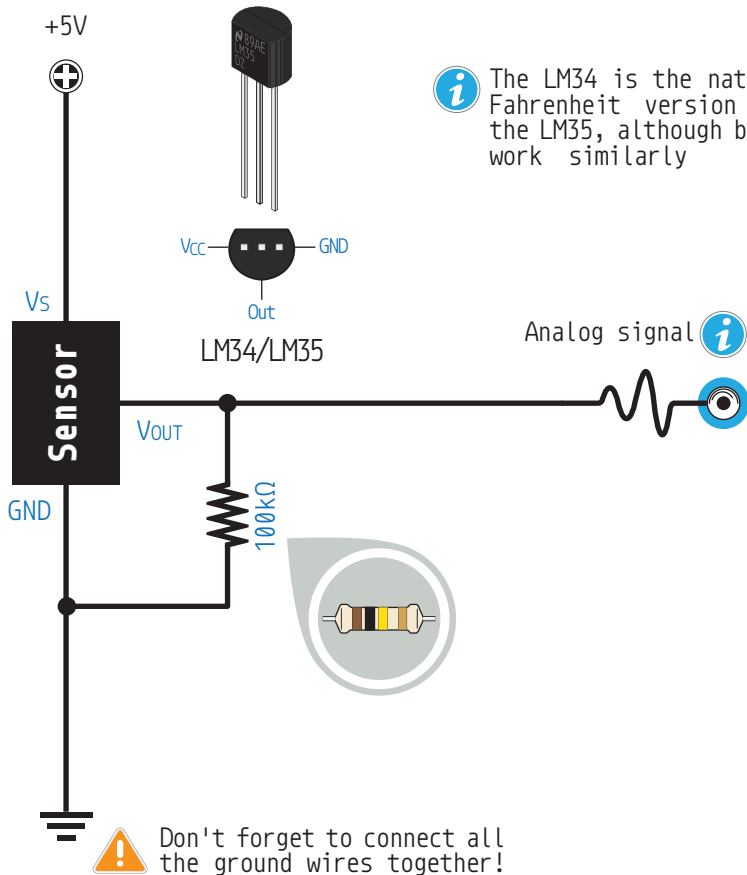

i The LM34 is the native Fahrenheit version of the LM35, although both work similarly



The LM35 is an analog, precision temperature sensor. This circuit allows for a measuring range of 2°C to +150°C (35.6°F to +302°F) with a temperature accuracy of $\pm 0.5^\circ\text{C}$ (0.9°F). The output of the sensor is linear with respect to the measured temperature, increasing its output voltage by 10mV per degree Celsius.






66

0-1.es/66

LM34/LM35 Temperature Sensor

Full Range

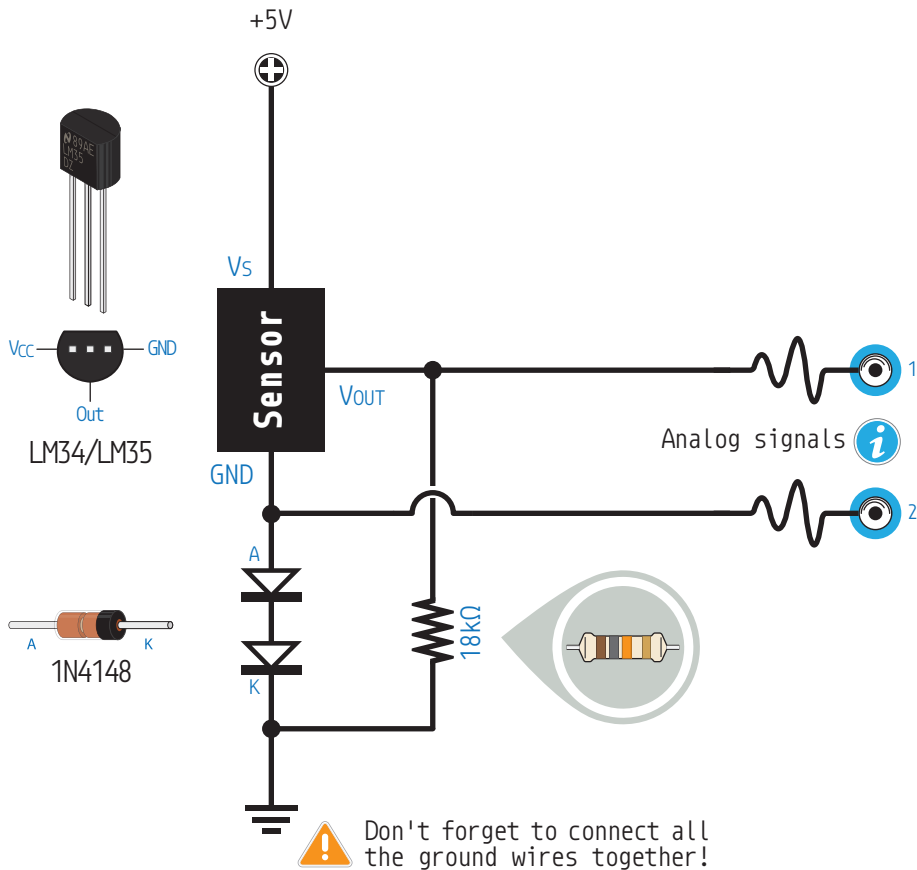

This circuit allows the LM35 to achieve its full potential, allowing for a temperature measuring range of -55°C to $+150^{\circ}\text{C}$ (-67°F to $+302^{\circ}\text{F}$). The voltage is measured between both analog signal outputs, so you need to read the values with your microcontroller and obtain the absolute value of the difference.






0-1.es/67

67

TMP36 Temperature Sensor

Basic Connections

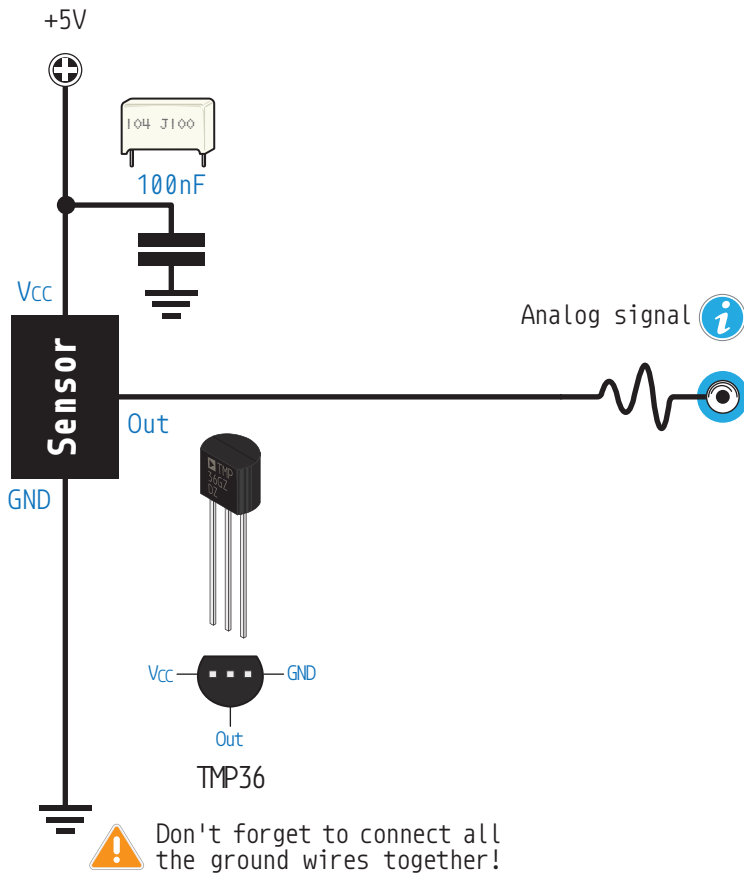

The TMP36 is an analog temperature sensor with a measuring range of -40°C to $+125^{\circ}\text{C}$ (-40°F to $+257^{\circ}\text{F}$). It has a temperature accuracy of $\pm 2^{\circ}\text{C}$ and it is very linear.






68

0-1.es/68

MCP9700 Temperature Sensor

Basic Connections

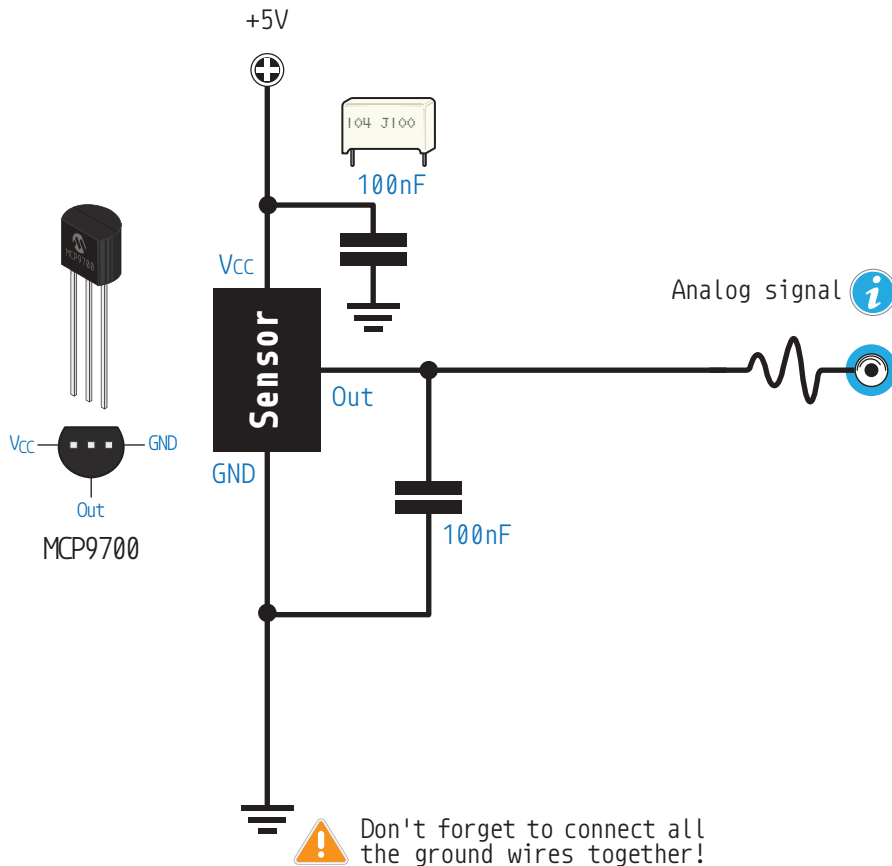

The MCP9700 is an analog temperature sensor with a measuring range of -40°C to $+125^{\circ}\text{C}$ (-40°F to $+257^{\circ}\text{F}$). It has a temperature accuracy of $\pm 2^{\circ}\text{C}$ and it is very linear.






0-1.es/69

69

LM335 Temperature Sensor

Basic Connections

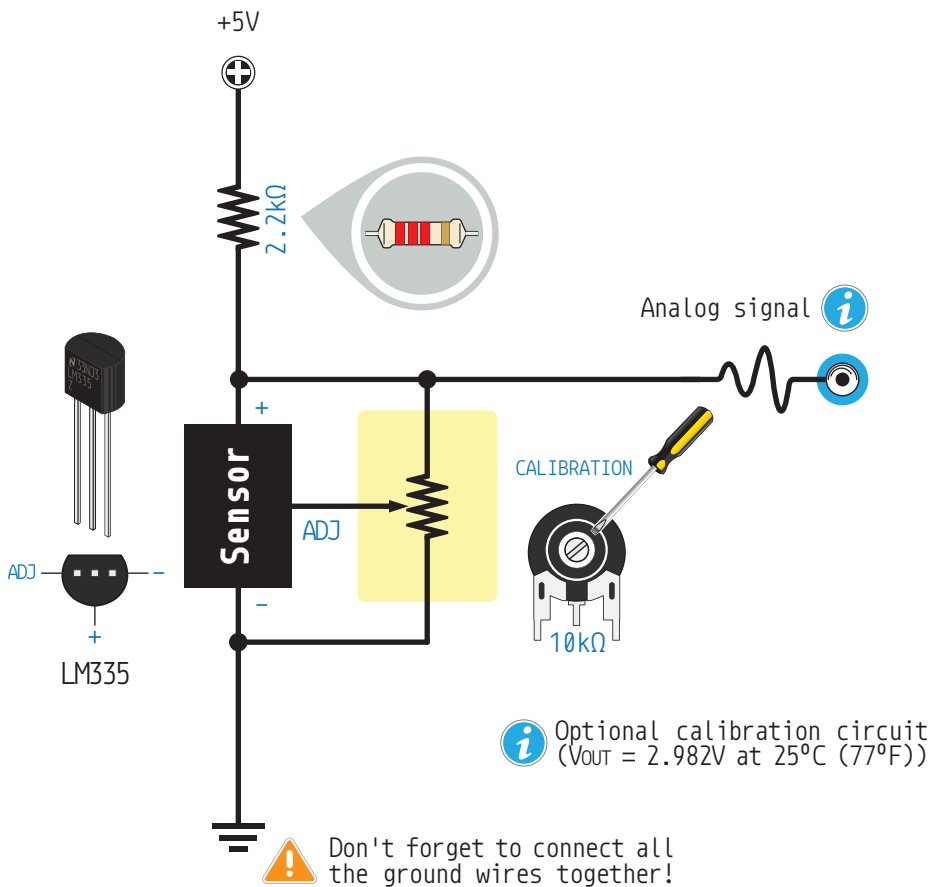

The LM335 is a digital, linear, precision temperature sensor. It has a temperature measuring range of $-55^{\circ}C$ to $+150^{\circ}C$ ($-67^{\circ}F$ to $+302^{\circ}F$) with an accuracy of $1^{\circ}C$ ($1.8^{\circ}F$). The LM335 measures temperature in Kelvin, so you will need to subtract 273 from your measurement to obtain the temperature in Celsius.






70

0-1.es/70

Thermocouple

Using the LM358 Op-Amp

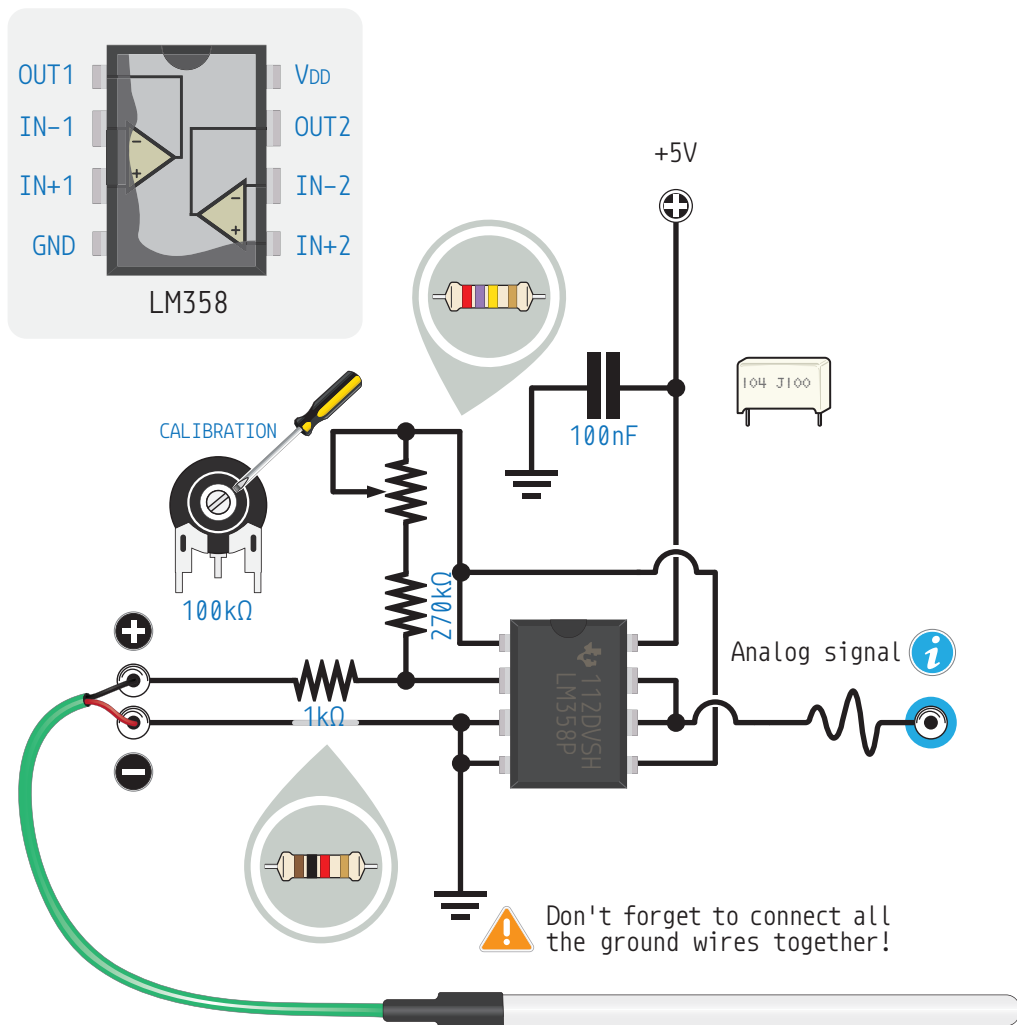

 Check wiring color codes online







0-1.es/71

71

DHT11 Temp. & Humidity Sensor

Basic Connections

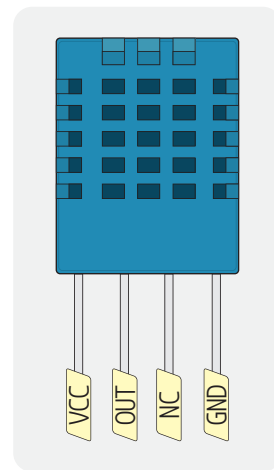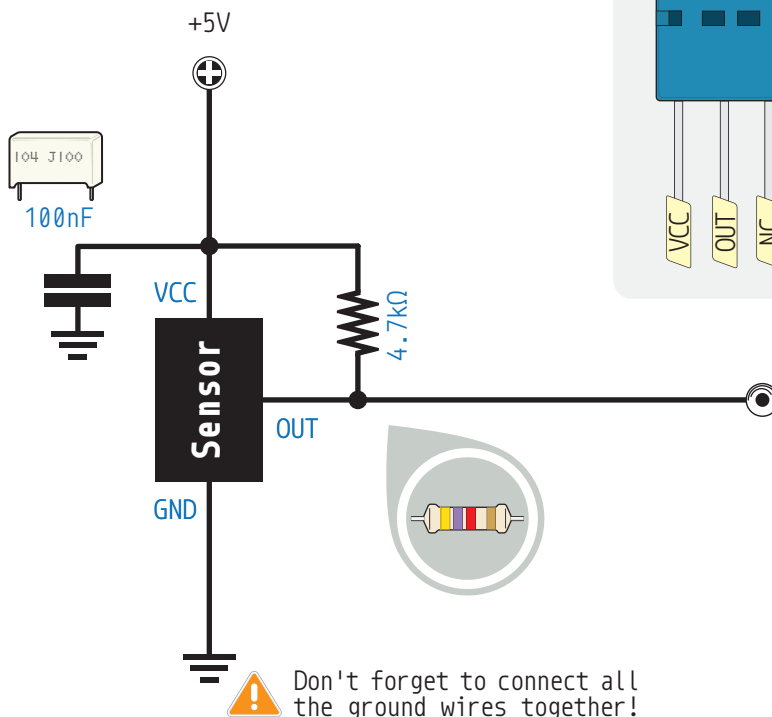

The DHT11 is a digital, low cost, medium precision humidity and temperature sensor. Its measuring ranges are 20 to 90% ($\pm 5\%$) for relative humidity and 0°C to 50°C ($\pm 2^{\circ}\text{C}$) (32°F to 122°F ($\pm 3.6^{\circ}\text{F}$)) for temperature.






72

0-1.es/72

DHT22 Temp. & Humidity Sensor

Basic Connections

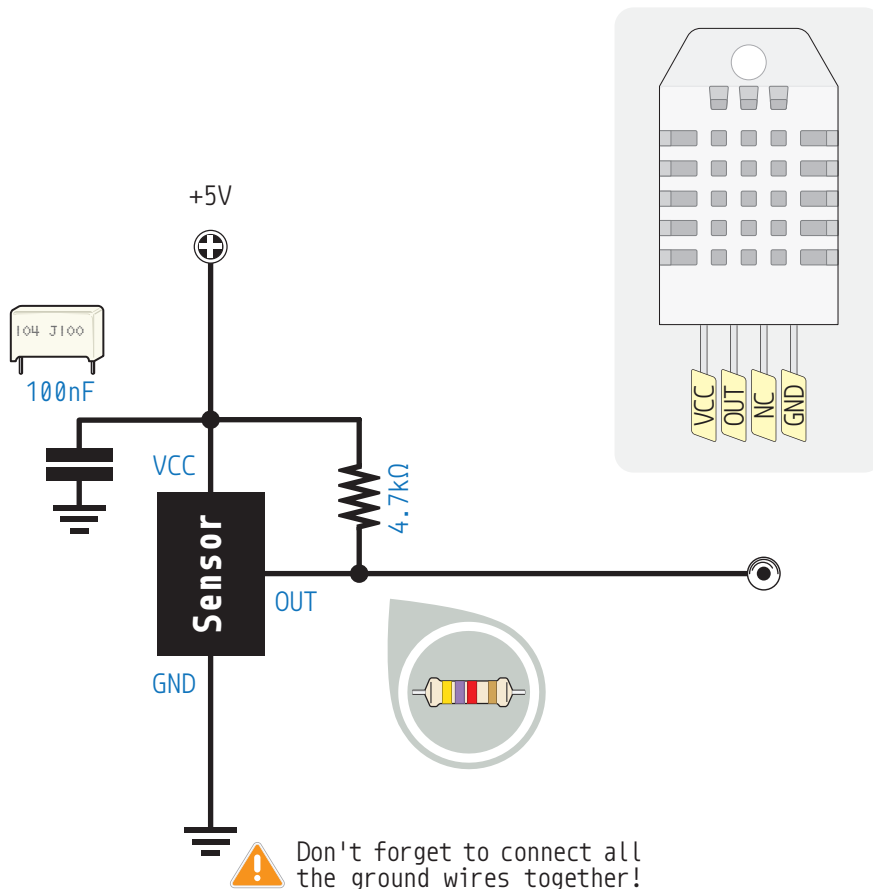

The DHT22 (also called AM2302) is a digital temperature and humidity sensor very similar to the DHT11, except it offers higher-precision readings. Its measuring ranges are 0 to 90% ($\pm 2\%$) for relative humidity and -40°C to 80°C ($\pm 0.5^{\circ}\text{C}$) (-40°F to 176°F) ($\pm 0.9^{\circ}\text{F}$) for temperature.






0-1.es/73

73

DHT11/DHT22 2-Wire Connection

Basic Connections

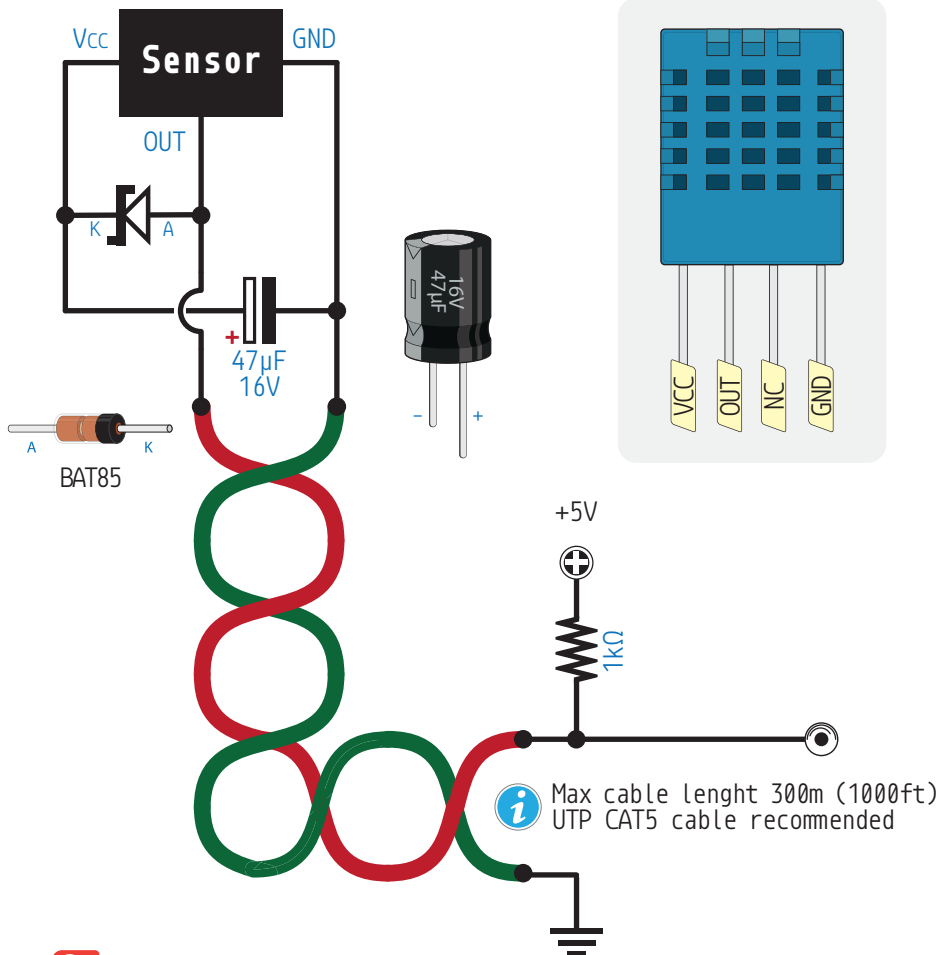

This 2-wire connection circuit allows for reliable measurements over long distances. Twisted pair cables like UTP CAT5, used in computer networks such as Ethernet, are affordable and ubiquitous.





74

0-1.es/74

DS18B20 Temperature Sensor

Basic Connections



Max cable length 40m (130ft)
UTP CAT5 cable recommended





100nF

+5V



4.7kΩ

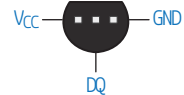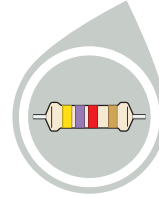

DS18B20

Don't forget to connect all the ground wires together!



The DS18B20 is a digital, precision temperature sensor with a measuring range of -55°C to $+150^{\circ}\text{C}$ ($\pm 0.5^{\circ}\text{C}$) (-67°F to $+257^{\circ}\text{F}$ ($\pm 0.9^{\circ}\text{F}$)). Its 1-wire interface requires only one port pin for communication, providing the temperature value with just a few lines of code and allowing multiple sensors to run in parallel.






0-1.es/75

75

NTC Thermistor

Basic Connections

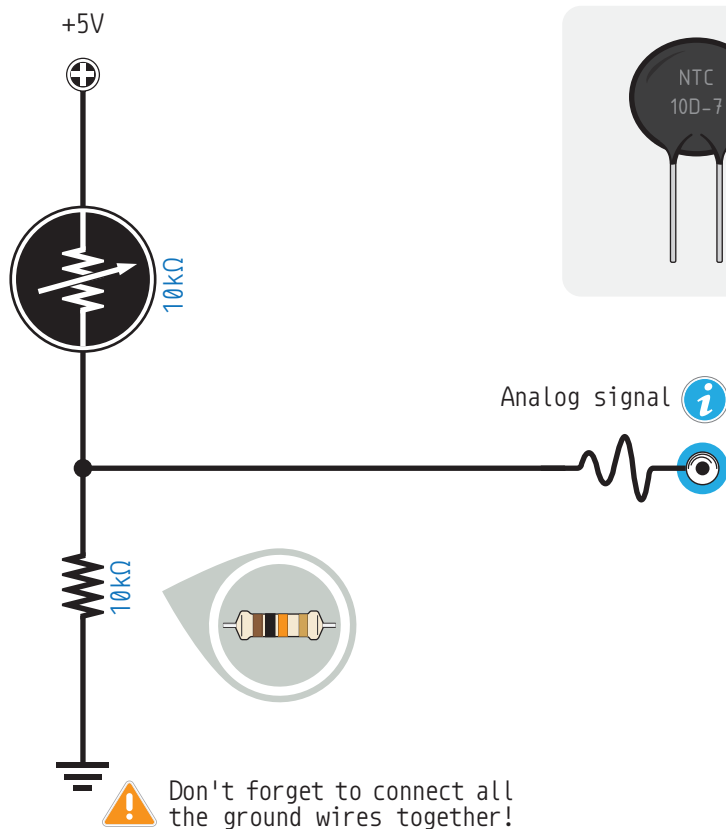


Thermistors (thermally-sensitive resistors) are a type of resistor whose resistance is dependent on temperature. Their temperature range is typically -55°C to 200°C (-67°F to 392°F). Thermistors are affordable, sensitive but not very linear.





RTD Temperature Sensor

Using a PT1000 Sensor

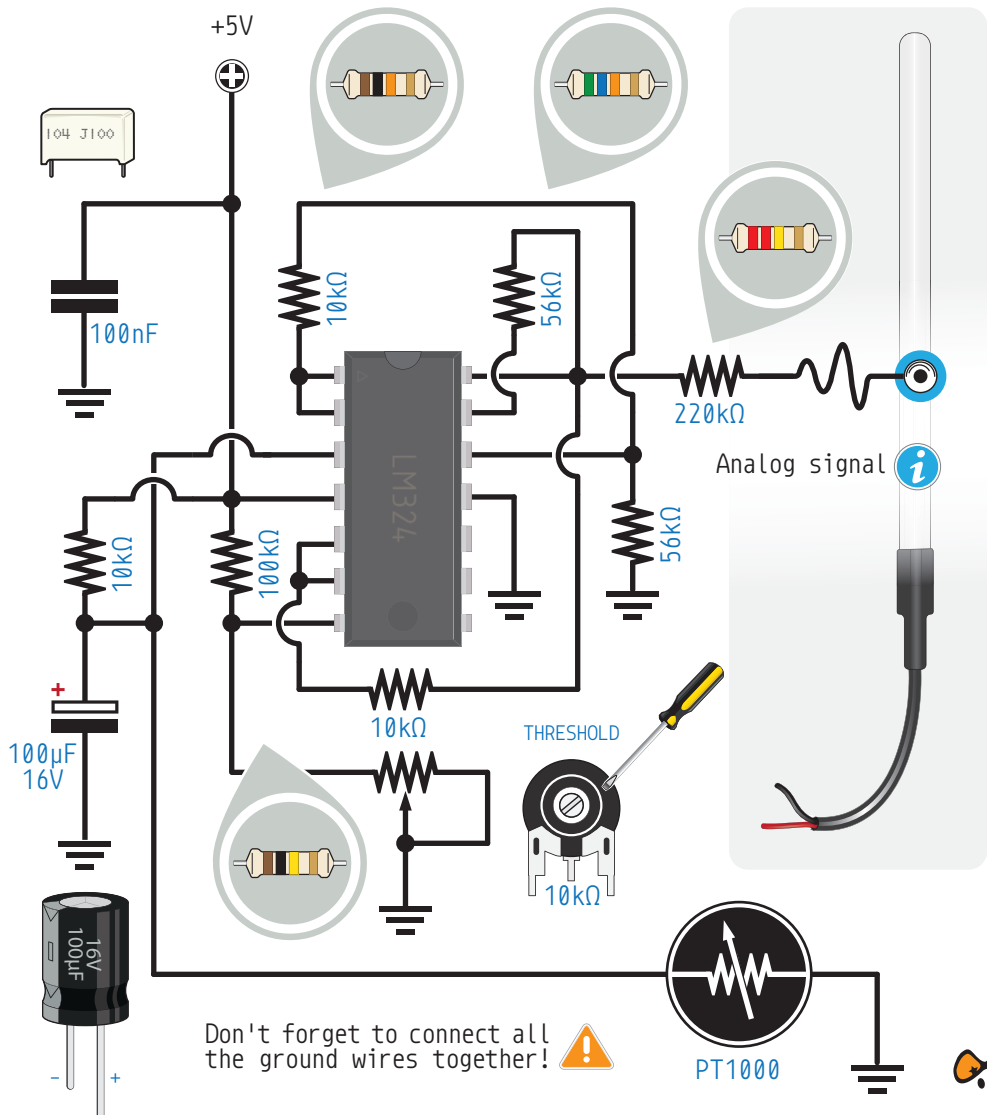




0-1.es/77

77

Gas Sensor

Using an MQ Series Sensor

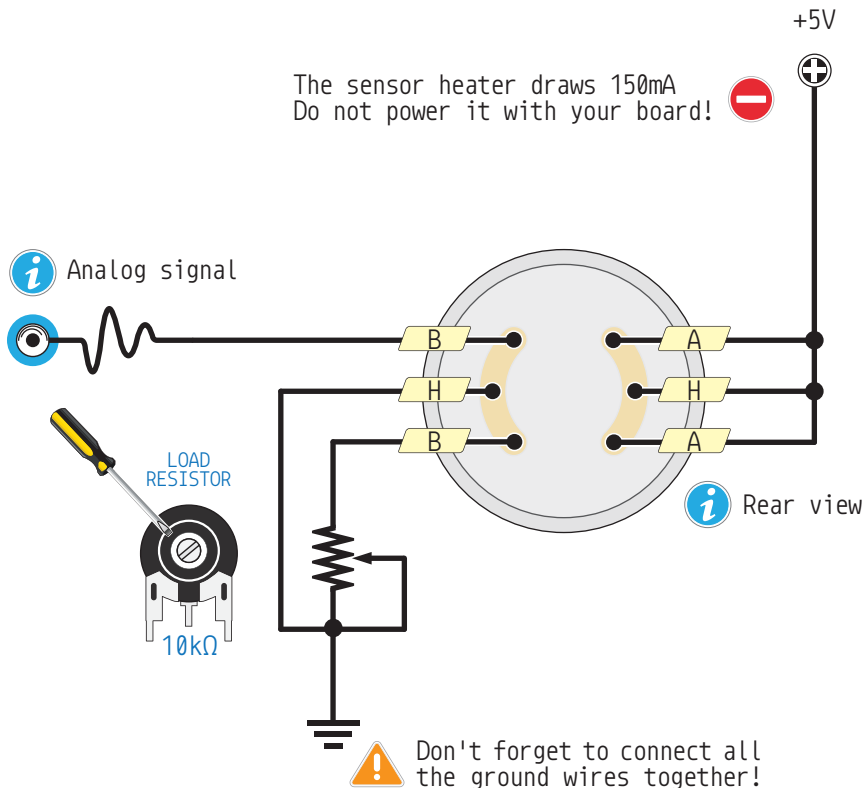

The MQ series of gas sensors use a small heater inside with an electro-chemical sensor. They are sensitive for a range of gasses at room temperature such as methane, butane, propane, natural gas, LPG, smoke, alcohol, ethanol, ozone, hydrogen, benzene, hydrogen sulfide, toluene, acetone, CO₂, CO, etc.






78

0-1.es/78

Sharp GP2Y0A21 Distance Sensor

Basic Connections

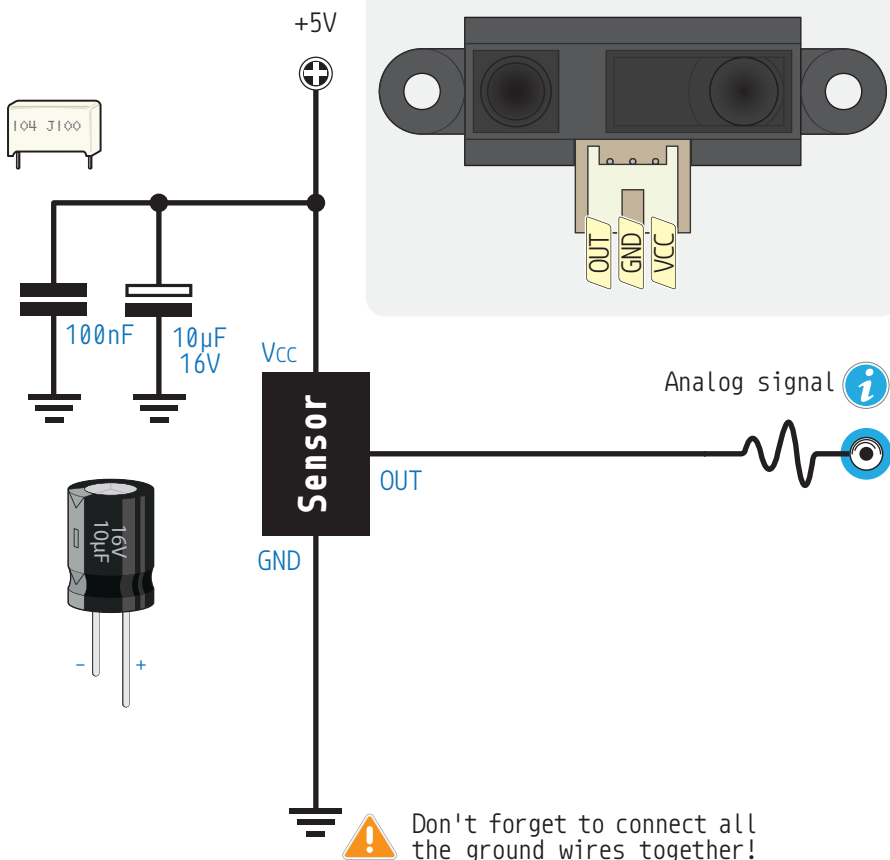

The Sharp GP2Y0A21 distance sensor is a popular choice for many projects that require accurate distance measurements, it has a measuring range of 10 to 80cm (4 to 32in). The relationship between the output voltage and the inverse of the measured distance is nonlinear and needs to be linearized in the code.





Basic Connections



microSD to SD card adapters come bundled with many microSD cards nowadays. You can build this circuit to convert that adapter into a microSD card reader for your microcontroller board.



79

0-1.es/79

SD Card Pinout






0-1.es/80

80

SD Card

Using the 4050 Buffer

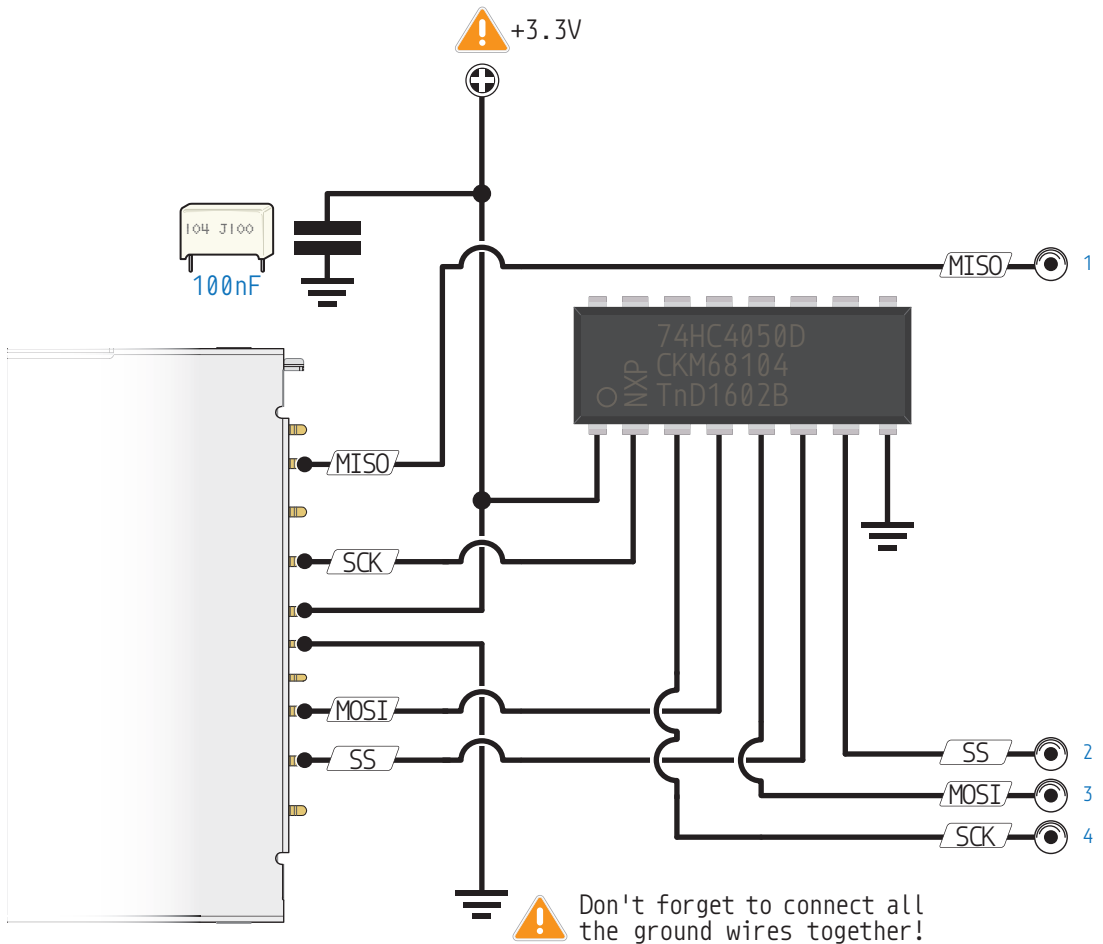

If you want to have a more professional, reliable and faster SD card reader you can opt for building this circuit using the 4050 buffer/converter instead of the DIY SD card reader circuit.






80

0-1.es/80

SD Card Socket

Pinout

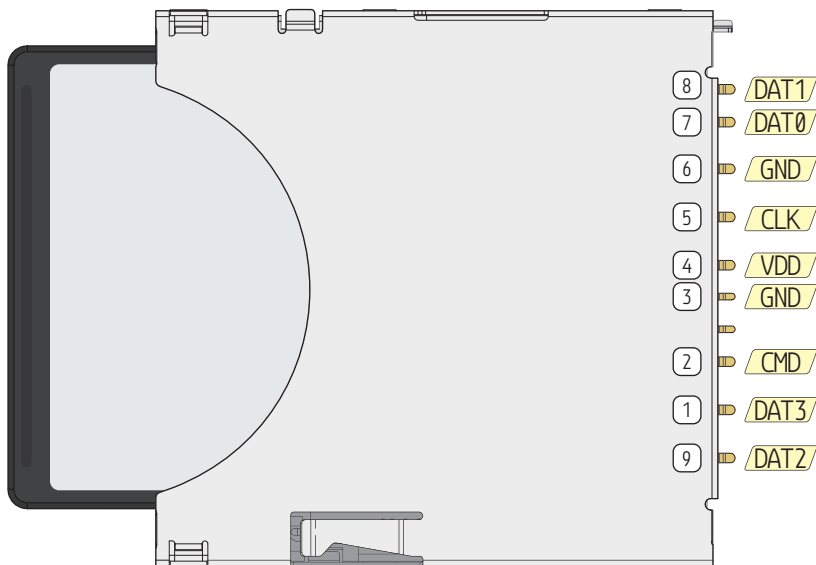

 Top view






0-1.es/81

81

3-Wire Computer Fan

Basic Connections

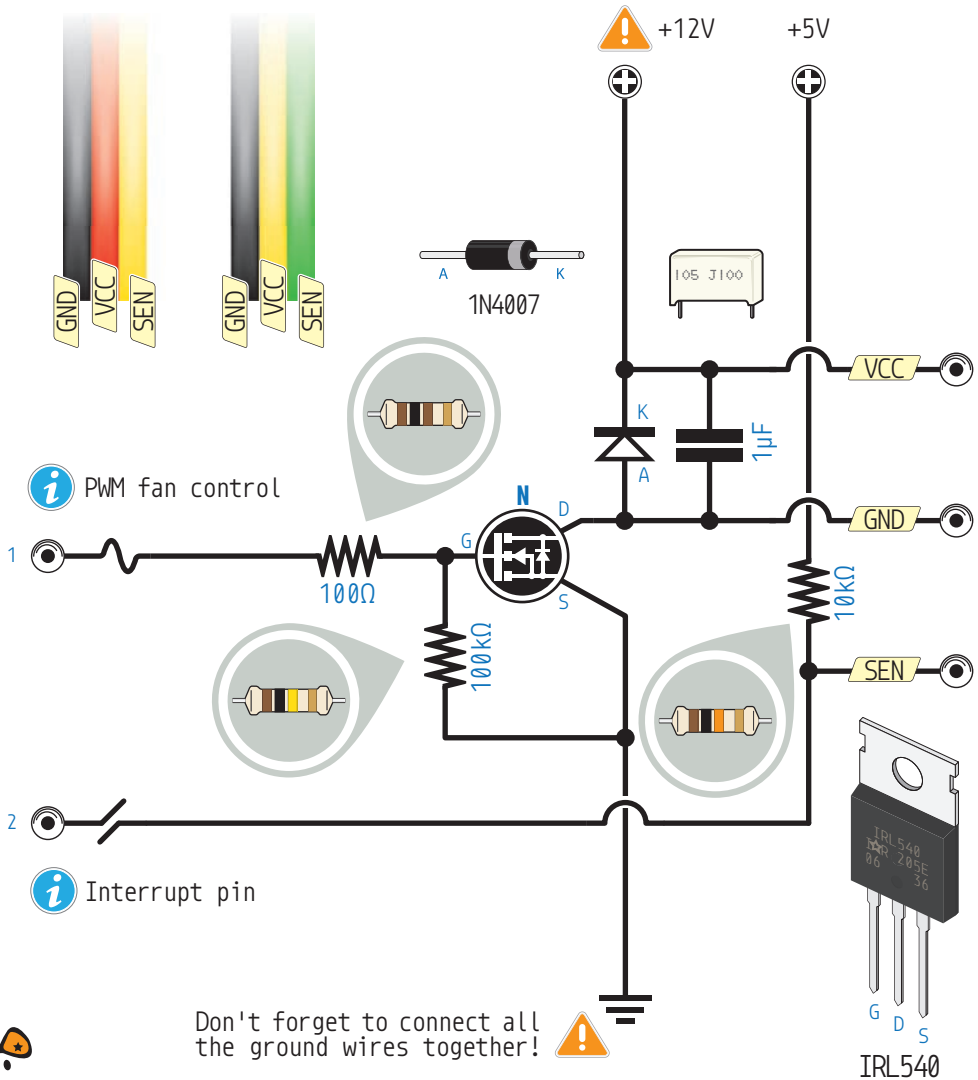




82

0-1.es/82

4-Wire Computer Fan

Basic Connections

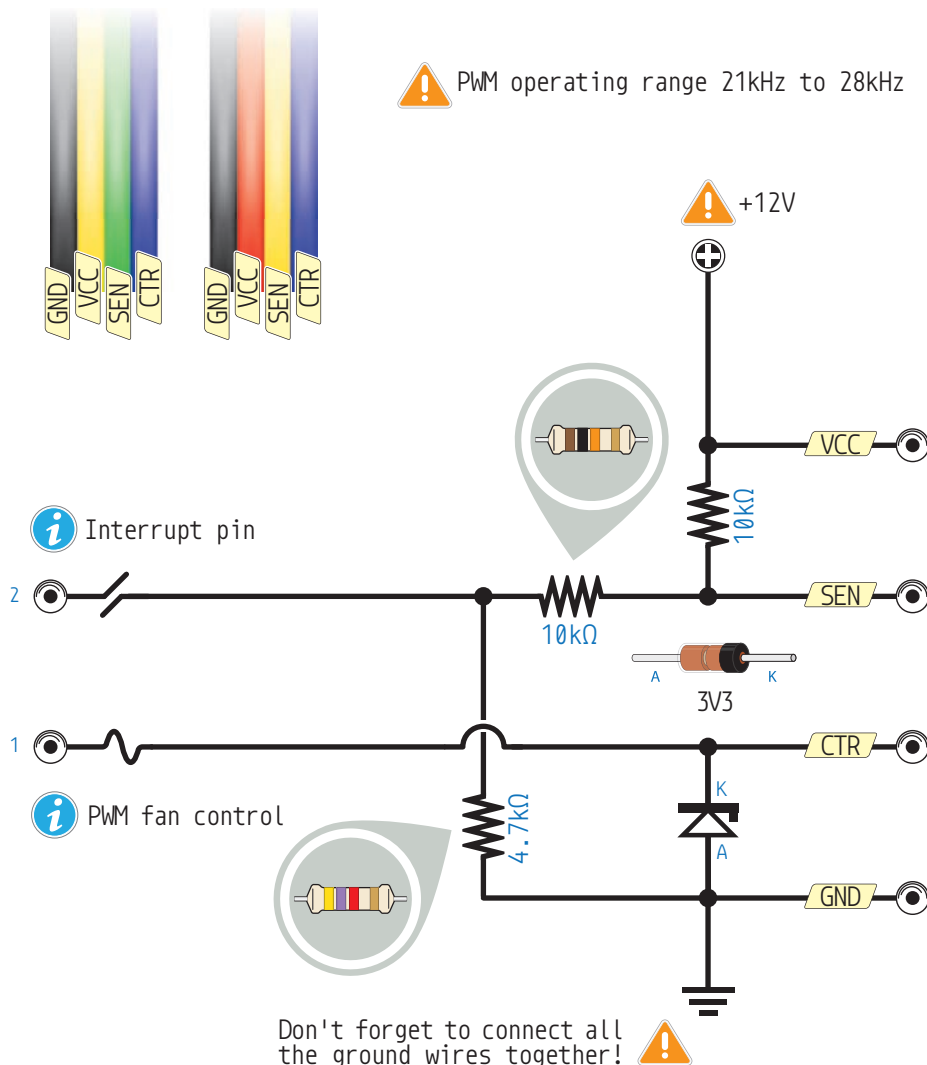




0-1.es/83

83

Bi-Directional Level Converter

Basic Connections

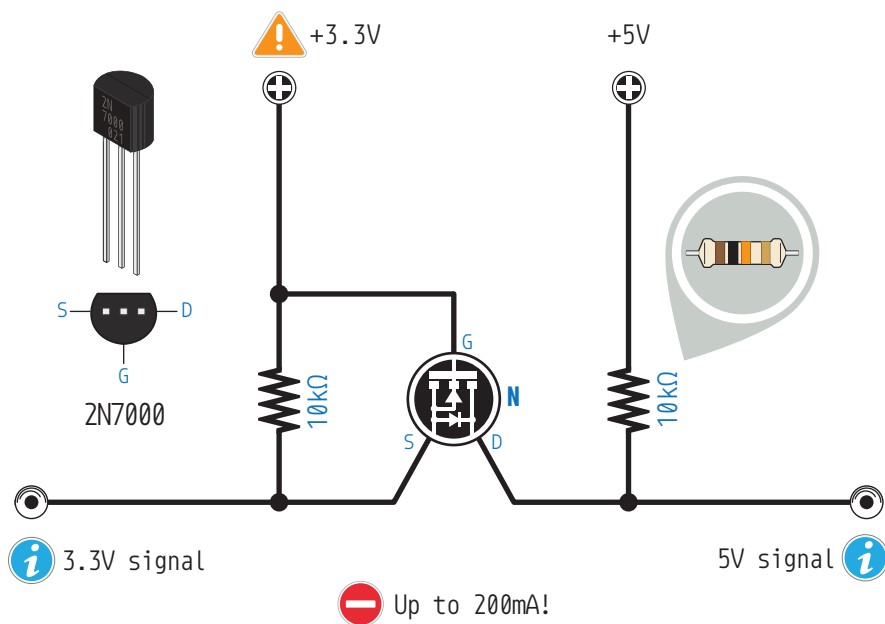

Don't forget to connect all the ground wires together! ⚠



Bi-directional logic level converters allow you to connect devices that use 3.3V logic level signals to microcontroller boards that use 5V, and vice versa. You can use both 3.3V and 5V supply voltages for this circuit or use only the 5V supply and a voltage divider to obtain 3.3V.






83

0-1.es/83

Bi-Directional Level Converter

Voltage Divider Connections

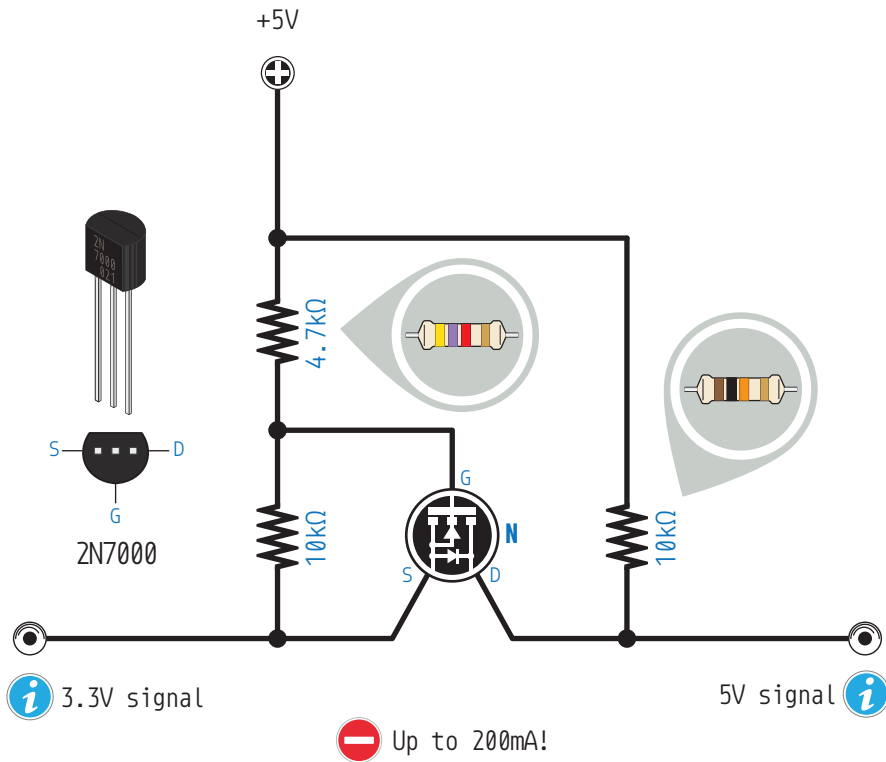

Don't forget to connect all the ground wires together!






0-1.es/84

84

3.3V to 5V Level Shifter

Basic Connections

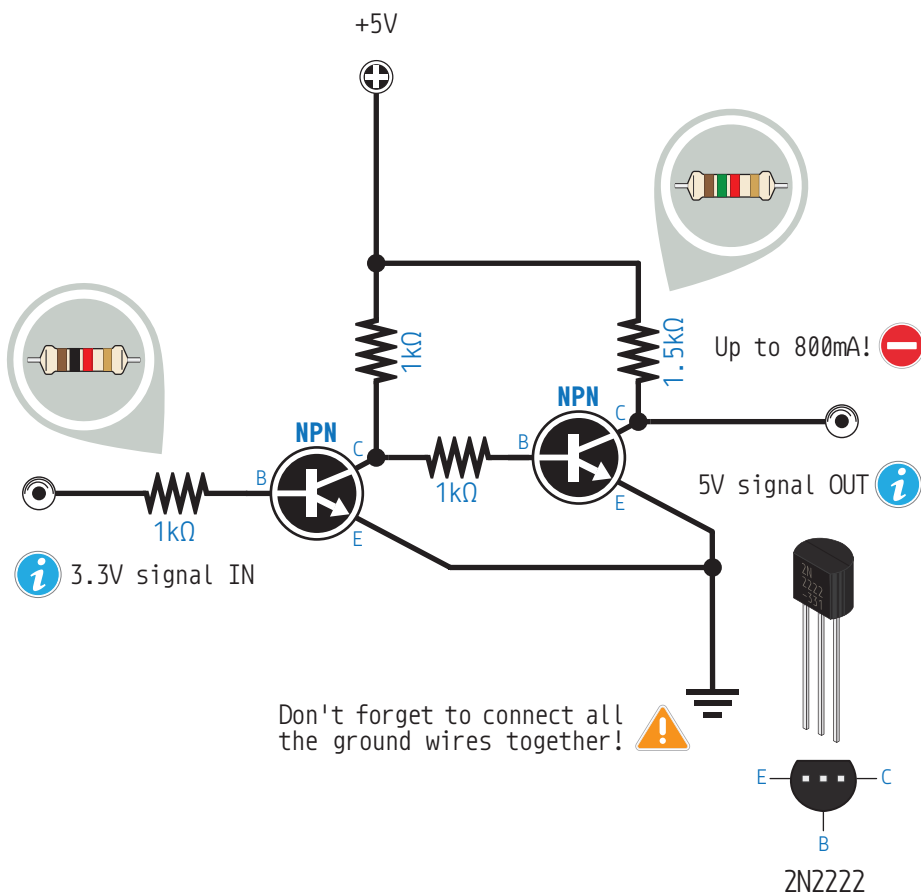

Logic level shifters allow you to connect devices that use 3.3V logic level signals to microcontroller boards that use 5V, or vice versa, depending on the circuit you build. Logic level shifters only allow for the signal to go from one particular logic level to another. Select the circuit according to your needs.






84

0-1.es/84

5V to 3.3V Level Shifter

Basic Connections

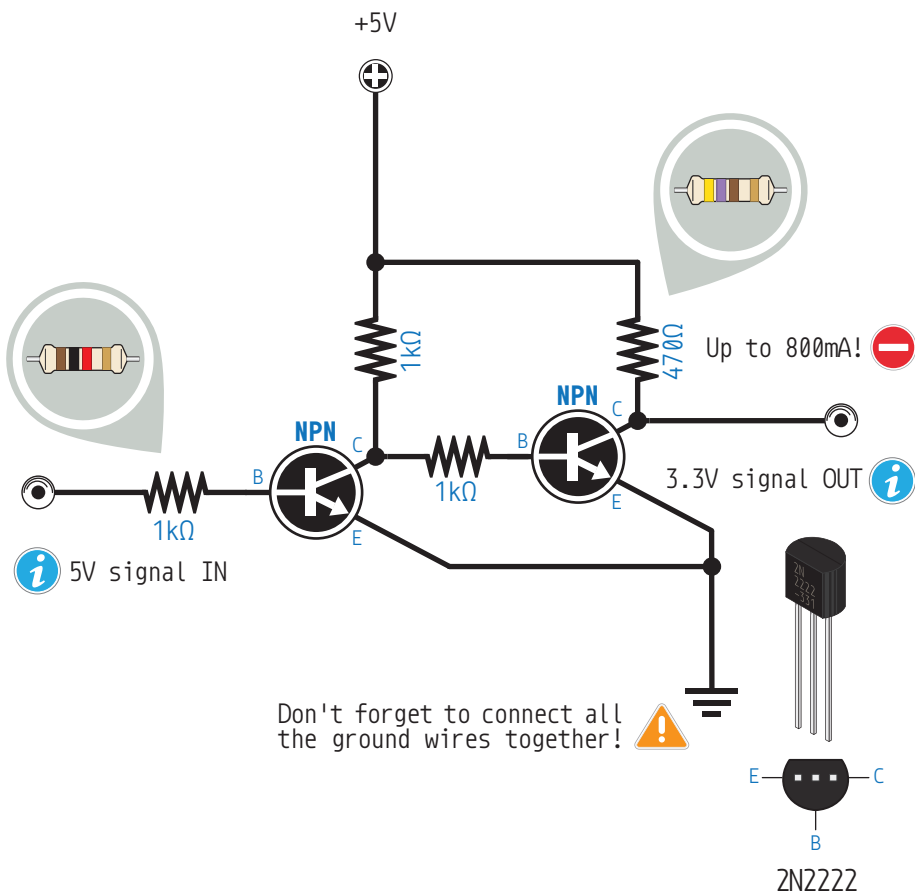




0-1.es/85

85

4050 Level Shifter


Pinout

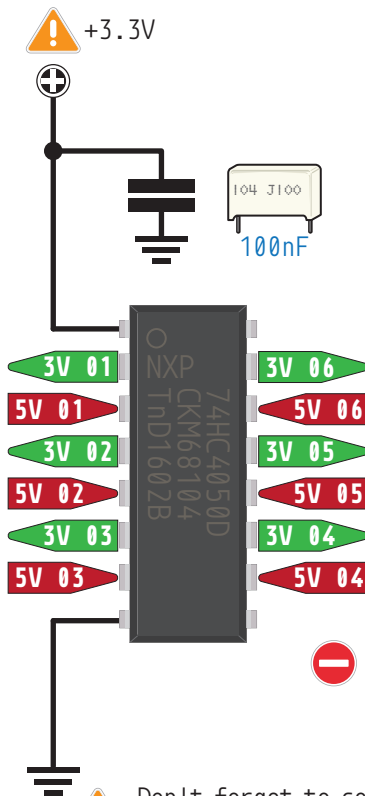

Up to 20mA per I/O pin!



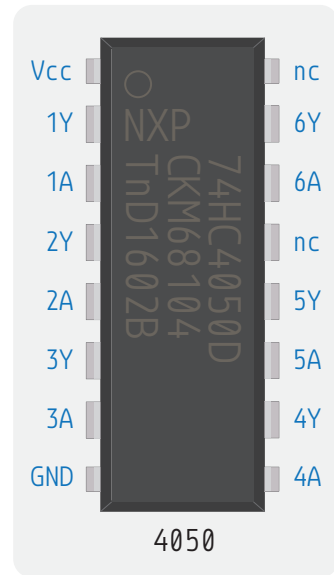Don't forget to connect all the ground wires together!



The 4050 is a hex buffer with over-voltage tolerant inputs. Inputs are over-voltage tolerant to up to 15V, which enables the device to be used in HIGH-to-LOW level shifting applications. The "hex" part means there's actually six separate buffers in one chip.







86

0-1.es/86

74125 Level Shifter

Pinout

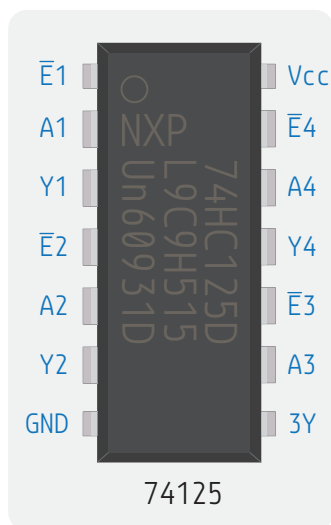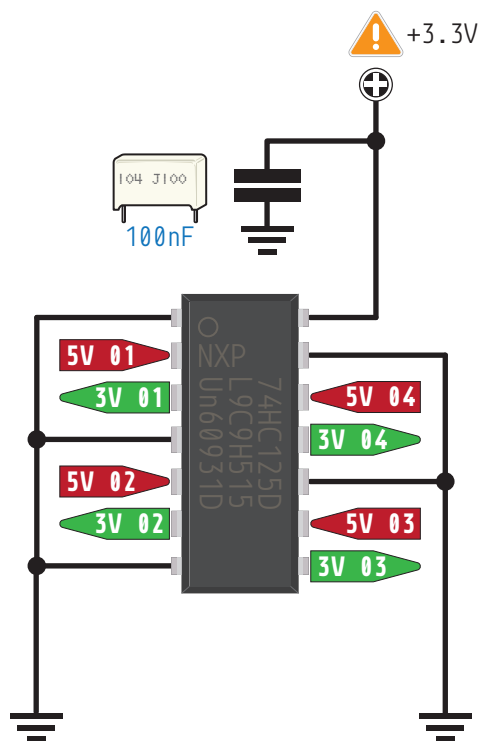

Up to 35mA per I/O pin!

Don't forget to connect all the ground wires together!



The 74125 is a quad buffer/line driver with 3-state outputs controlled by the output enable inputs (E). A HIGH on E pin causes the outputs to assume a high-impedance OFF state. The “quad” part means there’s actually four separate buffer-/line driver in one chip.






0-1.es/87

87

Voltage Divider

Theory

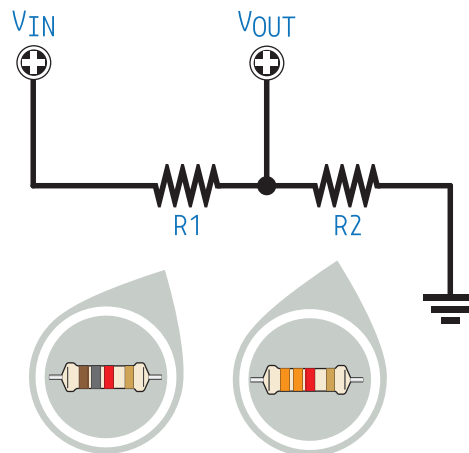

FORMULA

$$V_{OUT} = V_{IN} \times R2 / (R1 + R2)$$
$$V_{OUT} = 5V \times 3.3k\Omega / (1.8k\Omega + 3.3k\Omega)$$
$$V_{OUT} = 3.2V$$



A voltage divider is a simple circuit that produces an output voltage that is a fraction of its input voltage by using just two series resistors. Voltage dividers are one of the most fundamental circuits in electronics.






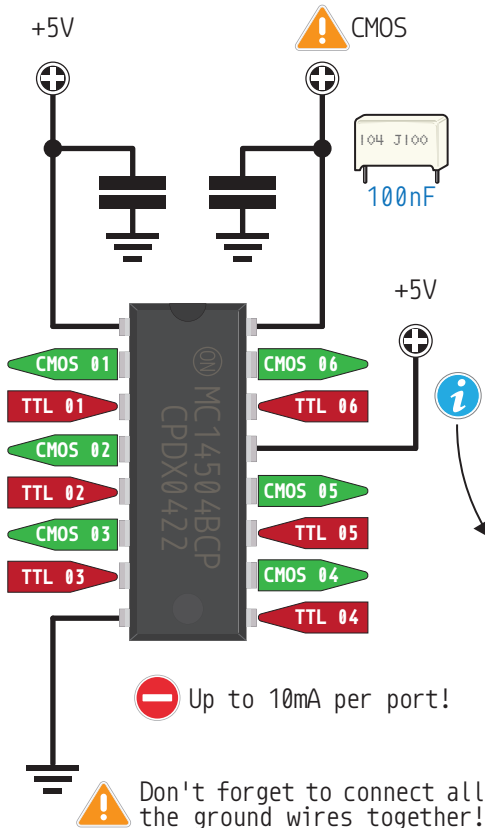
88

0-1.es/88


TTL-CMOS Level Shifter

Using the MC14504

 3V to 18V operation for V_{DD} and V_{CC}



 Up to 10mA per port!

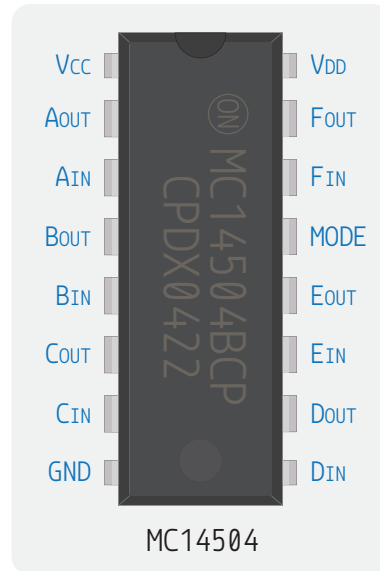

Mode select	Input logic levels	Output logic levels
1 (V _{CC})	TTL	CMOS
2 (V _{DD})	CMOS	CMOS



The MC14504x is a hex non-inverting level shifter using CMOS technology. The level shifter will shift a TTL signal to CMOS logic levels for any CMOS supply voltage between 5 and 15 volts. A control input also allows interface from CMOS to CMOS at one logic level to another logic level.






0-1.es/89


89

I/O Pin Protection

Using a Zener Diode

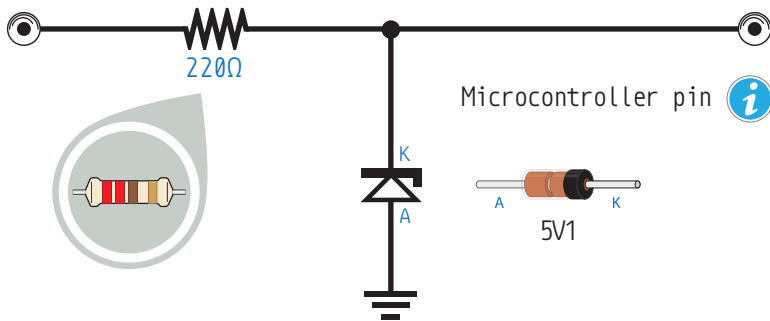

Using Clamping Diodes

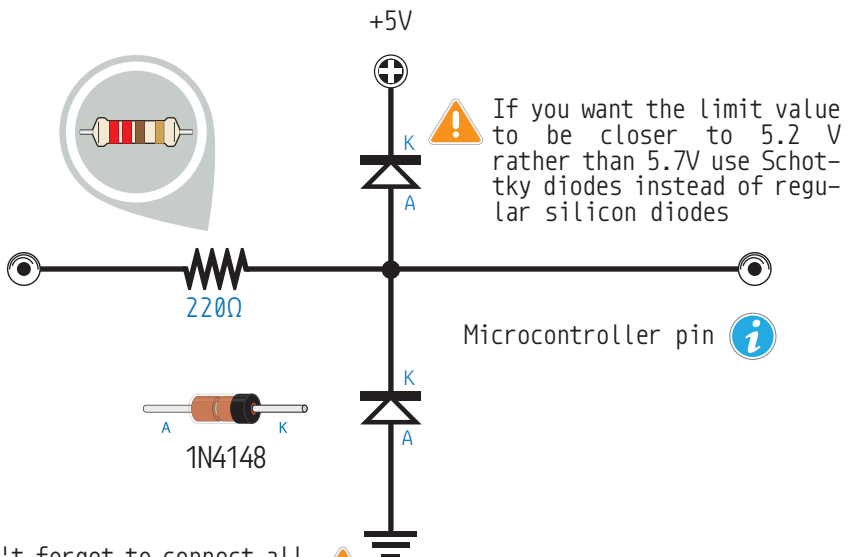

Don't forget to connect all the ground wires together!






90

0-1.es/90


I/O Pin Filtering & Protection

Basic Connections

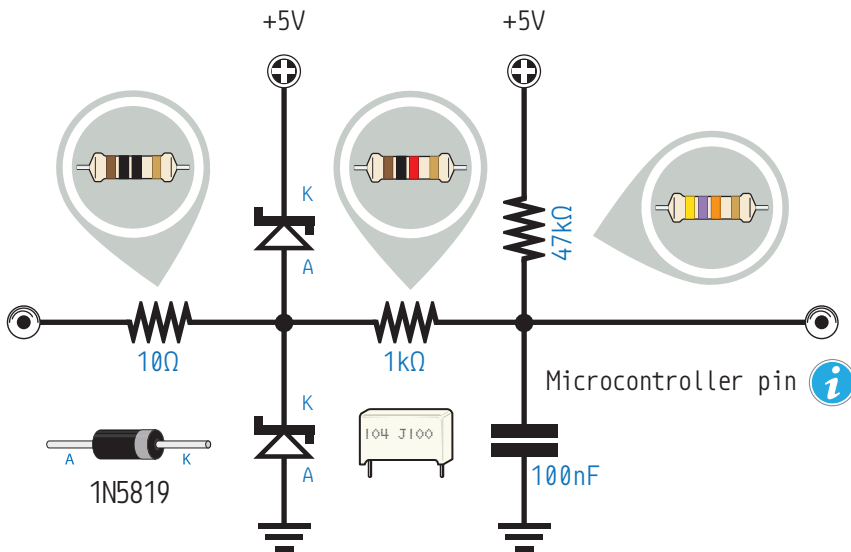

Two Microcontroller Boards

Basic Connections

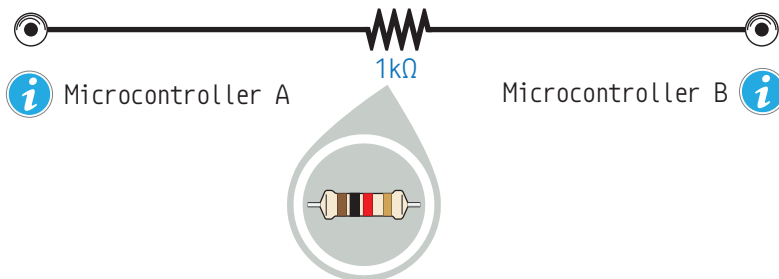

Don't forget to connect all the ground wires together!







0-1.es/91


91

VGA Output

Basic Connections

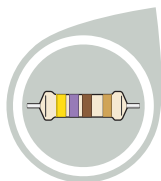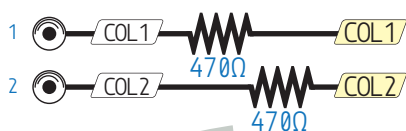

COL1/R	COL2/G	00	01	10	11
COL1/R	COL2/B	00	01	10	11
COL1/G	COL2/B	00	01	10	11
COL1/R	COL2/G/B	00	01	10	11
COL1/R/G	COL2/B	00	01	10	11
COL1/R/B	COL2/G	00	01	10	11

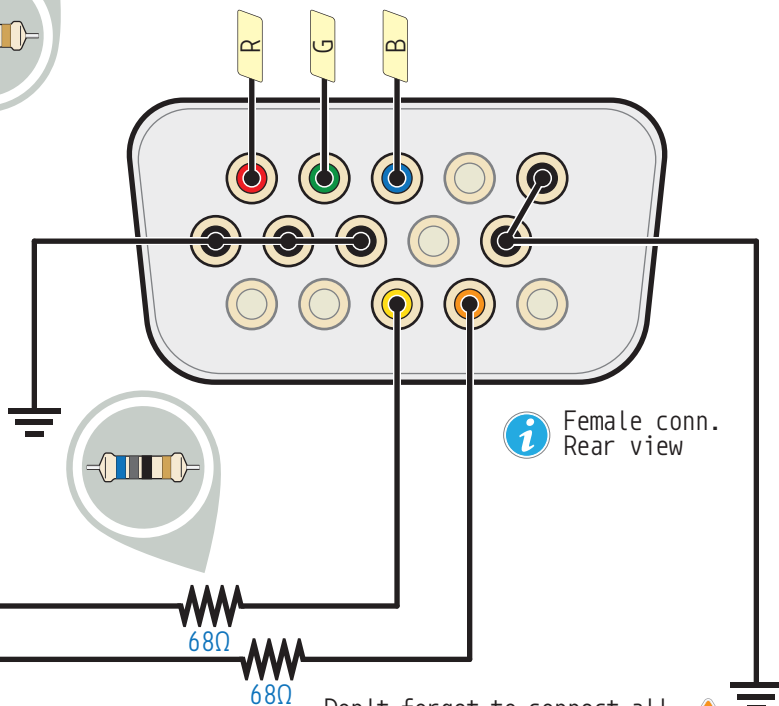

Don't forget to connect all the ground wires together!






92


0-1.es/92

Composite Output

Basic Connections

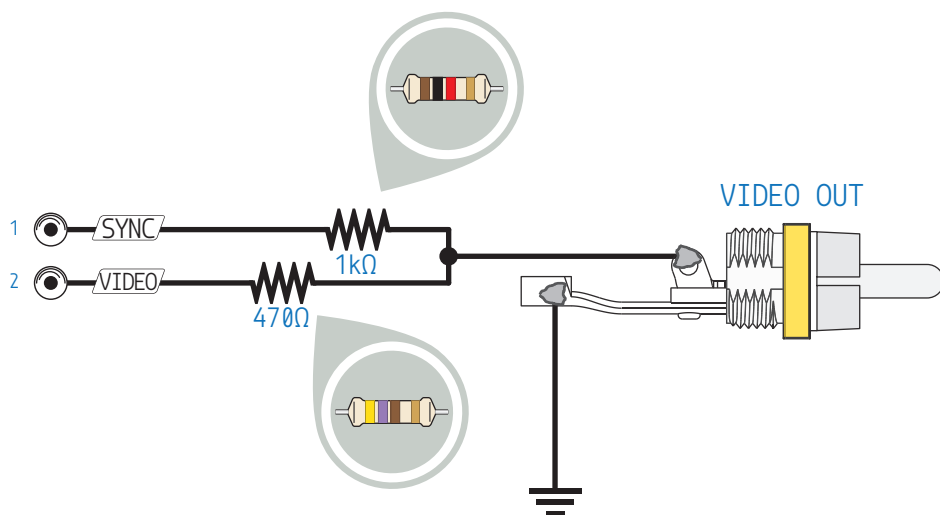

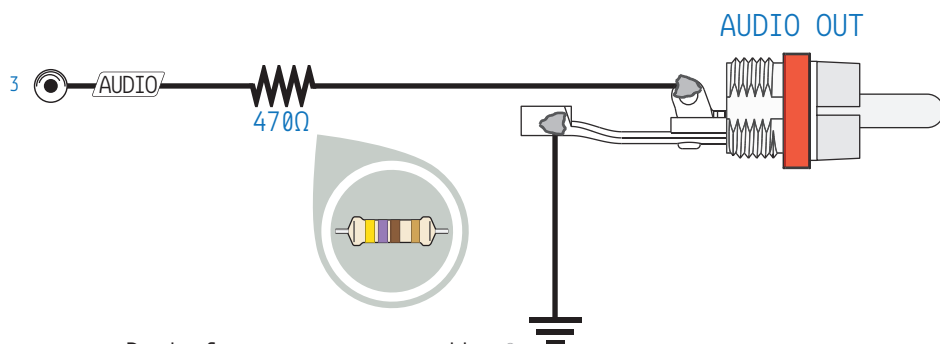75 Ω resistor required between VIDEO and GND on the RCA plug for a very small subset of TVs



Don't forget to connect all the ground wires together!








Audio Amplifier

Using the LM386 Audio Amplifier

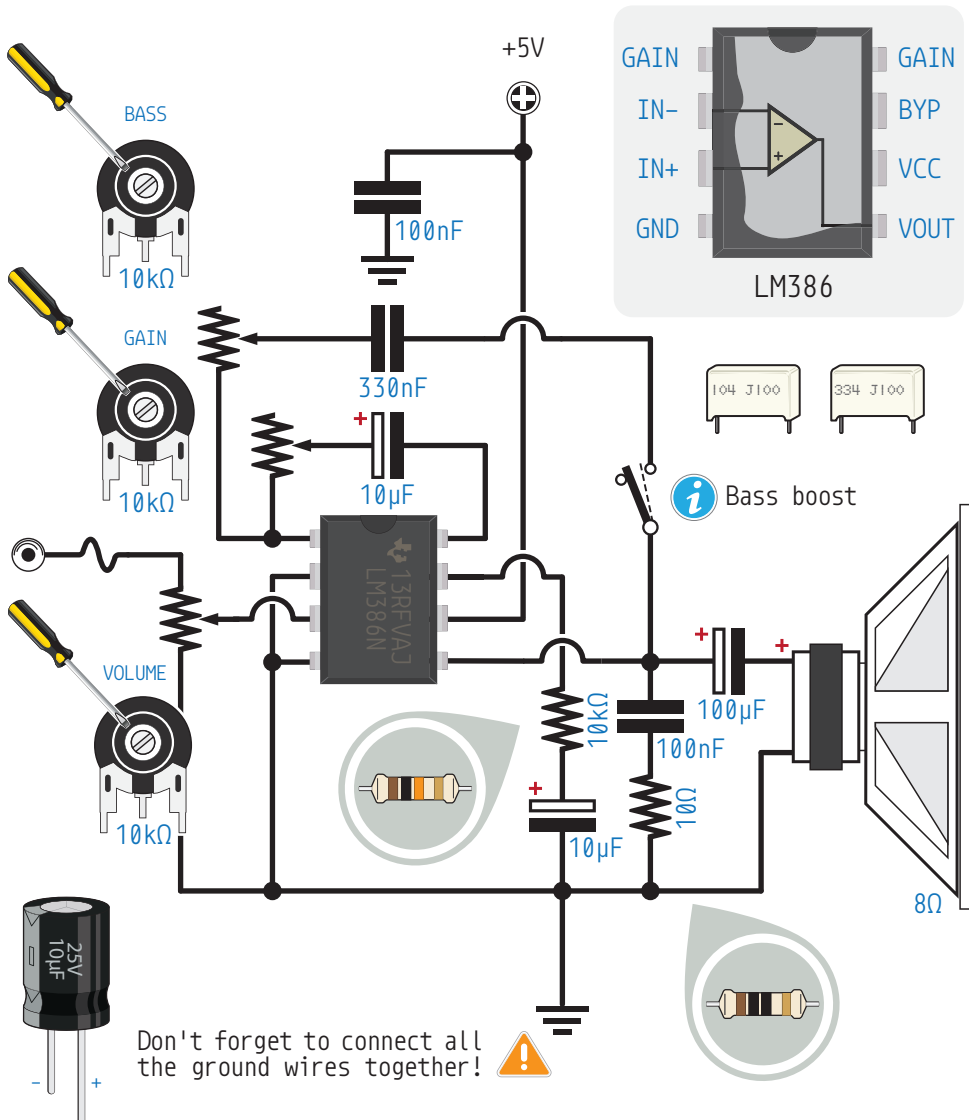




0-1.es/95

95

Preamplifier

Basic Connections

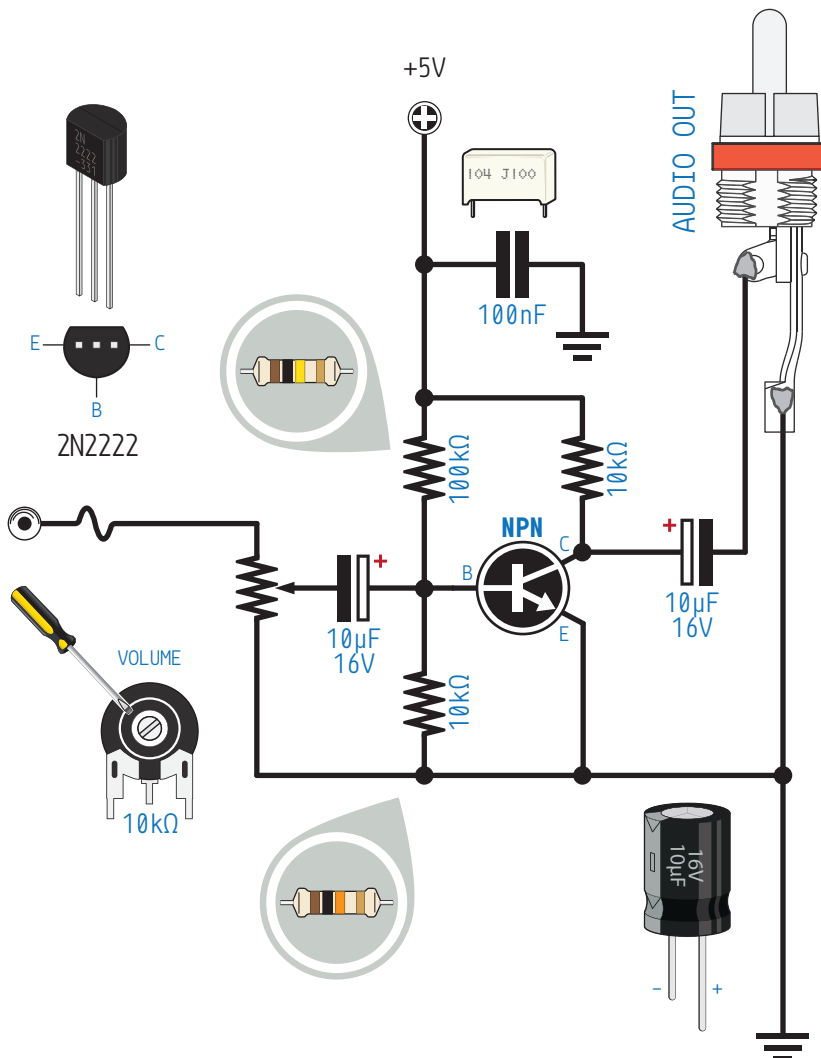

Don't forget to connect all the ground wires together!






96

0-1.es/96

Microphone

Using the LM386 Audio Amplifier

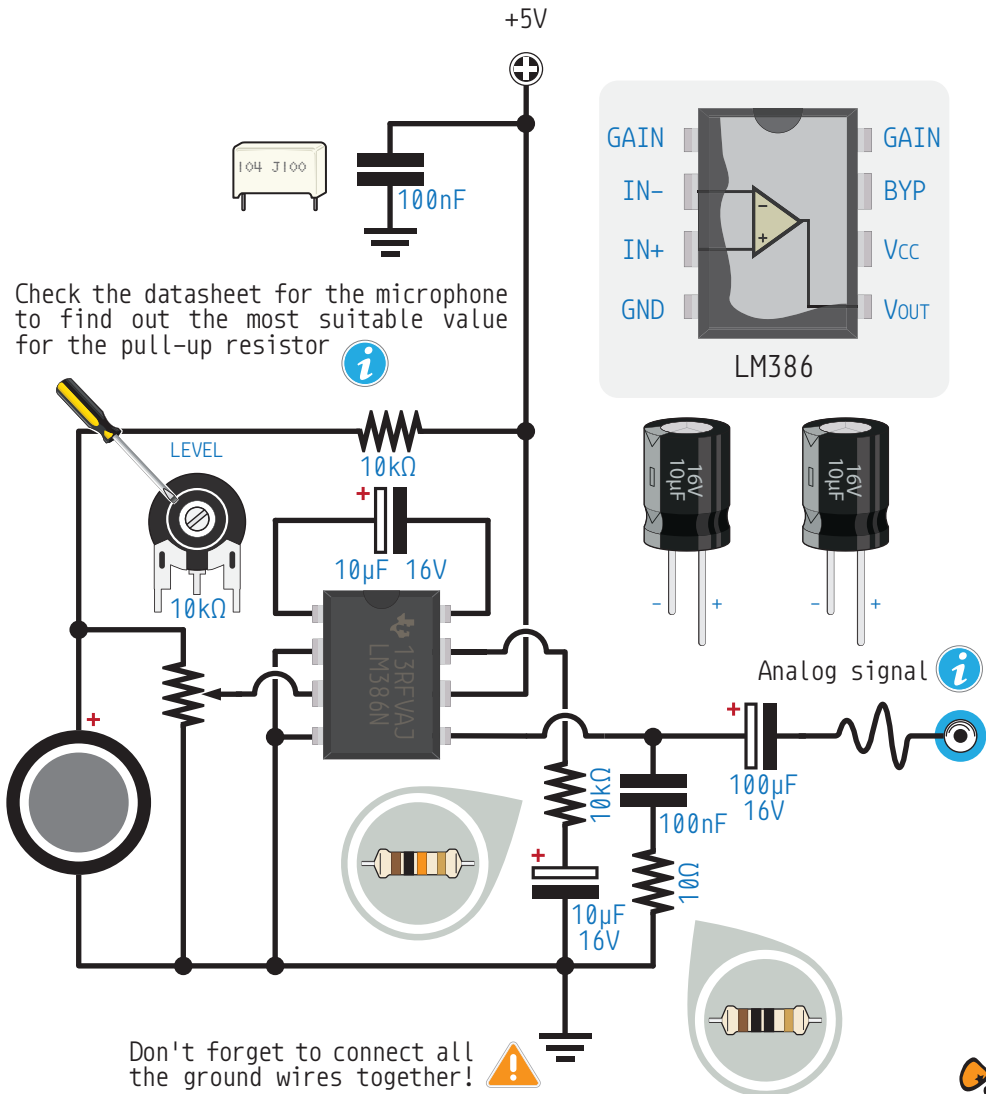




0-1.es/97

97

Simple 5V Power Supply

Basic Connections

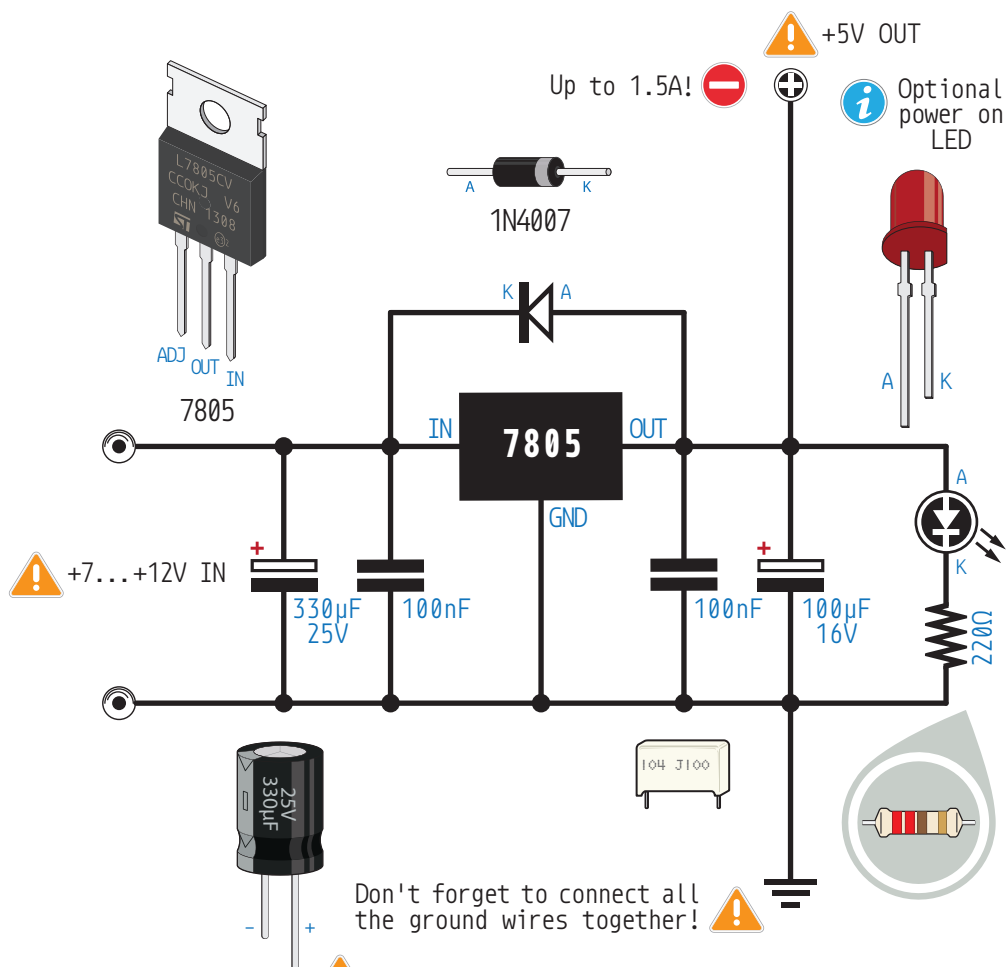

Don't forget to attach a heat sink to the 7805 if are connecting a high-power load!




98

0-1.es/98

Simple 3.3V Power Supply

Basic Connections

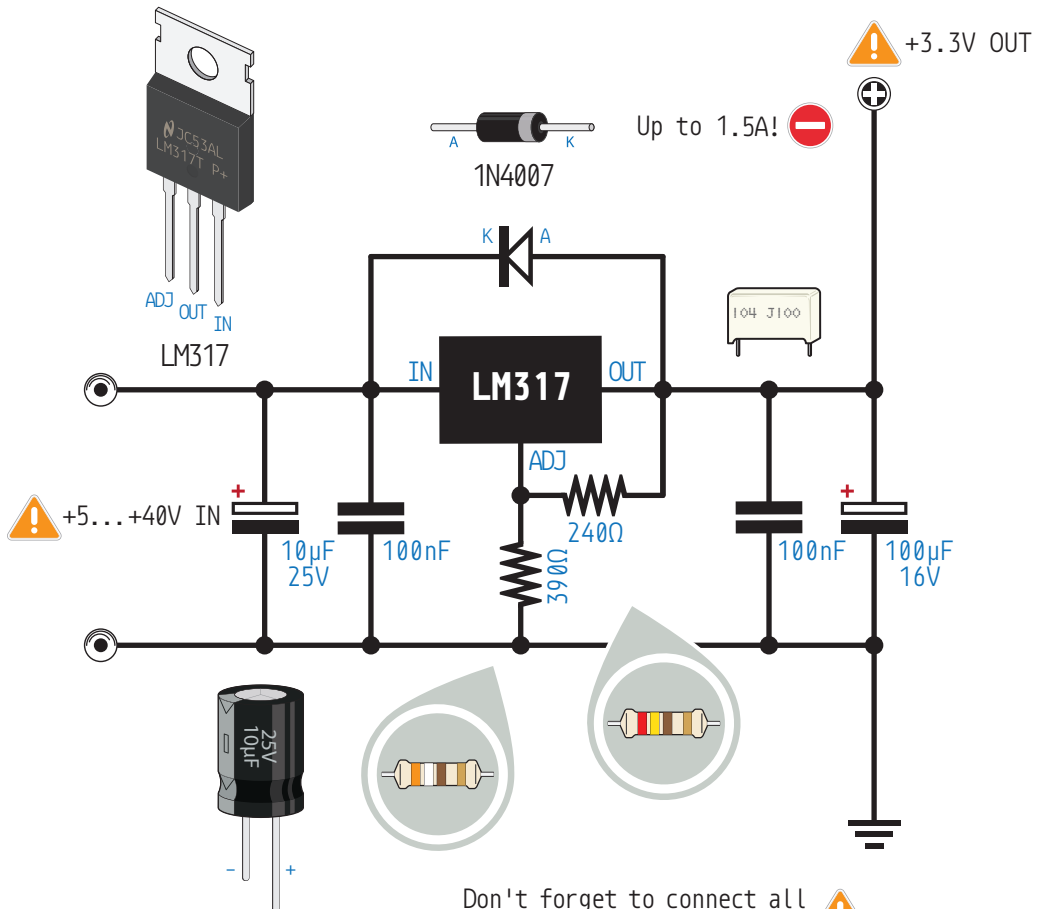

Don't forget to connect all the ground wires together! ⚠



Don't forget to attach a heat sink to the LM317 if are connecting a high-power load!






0-1.es/99



99

Simple Adjustable Power Supply

Using the LM317 Voltage Regulator

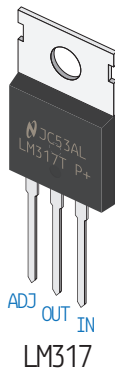

Up to 1.5A!

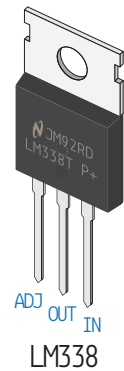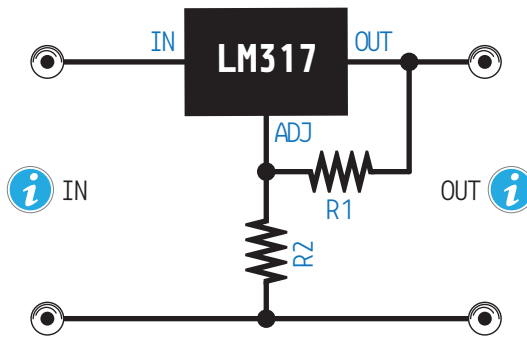

Up to 5A!

i You can use a trimmer instead of R1 and R2 to adjust the output voltage manually

$$V_{OUT} = 1.25 \times (1 + (R2 / R1))$$
$$V_{OUT} = 1.25 \times (1 + (390 / 240))$$
$$V_{OUT} = 3.28V$$

V _{OUT}	R1	R2
3.3V	240Ω	390Ω
5V	240Ω	750Ω
6V	240Ω	1kΩ
9V	240Ω	1.5Ω






100



0-1.es/100

Full-Wave Rectifier

Basic Connections

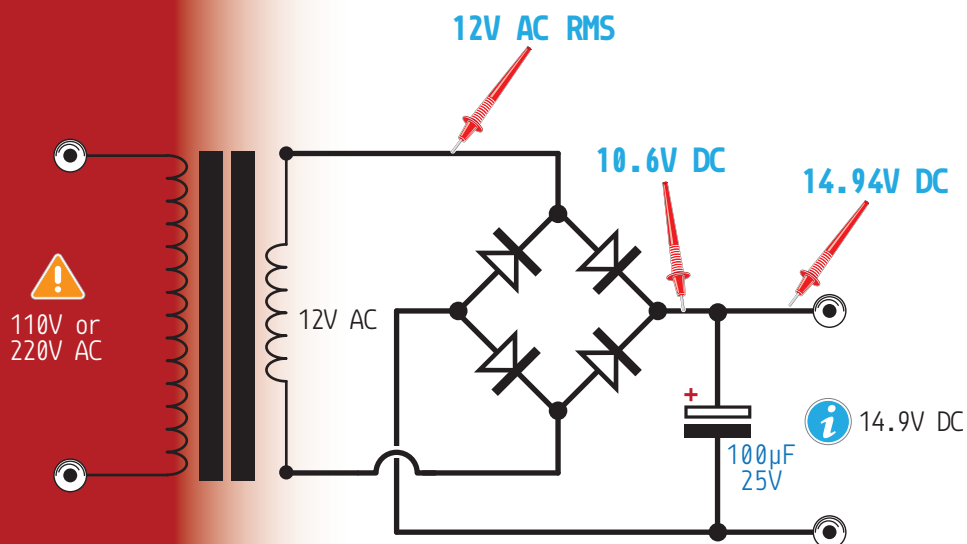

Bridge Rectifier

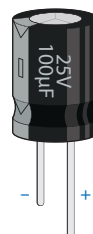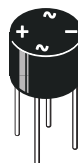

i When using a bridge rectifier and a capacitor

$$V_{OUT} = (V_{IN} - 1.4) \times 1.41$$

$$V_{OUT} = (12 - 1.4) \times 1.41$$

$$V_{OUT} = \mathbf{14.946V}$$



WARNING!



Mains voltage electricity is very dangerous. There is a high risk of death through electrocution if mains electricity is allowed to pass through your body, adding to the risk of fire or explosion if electricity is not cabled and fused correctly. **NEVER** connect mains voltage to a breadboard!

Use the instructions and suggestions in ABC: Basic Connections at your own risk. PighiXXX and the author disclaim all responsibility for any resulting damage, injury, or expense. It is your responsibility to make sure that your activities comply with the safety precautions.

WARNING!



Generally, dealing with voltages lower than 50V is relatively safe, but anything above that can be dangerous. Always make the proper connections with the wires **disconnected** from the power outlet. Isolation between wires and other parts of the circuit that work at lower voltages is crucial. Always use wires rated for the voltage and current applied to them. This also applies, specifically for current, for all circuits covered in this book.

Unless otherwise stated, do not connect DC signal ground (GND) and AC ground (earth) together!




0-1.es/101

101

TRIAC

Using the MOC3023S

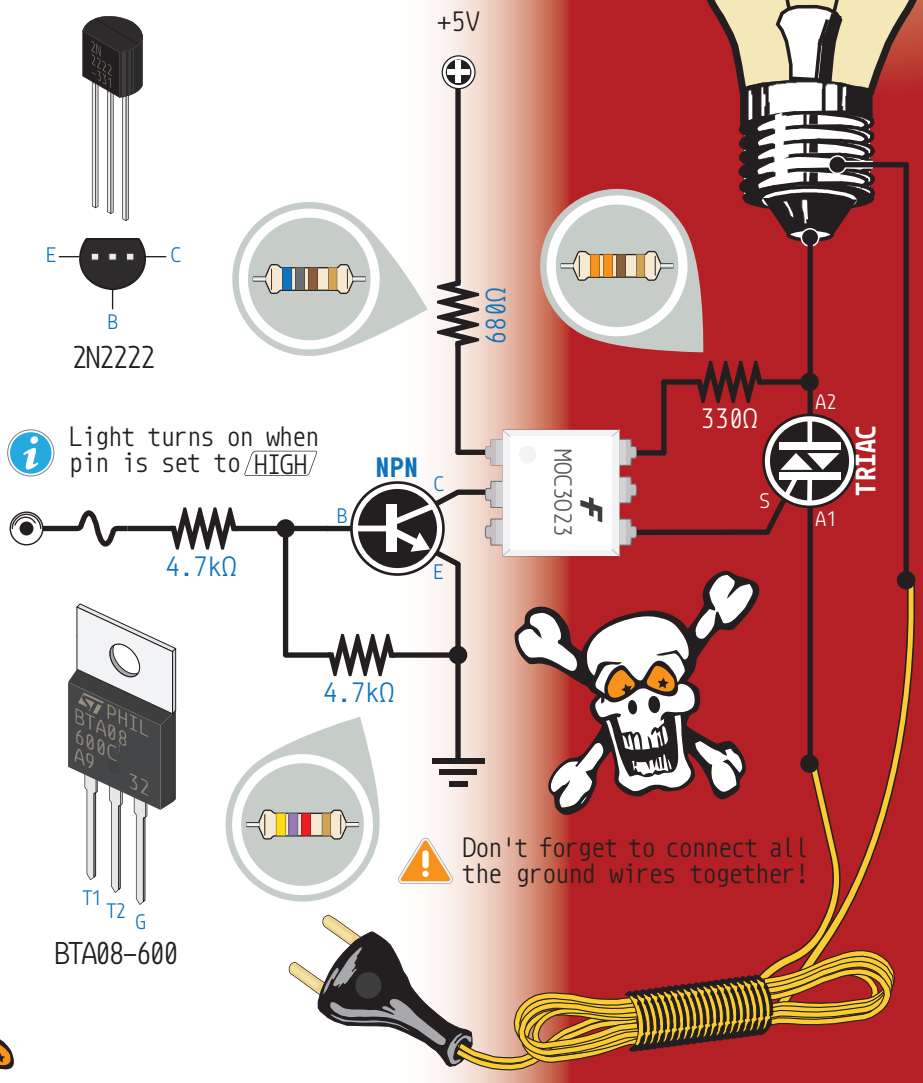


102

0-1.es/102

Zero-Crossing Detector

Using the H11AA1 Optocoupler

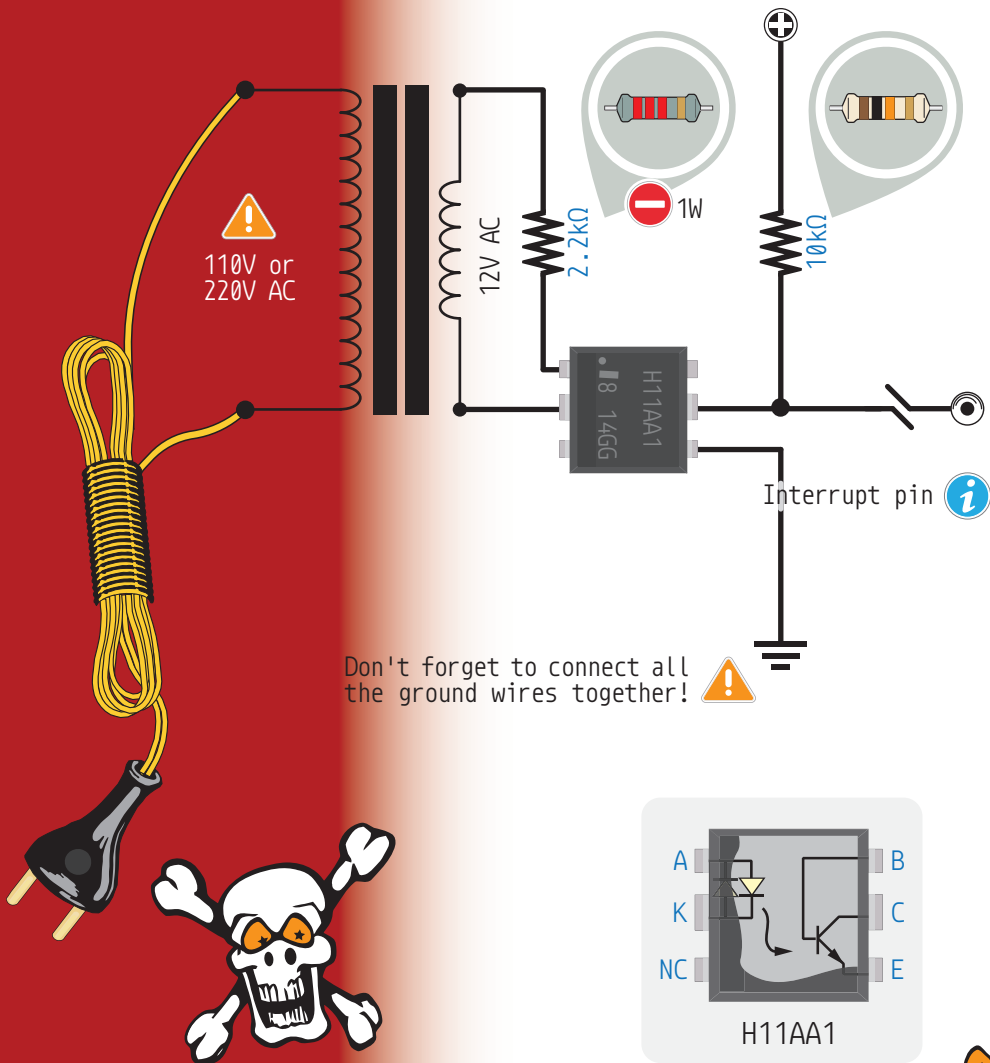




0-1.es/103

103

Solid-State Relay

Basic Connections

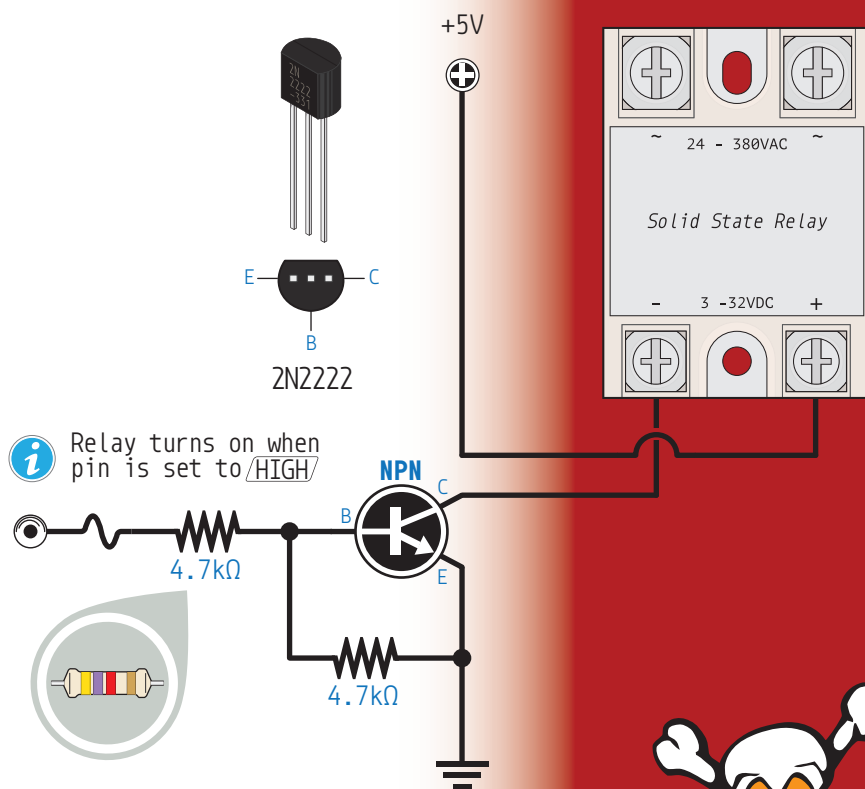




104

0-1.es/104

RC Snubber Network

Theory

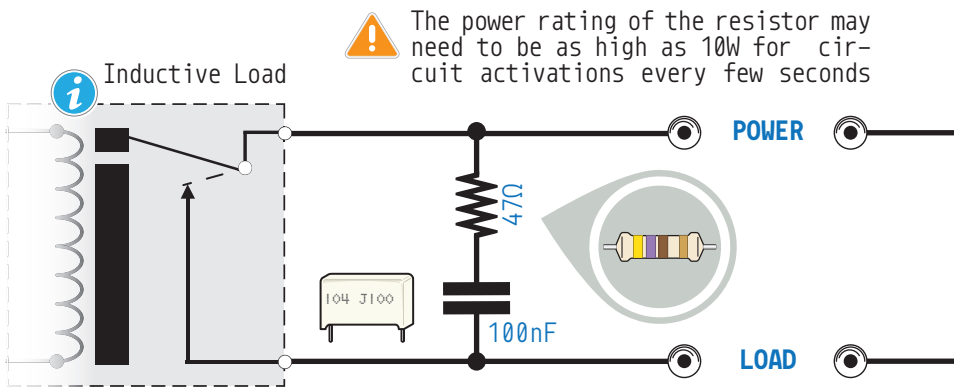

The power rating of the resistor may need to be as high as 10W for circuit activations every few seconds



The capacitor must be non-polarized and its voltage rating = voltage × (2 to 4)

FORMULA

$$C = \frac{I^2}{10}$$

$$R(\Omega) = \frac{E}{10 \times I \times (I + \frac{50}{E})}$$

SIMPLE FORMULA

$$R(\Omega) = \text{voltage(V)} \times (.5 \text{ to } 1)$$

$$C(\mu\text{F}) = \text{current(A)} \times (.5 \text{ to } 1)$$



Standard values are 47Ω for the resistor and 100nF for the capacitor



Snubbers are used in electrical systems with an inductive load where the sudden interruption of current flow leads to a sharp rise in voltage across the current switching device. A simple RC snubber uses a resistor and a capacitor in series to suppress a rapid rise in voltage.






0-1.es/105

105

Soft Latching Power ON Switch

Basic Connections

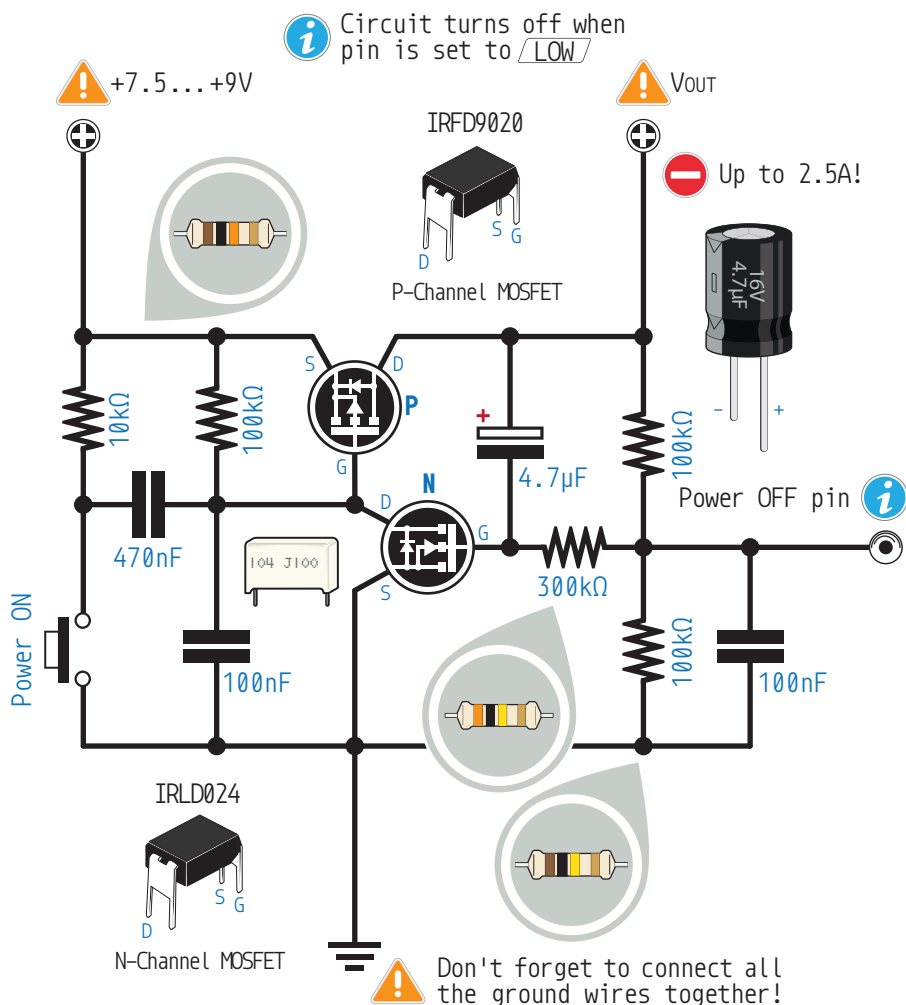




0-1.es/106

Reverse Voltage Protection

Basic Connections

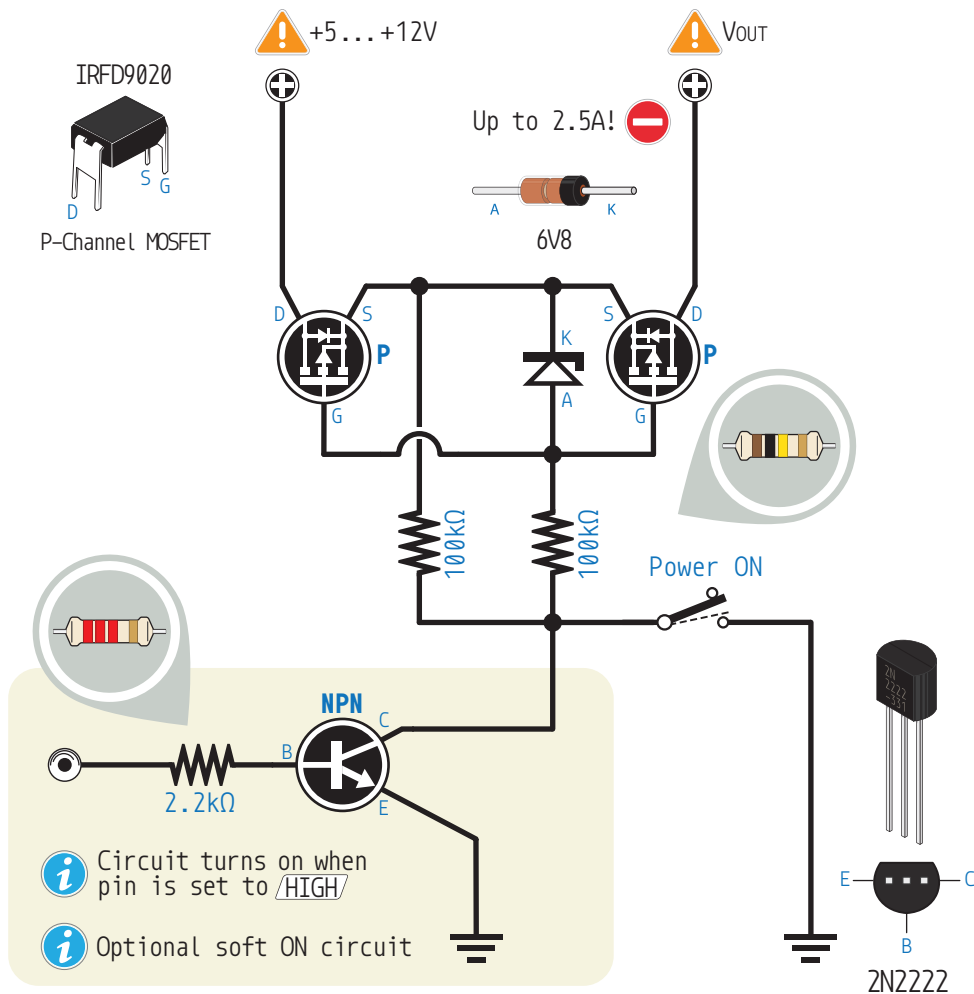


Don't forget to connect all the ground wires together! 





RS-485 Node Using the 75176 Transceiver

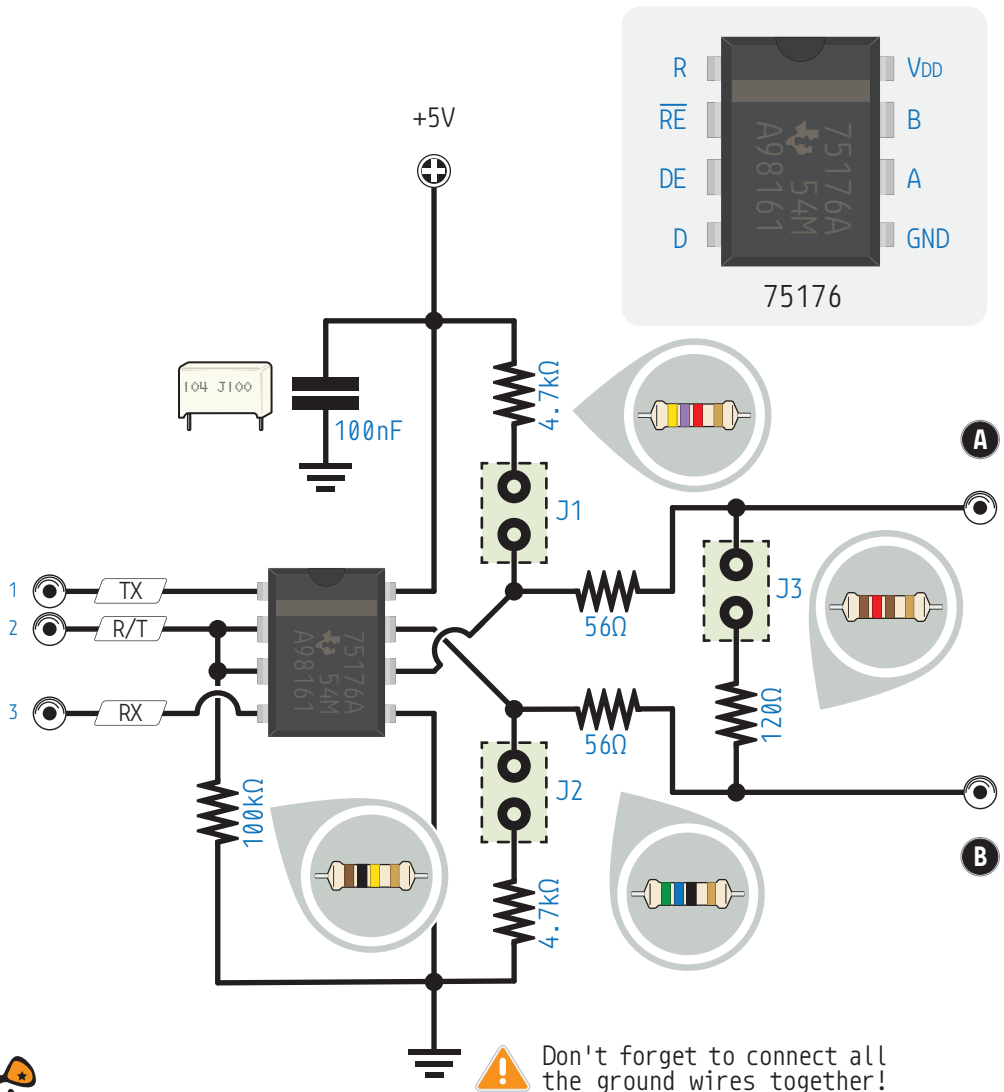




107

RS-485 Interface

Node Termination Jumpers

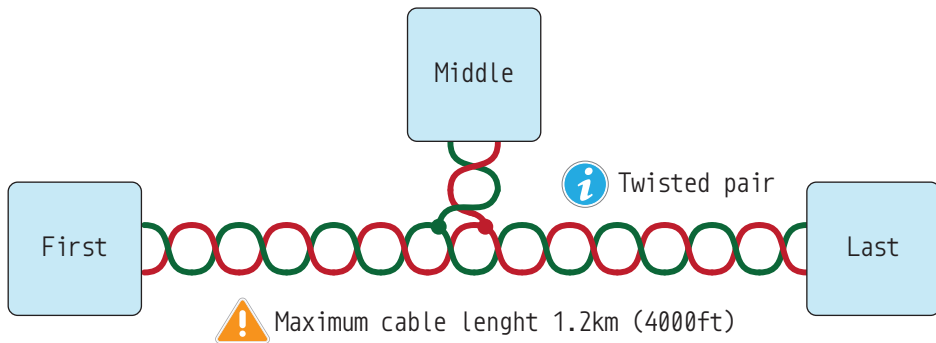

First Node



Middle Node



Last Node



Maximum number of drivers and receivers per line: 32



RS-485 is a standard for serial communication transmission of data, especially useful to transmit data over long distances and in electrically noisy environments. Typical applications are process automation (chemicals, brewing, paper mills), factory automation, security, and motor control.






0-1.es/108


108

MIDI IN

Using the 6N138 Optocoupler

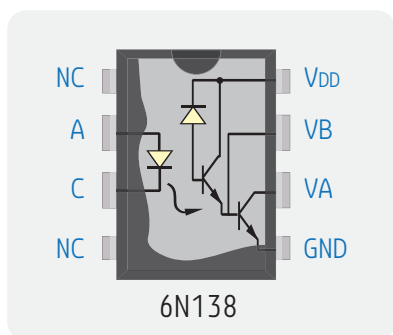

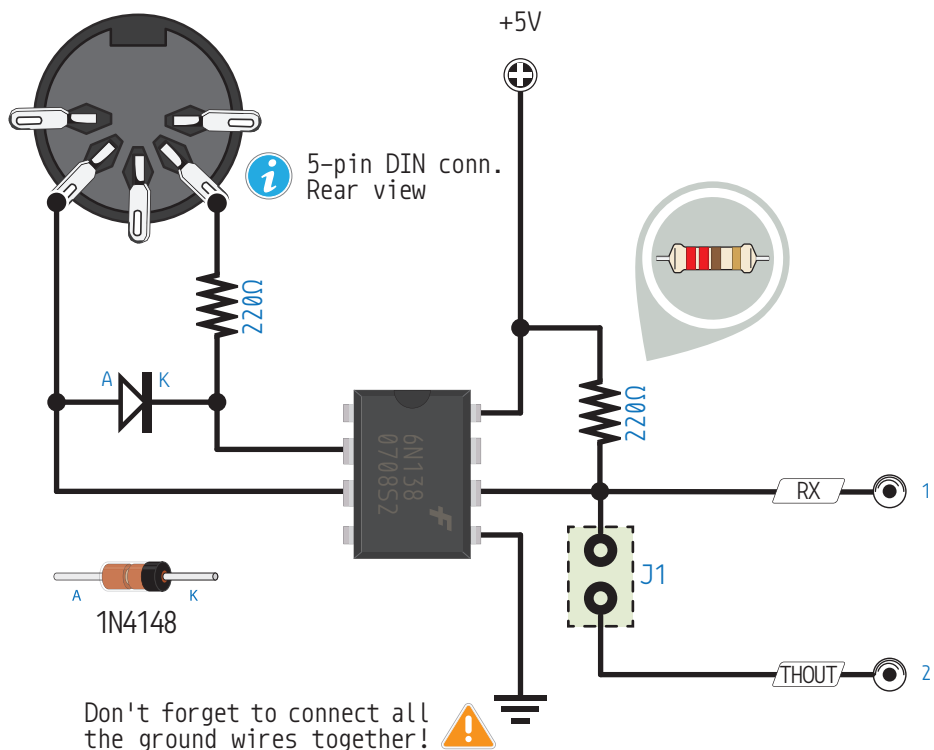i Short J1 to copy data stream from the input to the THRU port



Don't forget to connect all the ground wires together! **!**




109

0-1.es/109

MIDI OUT

Using the 74HCT125 Bus Buffer

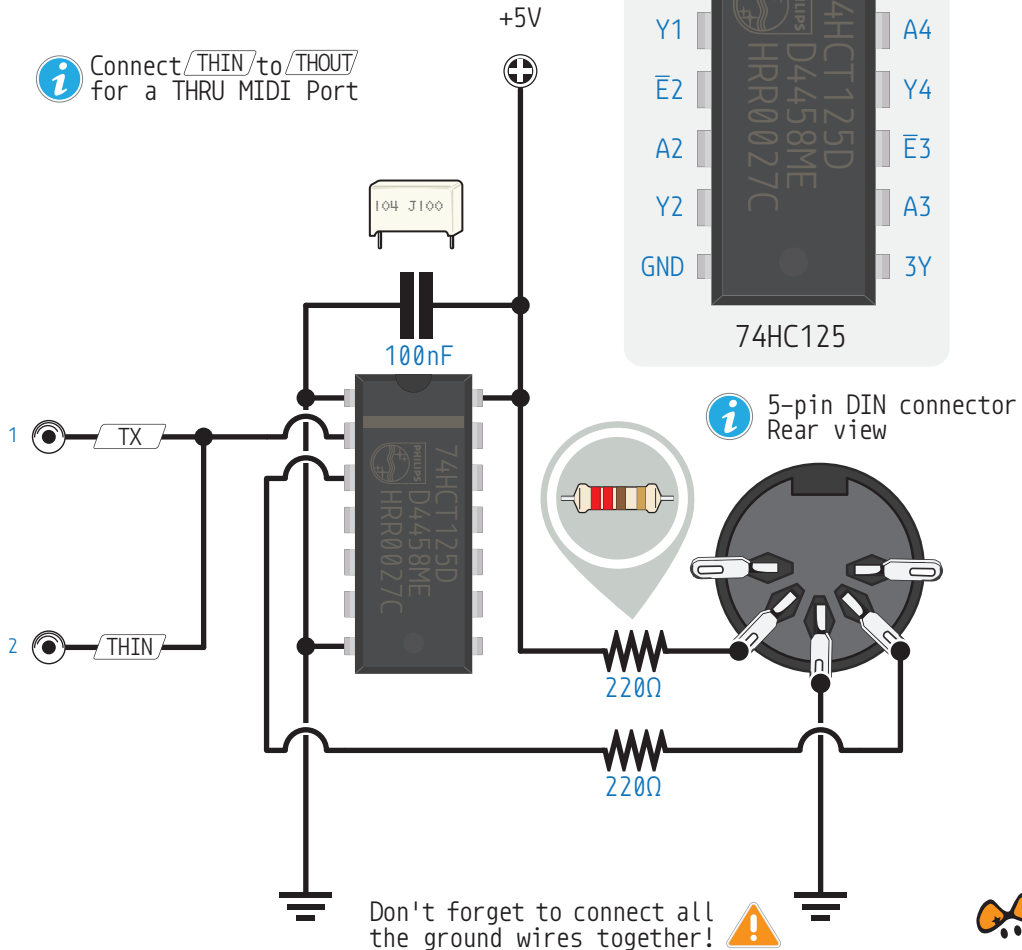i Connect THIN to THOUT for a THRU MIDI Port






0-1.es/110

110

Multiple MIDI OUT

Basic Connections

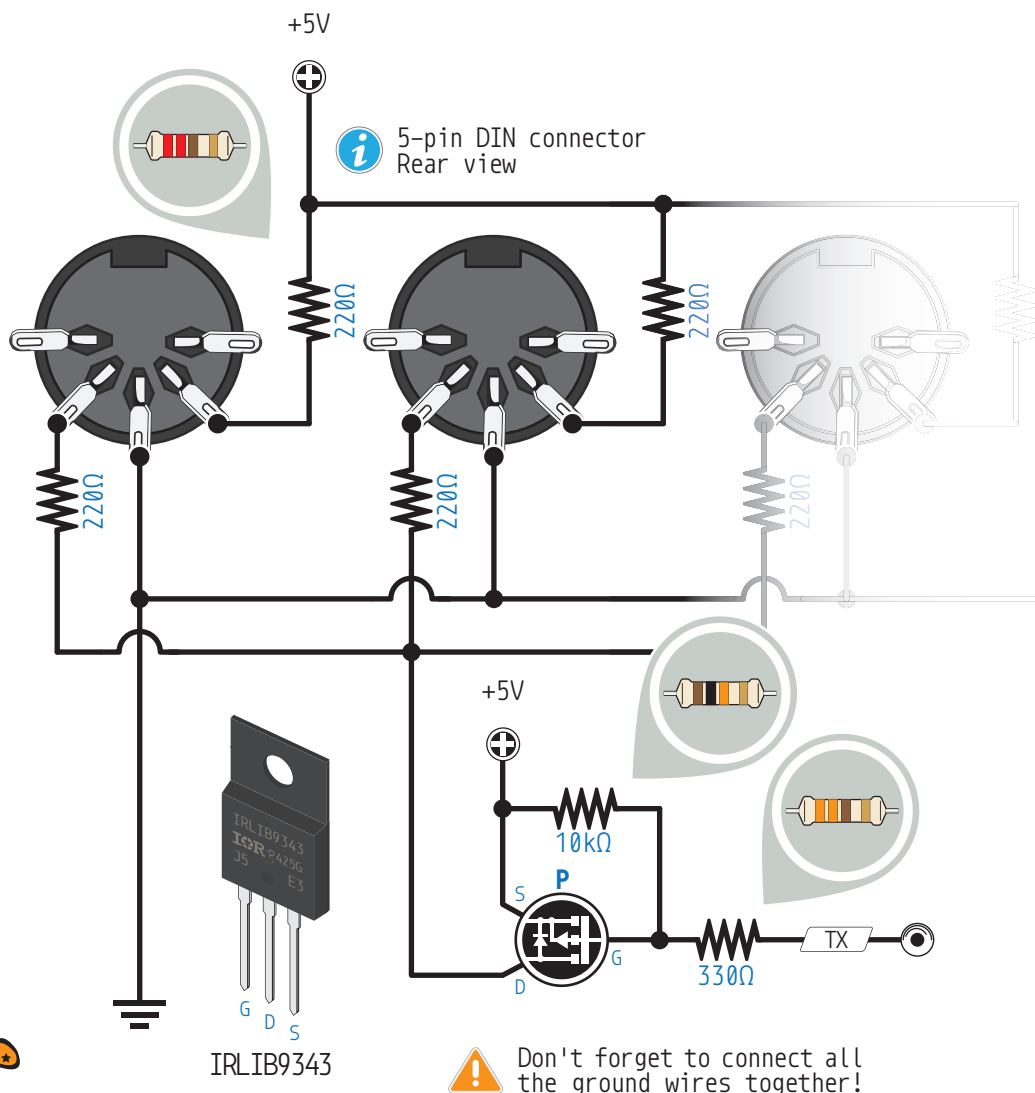




110

0-1.es/110

MIDI


Pinout

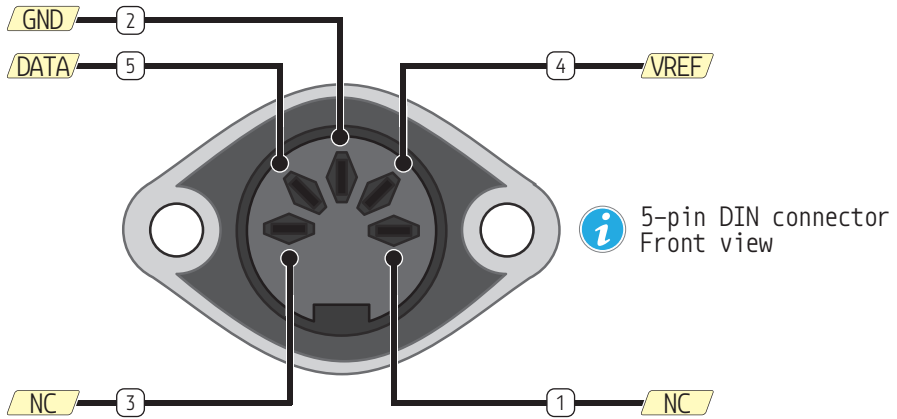

i Pins **3** and **1** are used for implementing power over MIDI

MIDI Daisy Chain

i Shielded twisted pair

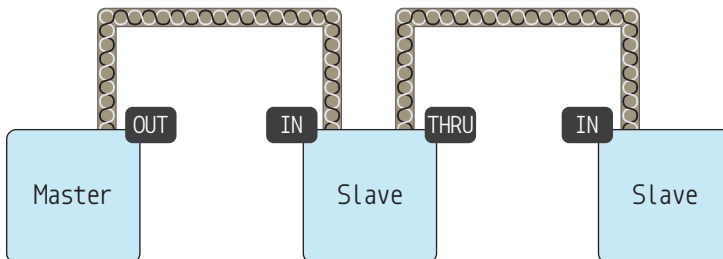

MIDI is a widely-used protocol that allows a wide variety of electronic musical instruments, computers and other related devices to connect and communicate with one another. You can build a MIDI controller with your microcontroller board and connect it to your computer to control a sequencer and play music!






0-1.es/111

111

DMX Interface

Using the 75176 Transceiver

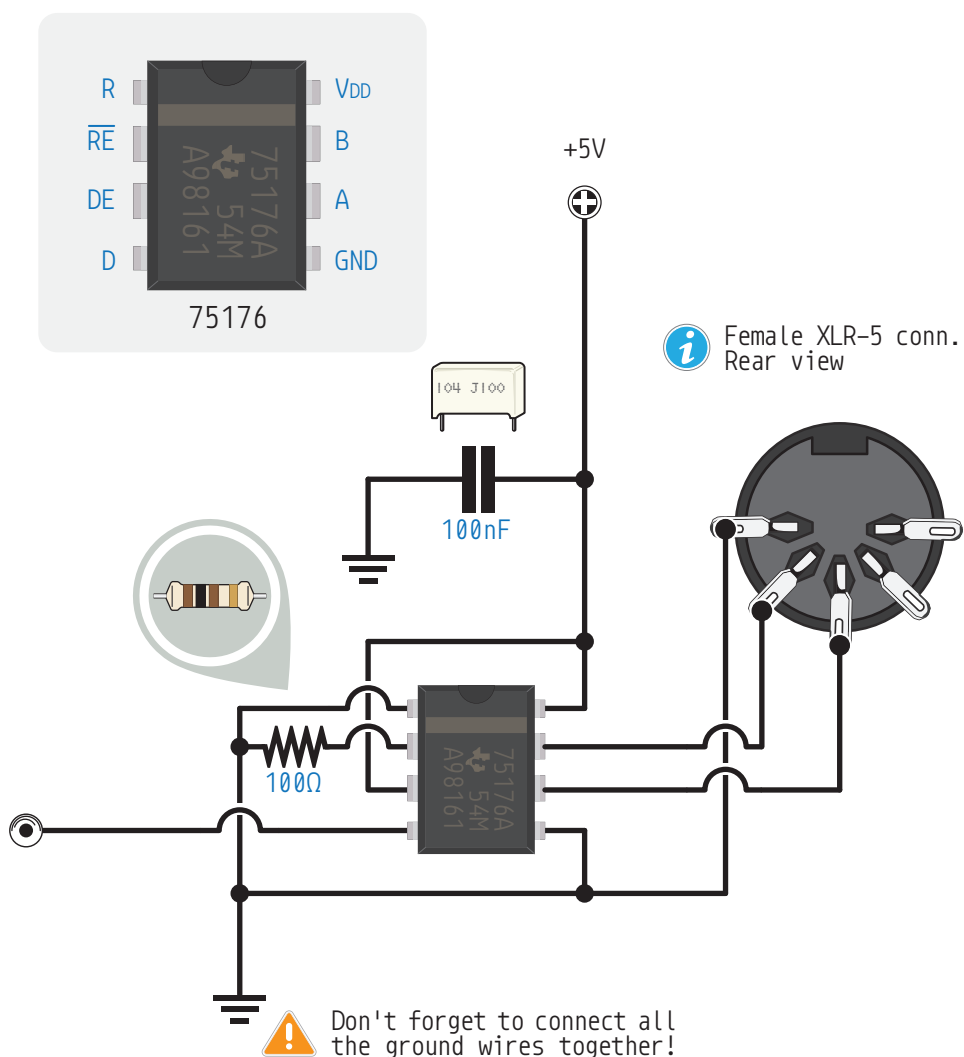





111

0-1.es/111

DMX Pinout

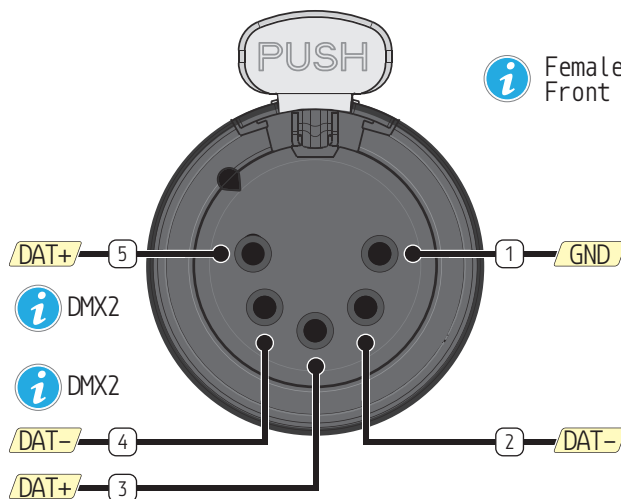

i Female XLR-5 connector
Front view

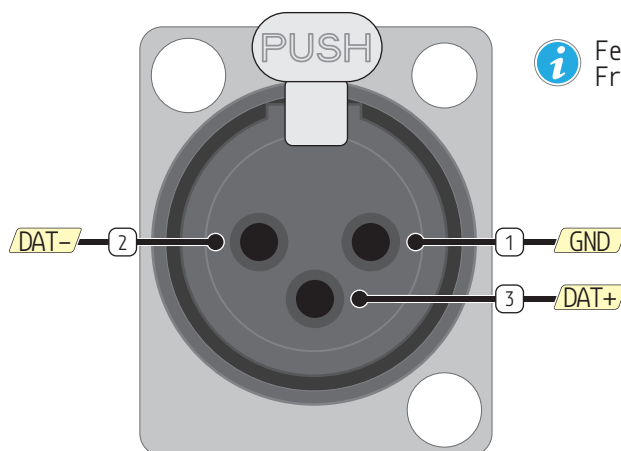

i Female XLR-3 conn.
Front view






0-1.es/112

112

RS-232 Interface

Using the MAX232 RS-232 Driver

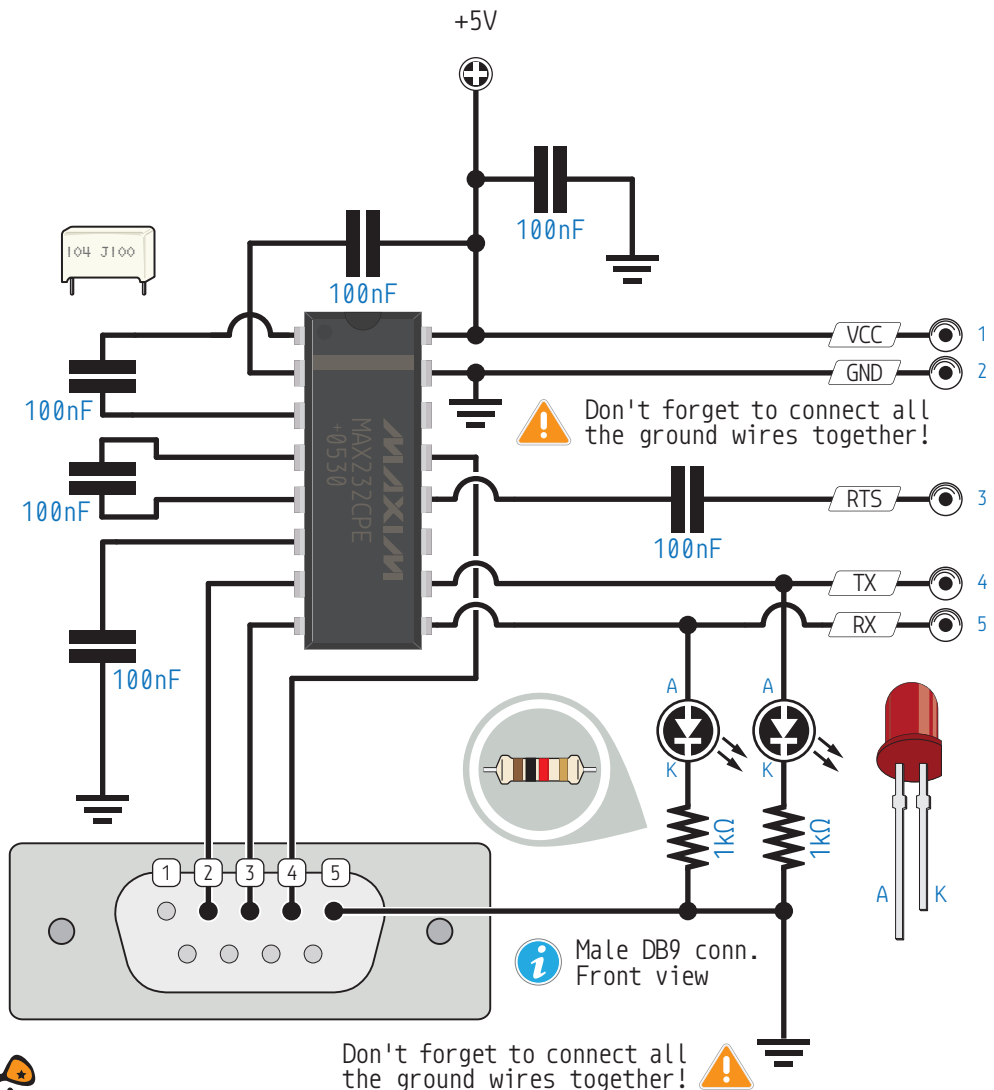





112

0-1.es/112

RS-232 MAX232 Pinout

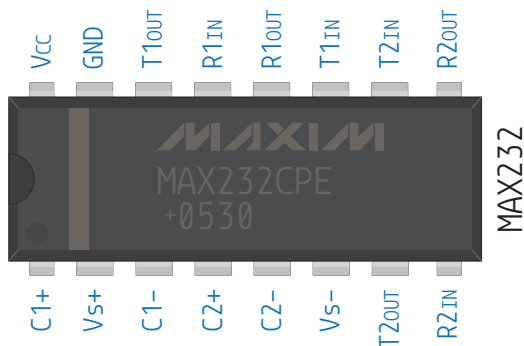

RS-232 Pinout

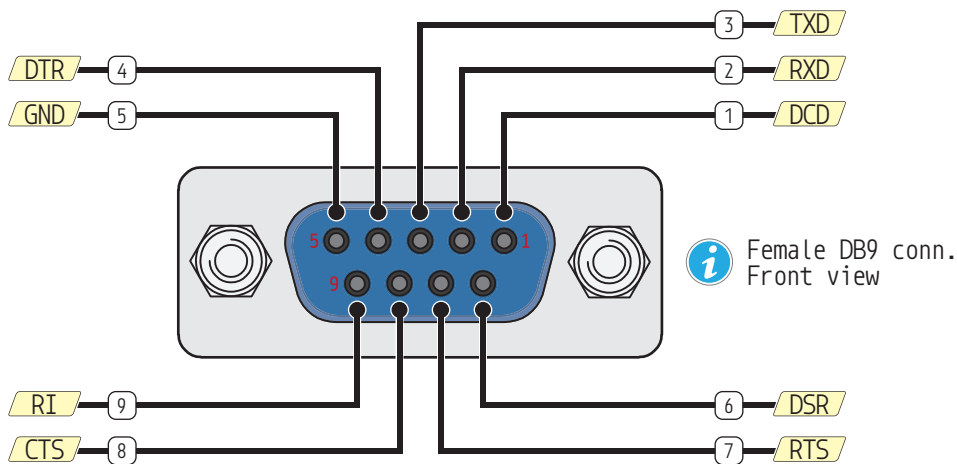

RS-232 is a standard for serial communication transmission of data. It was once a standard feature of a personal computer, but USB has displaced it from most of its peripheral interface roles mainly because of its low transmission speed. Nevertheless, RS-232 devices are still used, especially in industrial machines.






0-1.es/113

113

RTC

Using the DS1307 I²C RTC

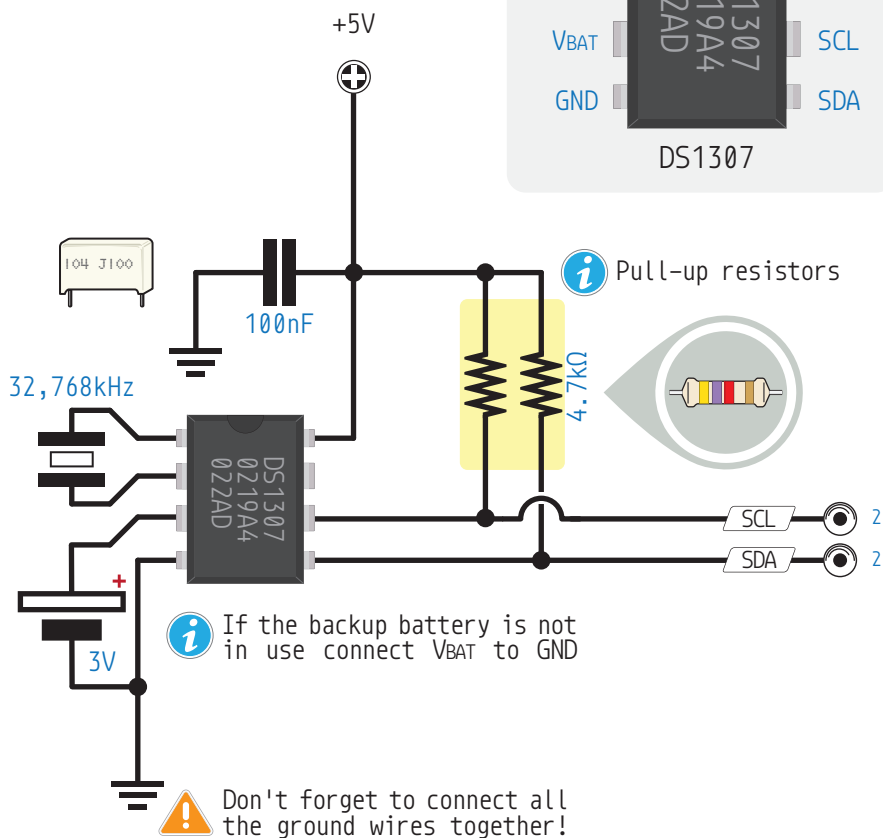




114

0-1.es/114

EEPROM

Using the 24Cxx Series EEPROM

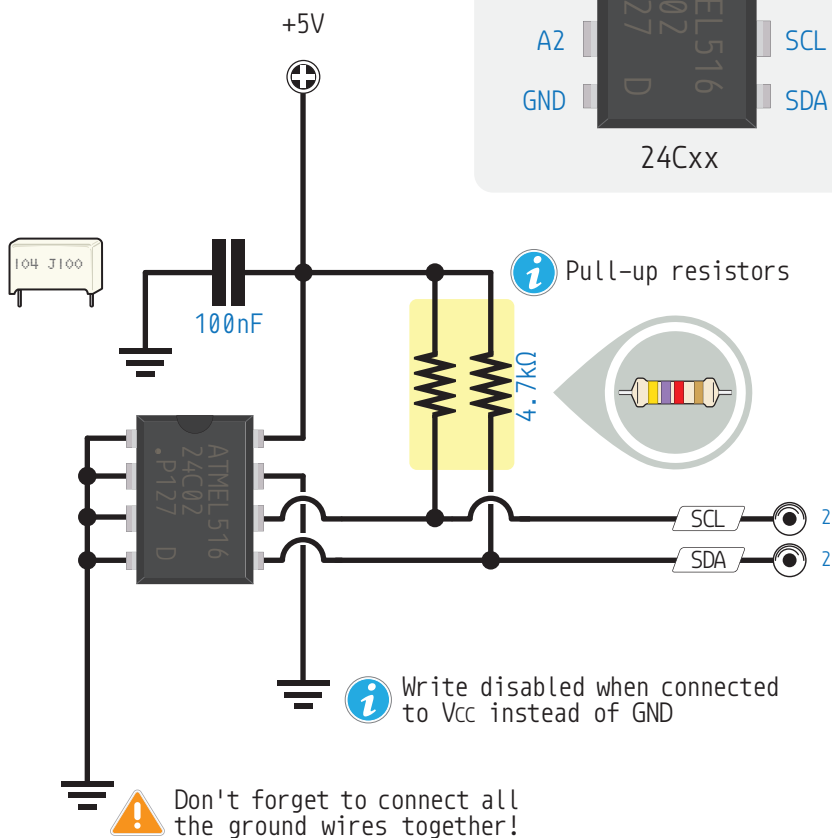




0-1.es/115

115

Digital Potentiometer


Using the MCP416x

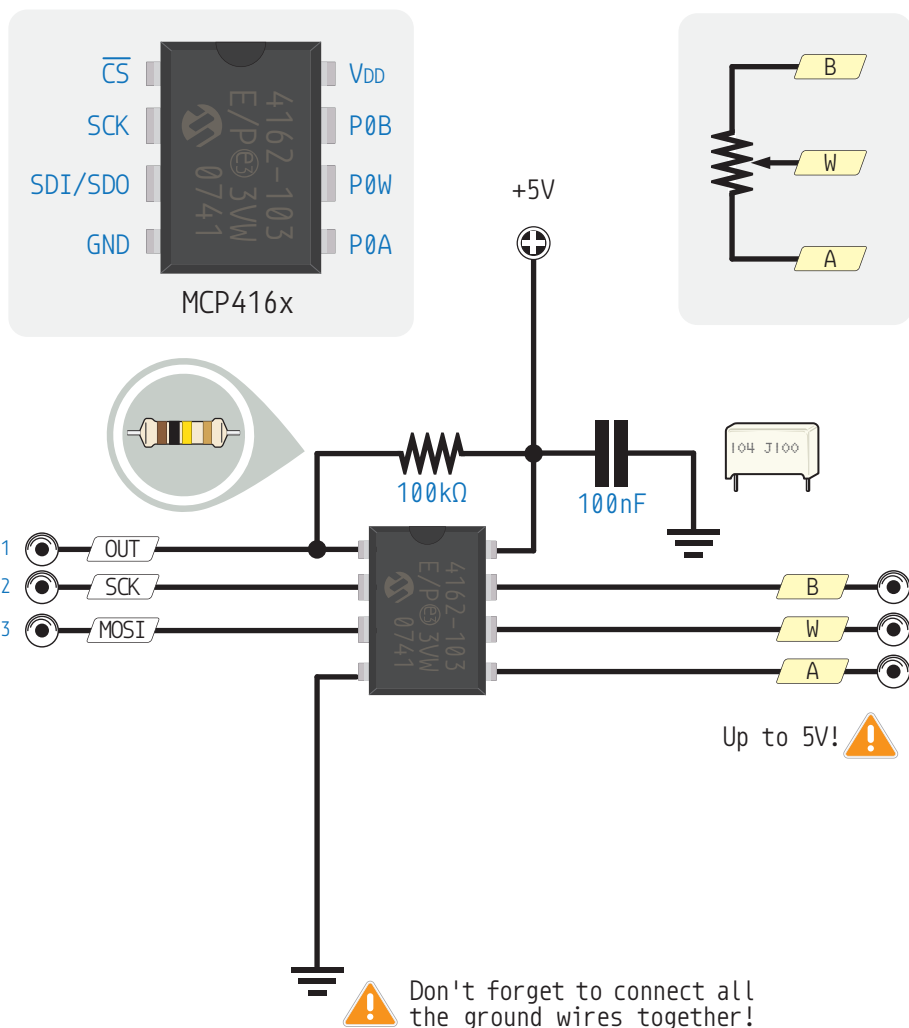



Buffer

Using the LM358

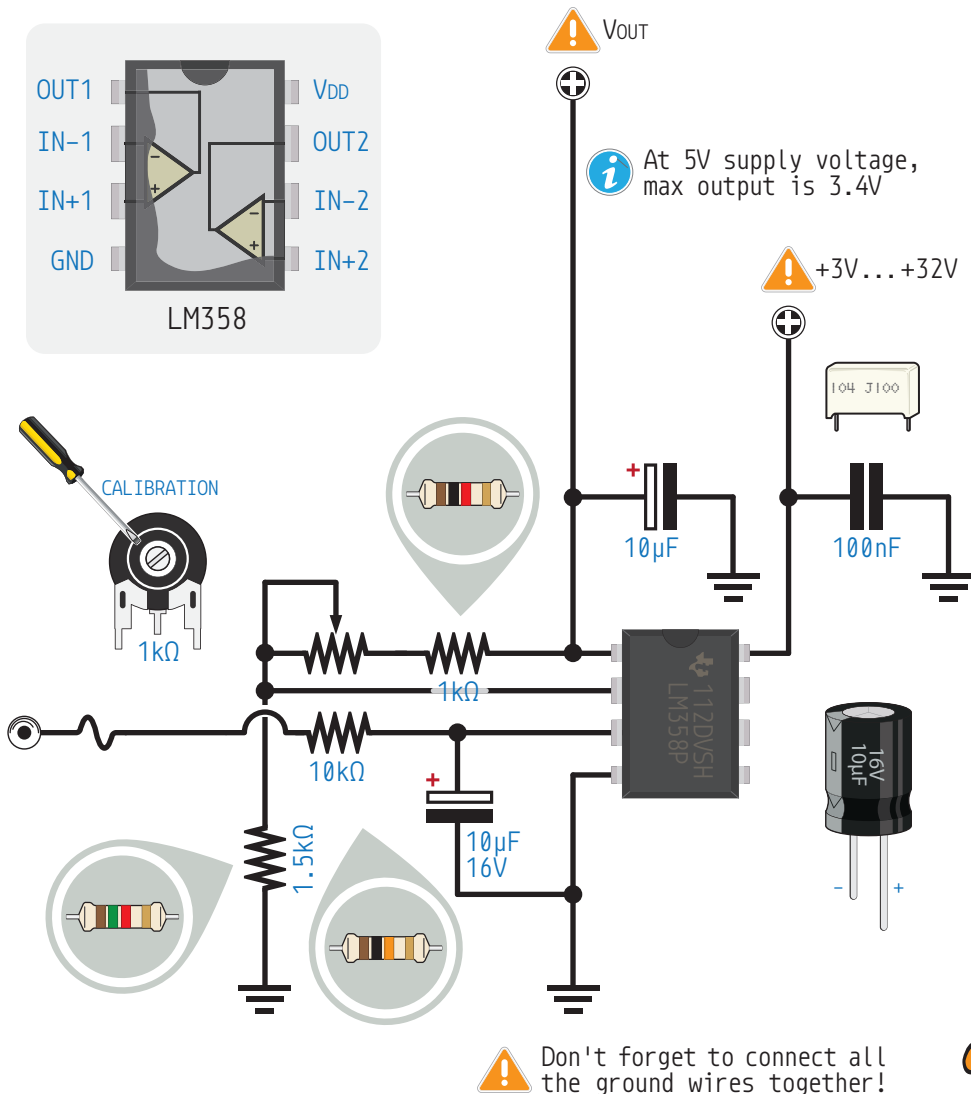




0-1.es/117

117

Hall Effect Sensor

Using the SS49E Hall Effect Sensor

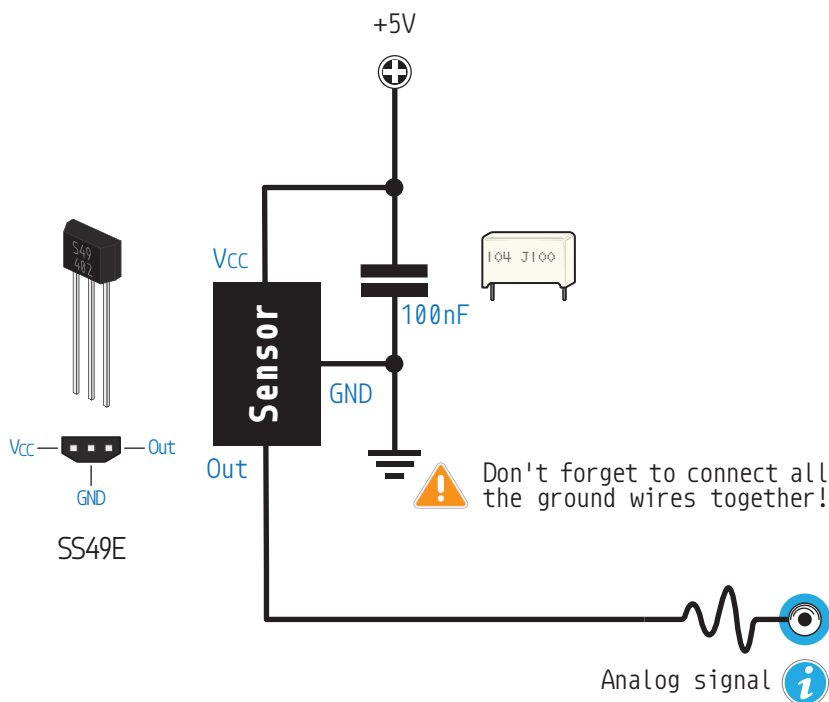

A Hall effect sensor is a transducer that varies its output voltage in response to a magnetic field. The output voltage is set by the supply voltage and varies linearly in proportion to the strength of the magnetic field. They are used for proximity switching, positioning or speed detection.






0-1.es/118

Spectrum Analyzer

Using the MSGEQ7 Equalizer

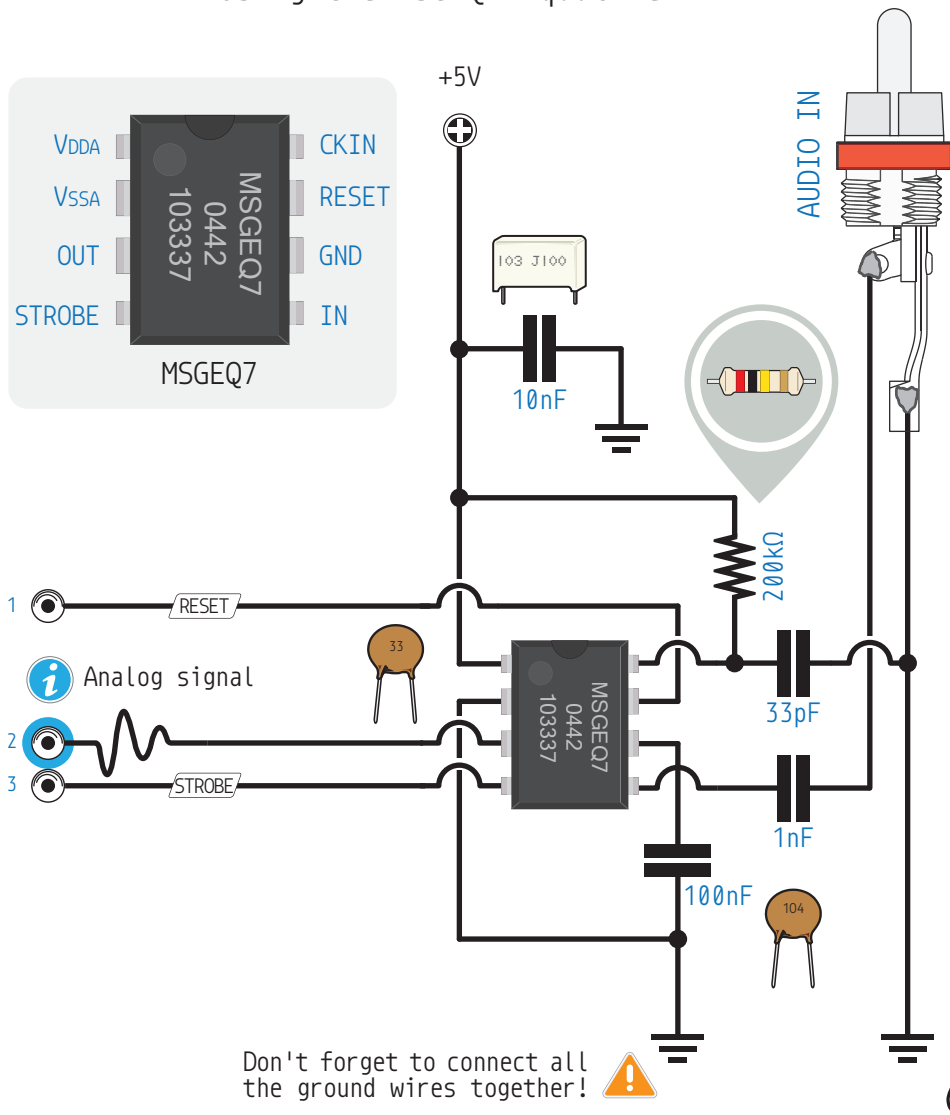




0-1.es/119

119

Flex Sensor

Basic Connections

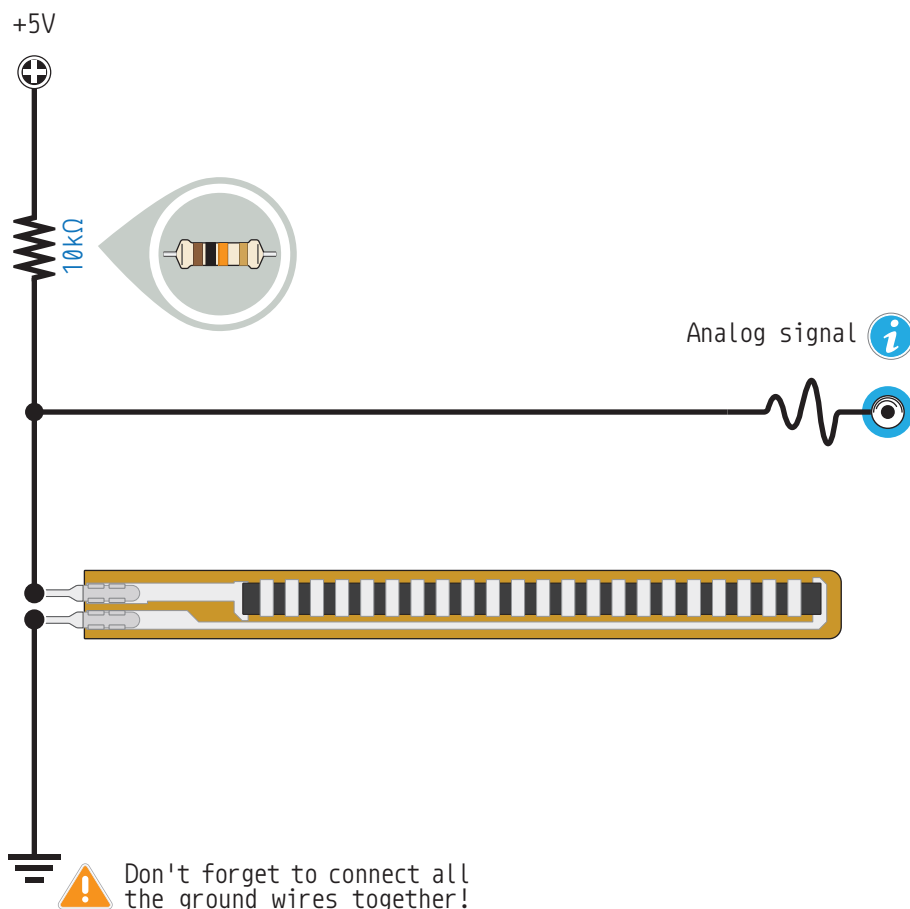

This flex sensor is a variable resistor whose resistance increases as the body of the component bends. Sensors like these were used in the Nintendo Power Glove and are patented technology of Spectra Symbol. Please be careful not to bend them too much, especially at the base of the device, as they can get damaged.






120

0-1.es/120

Piezo Sensor

Basic Connections

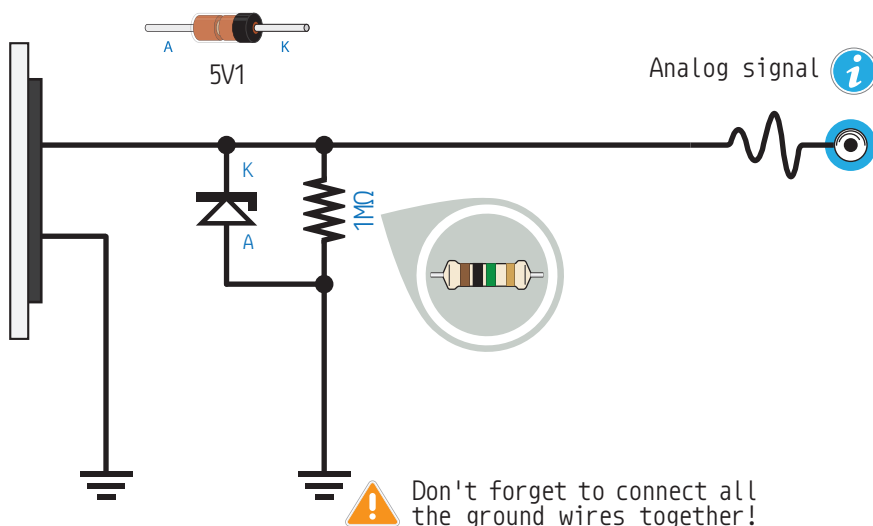

Piezoelectric sensors use the piezoelectric effect to measure changes in pressure, vibration, temperature, strain, or force and converted into a voltage. The piezoelectric effect is generally reversible and sensors can work also as output devices. If you open a piezo buzzer you can hack it into a piezo sensor.






0-1.es/121

121

Op-Amp Threshold Switch

Using the LM358 Op-Amp

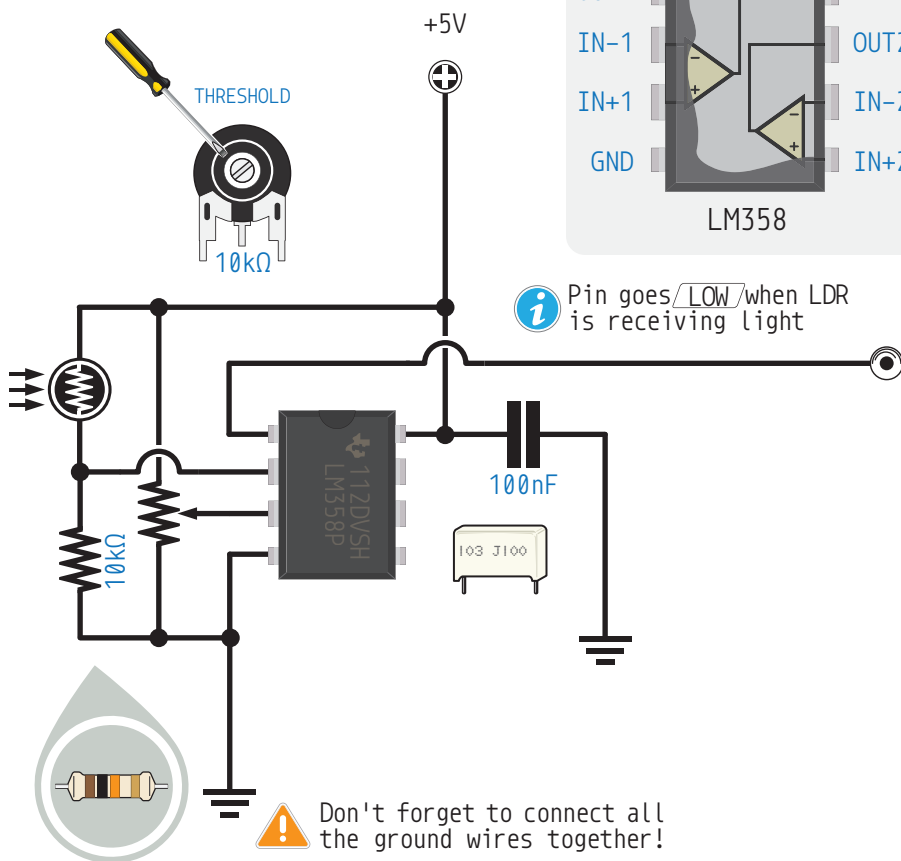

The LM358 op-amp acts as a voltage comparator so you have to adjust the 10kΩ potentiometer for your desired activation threshold. You could replace the photo-resistor with any other resistive sensor!






122

0-1.es/122

DAC

Using the MCP4921 12-Bit DAC

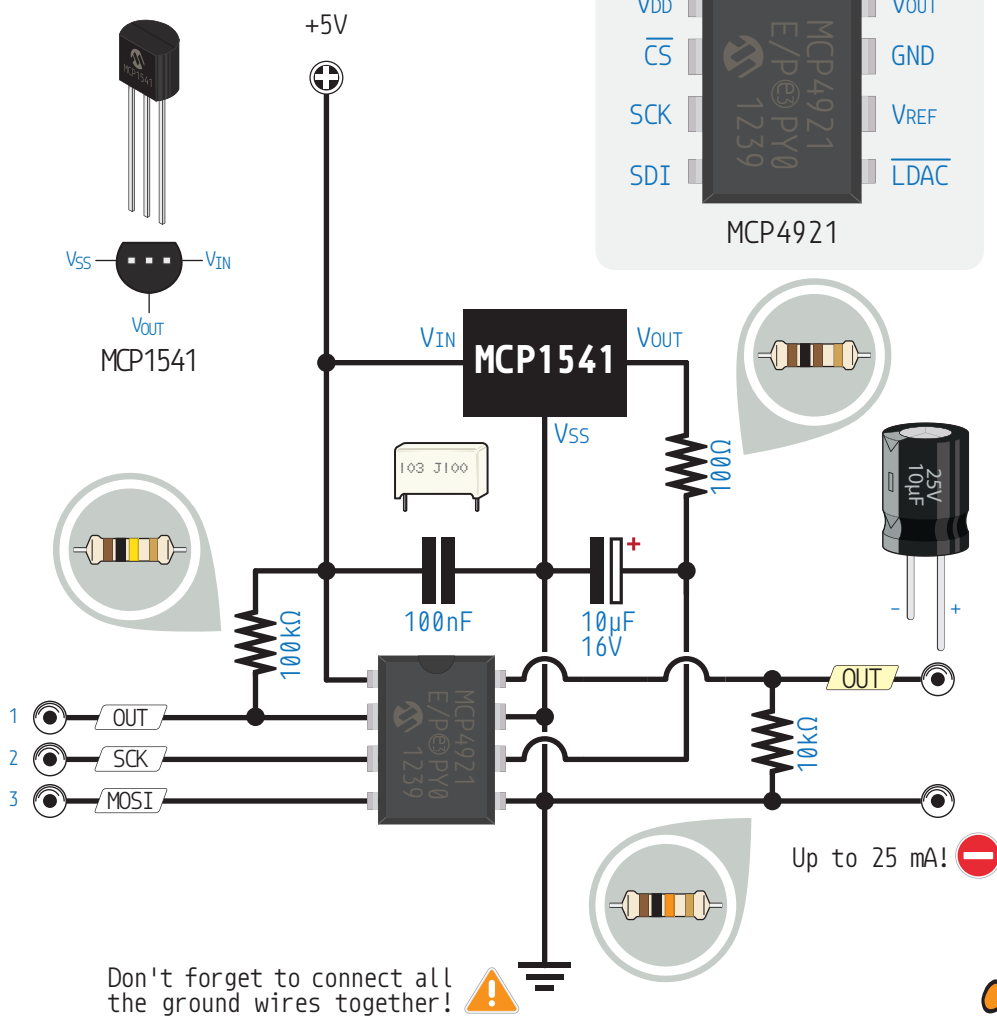



H-Bridge
Using the L293D

100nF

104 J100

L293D
W991Z0145
MALAYSIA

+5V

DIR01

DIR01

DIR01

DIR01

+4.5...36V

100µF 50V

Maximum 600mA per channel!

 Motors power supply!



The L293D is a quadruple high-current half-H driver. It is designed to provide bidirectional drive currents of up to 600mA at voltages from 4.5V to 36V and it is able to drive inductive loads such as relays, solenoids, DC and bipolar stepper motors.






123

0-1.es/123

LD293D

Pinout

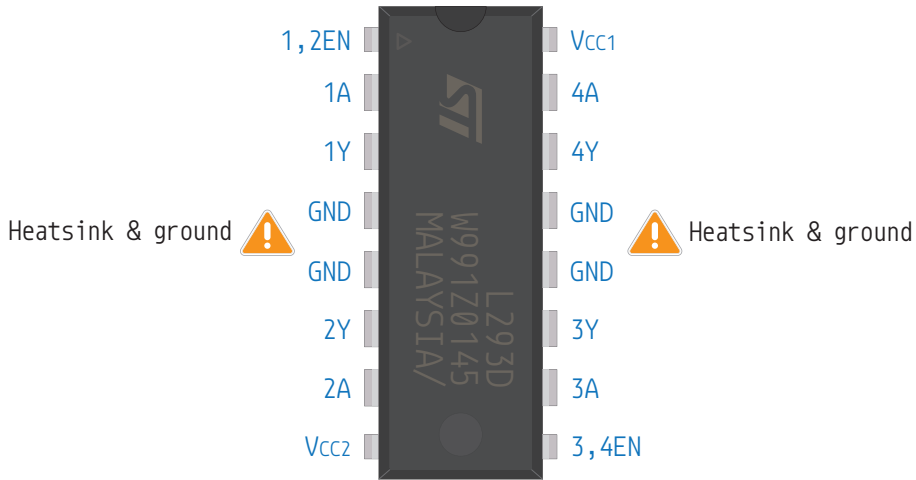

L293D

Function Table

<div><div>DIR01</div><div>DIR10</div></div> <div><div></div><div></div></div> <div><div></div><div>PWM Speed</div></div>	<div><div>DIR01</div><div>DIR10</div></div> <div><div></div><div></div></div> <div><div></div><div>PWM Speed</div></div>	<div><div>DIR01</div><div>DIR10</div></div> <div><div></div><div></div></div> <div><div></div><div>PWM Speed</div></div>





Using the ULN2803 Darlington Transistor Array






124

0-1.es/124

Stepper Motor

Basic Concepts

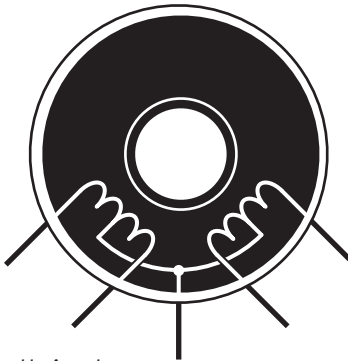There exist two main types of stepper motors: unipolar and bipolar. In essence, they both work in the same way: electromagnets are turned on sequentially, causing the central motor shaft to turn. One difference between the two types is their voltage levels.




Unipolar stepper motor

One difference between the two types is their voltage levels. **Unipolar** stepper motors operate only with positive voltages applied to the electromagnetic coils, e.g., 5V HIGH and 0V LOW.

Bipolar stepper motors have two polarities: positive and negative, so their HIGH and

LOW voltages would be, for instance, 2.5V and -2.5V respectively. This configuration requires H-bridge circuitry to reverse the current flow through the phases, producing the two polarities of the magnetic field. By energizing the phases with alternating the polarity, all the coils can be put to work turning the motor. Bipolar stepper motors have more torque because current flows through the entire coil, producing a stronger magnetic field to induce the shaft to rotate to the appropriate angle.

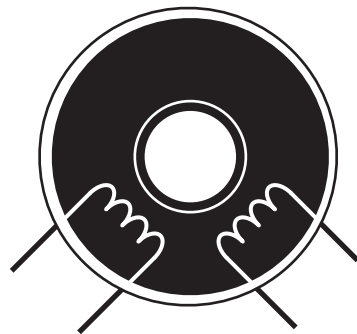

Bipolar stepper motor






0-1.es/125

125

Bipolar Stepper Motor

Using the L293D Motor Driver

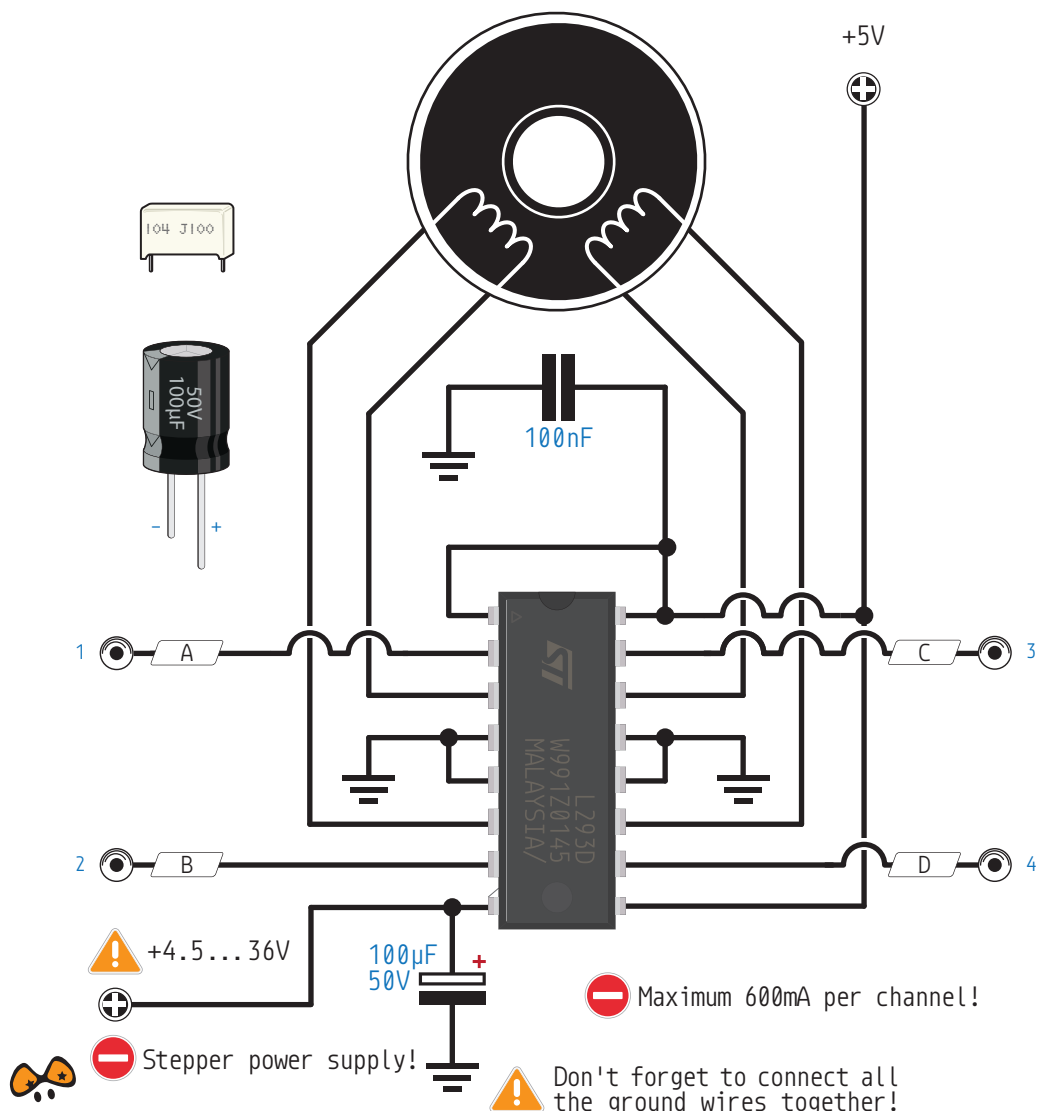



125

0-1.es/125

Bipolar Stepper Motor

Step Sequence

Full Step				
A	B	C	D	Step
				1
				2
				3
				4

HIGH LOW

Stepper motors can be driven in two different patterns or sequences: full step sequence and half step sequence. In the full step sequence, two coils are energized at the same time and the motor shaft rotates. The order in which coils have to be energized is given in the table. In the half step sequence, the motor step angle is reduced in half, therefore the number of steps and the angular resolution are doubled. Half step mode is usually preferred over full step mode. The table shows the energizing pattern of the coils.

Half Step				
A	B	C	D	Step
				1
				2
				3
				4
				5
				6
				7
				8

HIGH LOW

Step Angle

The step angle of a stepper motor is defined as the angle traversed by the stepper motor in one step. To calculate step angle simply divide 360 by the number of steps that it takes the stepper motor to complete one revolution. In half step mode, the number of steps per revolution doubles.







0-1.es/126

126

Stepper Motor

Phases

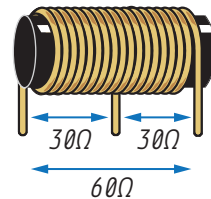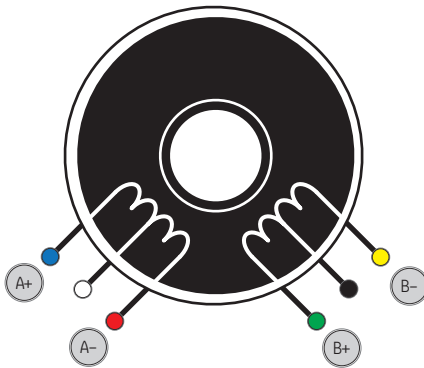It's easy to identify which color corresponds to each phase inside the stepper motor, as well as the common terminals (A and B). We assume that each coil has a resistance of 30Ω .



Use a multimeter and set it to the 200Ω range. Place the positive (+) terminal of the tester on a wire (e.g., blue) and with the negative terminal of the tester (-) begin measuring the resistance on all remaining wires.



Blue-Green



Blue-Red






126

0-1.es/126





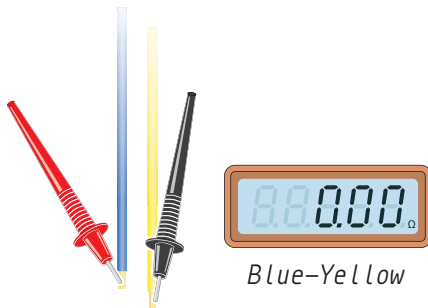

Stepper Motor













Phases



Measuring the resistance with the rest of wire combinations, we will obtain a table with all measured values:

From these measurements it can be deduced that the connections are of this type:

					
A+	B+	A-	B-	A	B

						
		∞	60Ω	∞	30Ω	∞
	∞		∞	60Ω	∞	30Ω
	60Ω	∞		∞	30Ω	∞
	∞	60Ω	∞		∞	30Ω
	30Ω	∞	30Ω	∞		∞
	∞	30Ω	∞	30Ω	∞	



B1

UNO Pinout

0-1.es/B1

+7V...+12V

PWM Pin
Port power group

Power	Serial PIN
GND	PIN Function
Physical PIN	Interrupt PIN
Port PIN	Control PIN
Analog PIN	IDC




Input voltage to the board when it's using an external power supply. Not USB bus voltage!

Logic reference voltage for shields
Connected to the 5V bus

! Absolute MAX per pin
40mA, 20mA recommended


! Absolute MAX 200mA
for the entire package

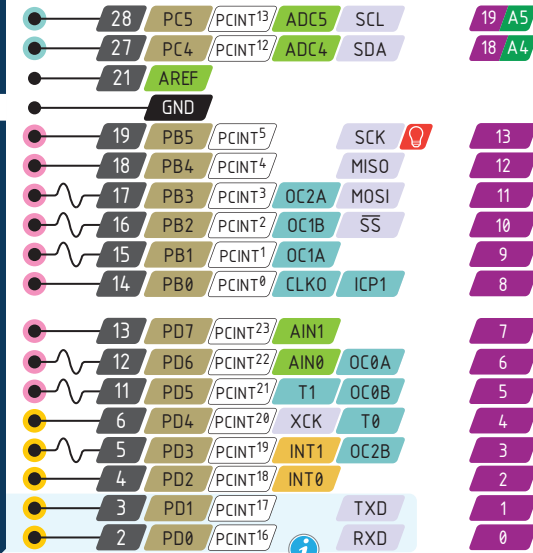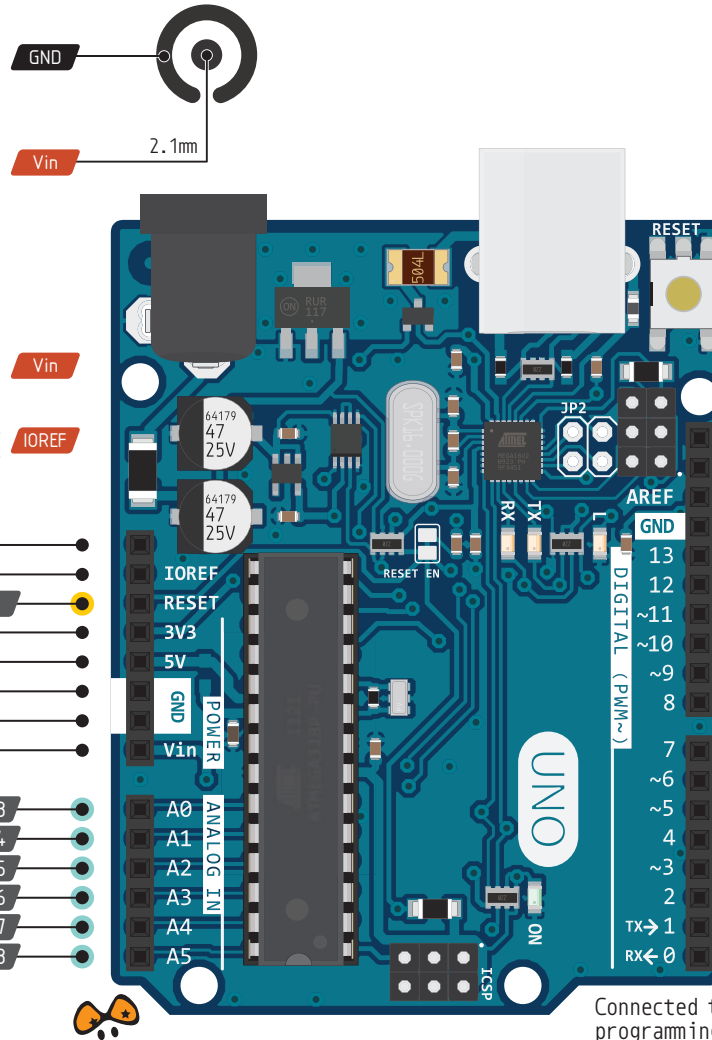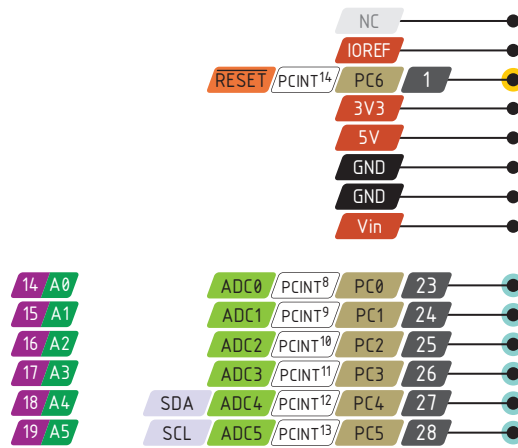! The total current of each
port power group **should**
not exceed 100mA




Connected to the ATmega and used for USB programming and communicating with it

ICSP Pinout

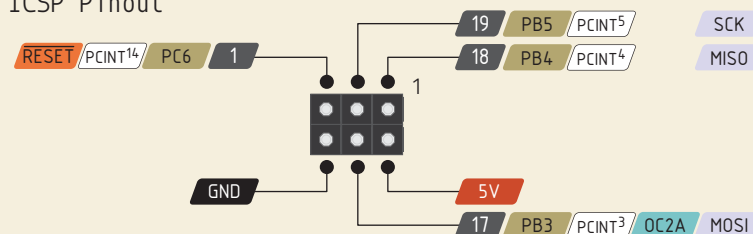

16U2 ICSP Pinout

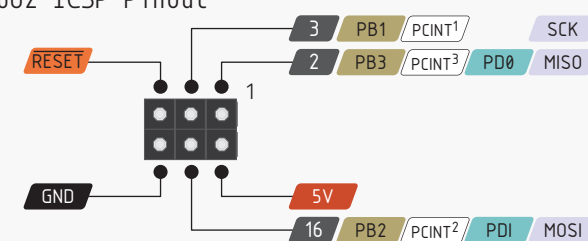

B2

0-1.es/B2


LEONARDO Pinout

Input voltage to the board when it's using an external power supply. Not USB bus voltage!

Logic reference voltage for shields
Connected to the 5V bus

18	A0	ADC7	TDI
19	A1	ADC6	TDO
20	A2	ADC5	TMS
21	A3	ADC4	TCK
22	A4	ADC1	
23	A5	ADC0	

PF7	36
PF6	37
PF5	38
PF4	39
PF1	40
PF0	41

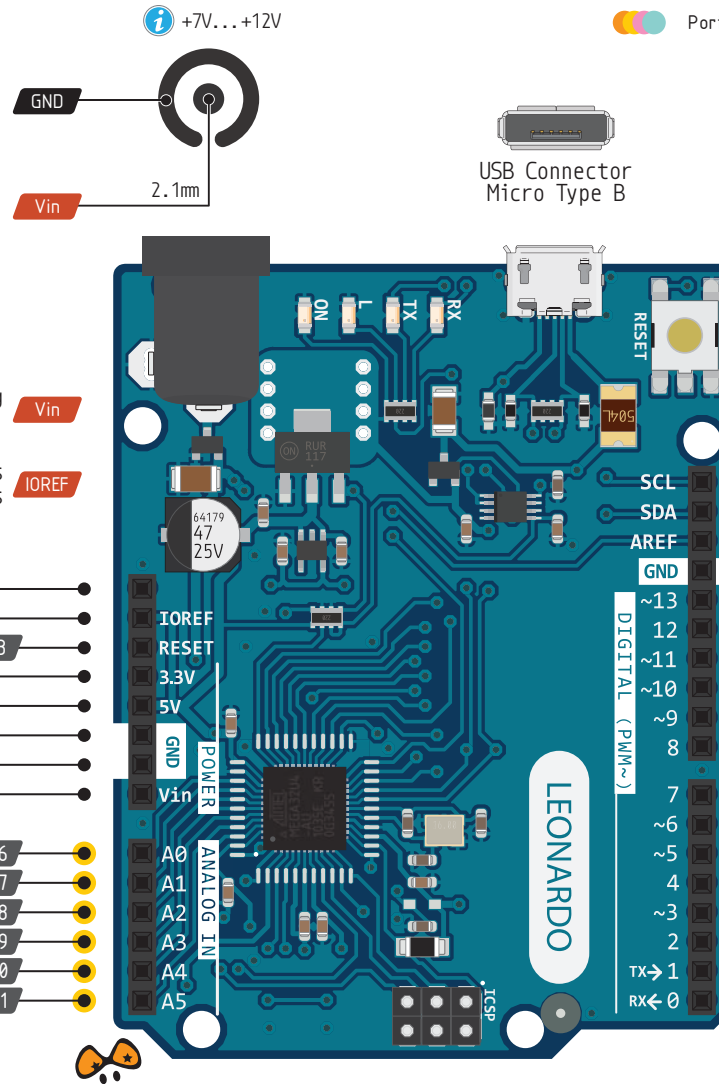

PWM Pin

Port power group

Power	Serial PIN
GND	PIN Function
Physical PIN	Interrupt PIN
Port PIN	Control PIN
Analog PIN	IDE


Absolute MAX per pin
40mA, 20mA recommended

Absolute MAX 200mA
for the entire package

The total current of each
port power group **should**
not exceed 100mA

	18	PD0	OC0B	INT0	SCL	3	
	19	PD1	INT1	SDA		2	
	42	AREF					
		GND					
	32	PC7	ICP3	OC4A	CLK0	13	
	26	PD6	T1	OC4D	ADC9	12 A11	
	12	PB7	PCINT7	OC1C	OC0A	RTS	11
	30	PB6	PCINT6	OC1B	OC4B	ADC13	10 A10
	29	PB5	PCINT5	OC1A	OC4B	ADC12	9 A9
	28	PB4	PCINT4		ADC11		8 A8
	1	PE6	AIN0	INT.6			7
	27	PD7	T0	OC4D	ADC10		6 A7
	31	PC6	OC3A	OC4A			5
	25	PD4	ICPI		ADC8		4 A6
	18	PD0	OC0B	INT0	SCL		3
	19	PD1		INT1	SDA		2
	21	PD3		INT3	TXD1		1
	20	PD2		INT2	RXD1		0

ICSP Pinout

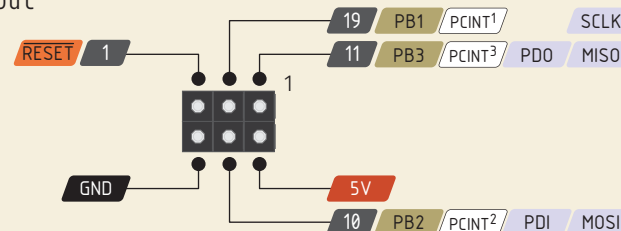

B3


0-1.es/B3

FLUO WiFi Pinout

Input voltage to the board when it's using an external power supply. Not USB bus voltage!

Logic reference voltage for shields
Connected to the 5V bus

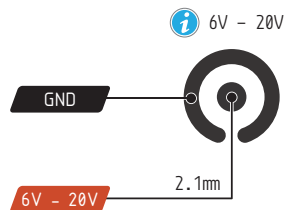The **maximum recommended** current you can draw is 750mA for 3.3V and 750mA for 5V



USB Connector
Micro Type B

ESP-32 Gateway

24	PC5	PCINT21	TDI	RX5
23	PC4	PCINT20	TD0	TX5
30	PA7	PCINT7	ADC7	ATMEGINT



Power	Serial PIN
GND	PIN Function
Physical PIN	Interrupt PIN
Port PIN	Control PIN
Analog PIN	IDE

PWM Pin

Absolute MAX per pin
40mA, 20mA recommended


Absolute MAX 200mA
for the entire package

GPIO pins rated at 5V

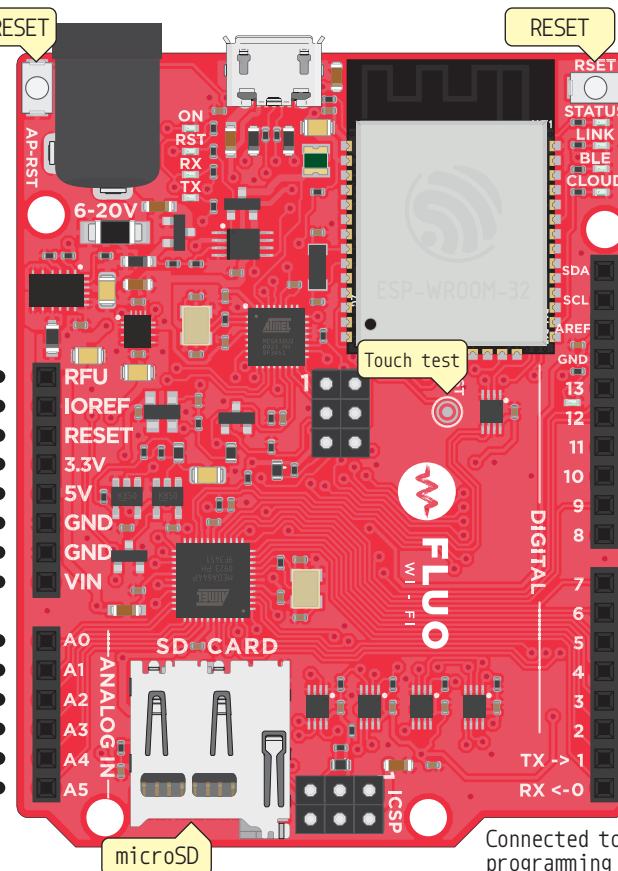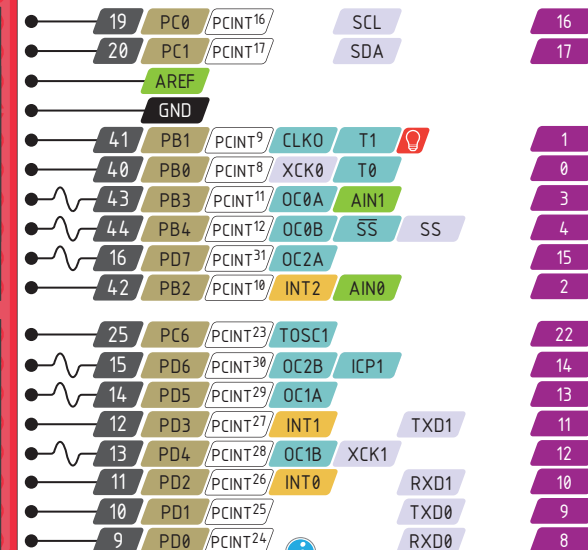


Connected to the ATmega and used for USB programming and communicating with it

ICSP Pinout

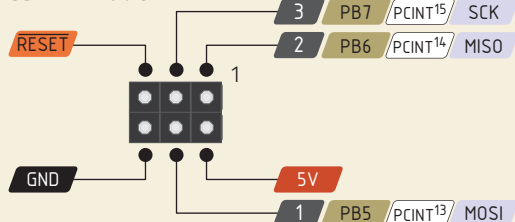

16U2 ICSP Pinout

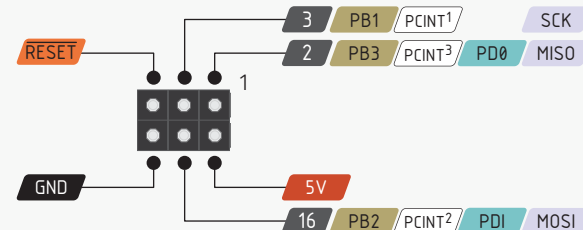


B4

0-1.es/B4

Nano Pinout


PWM Pin
Port power group

Power	Serial PIN
GND	PIN Function
Physical PIN	Interrupt PIN
Port PIN	Control PIN
Analog PIN	IDE

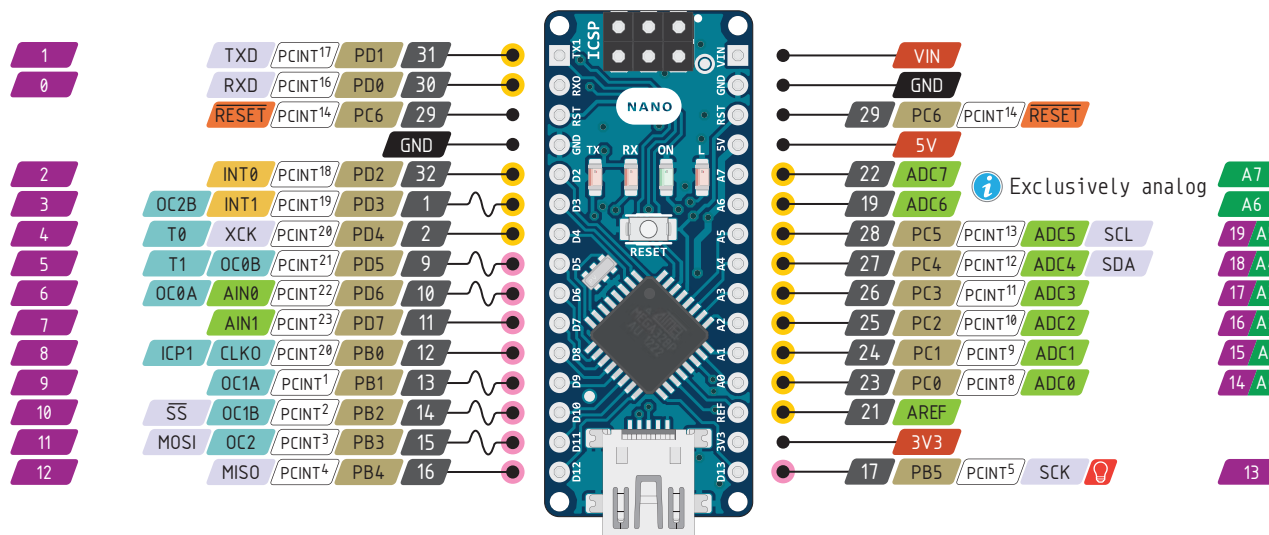

USB Connector
Mini Type B

ICSP Pinout

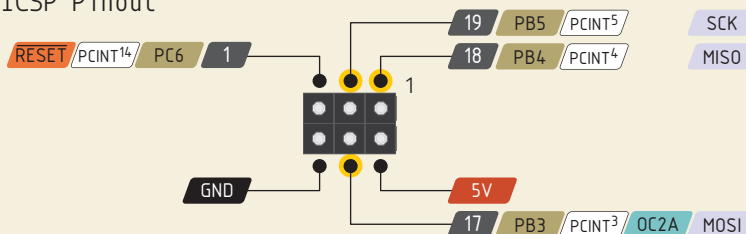

VIN Input voltage to the board when it's using an external power supply. Not USB bus voltage!

Absolute MAX per pin
40mA, 20mA recommended

Absolute MAX 200mA
for the entire package

The total current of each
port power group **should**
not exceed 100mA






B5

0-1.es/B5

NodeMCU Pinout

	Power		Serial PIN
	GND		PIN Function
	Physical PIN		Interrupt PIN
	Port PIN		Control PIN
	Analog PIN		


PWM Pin

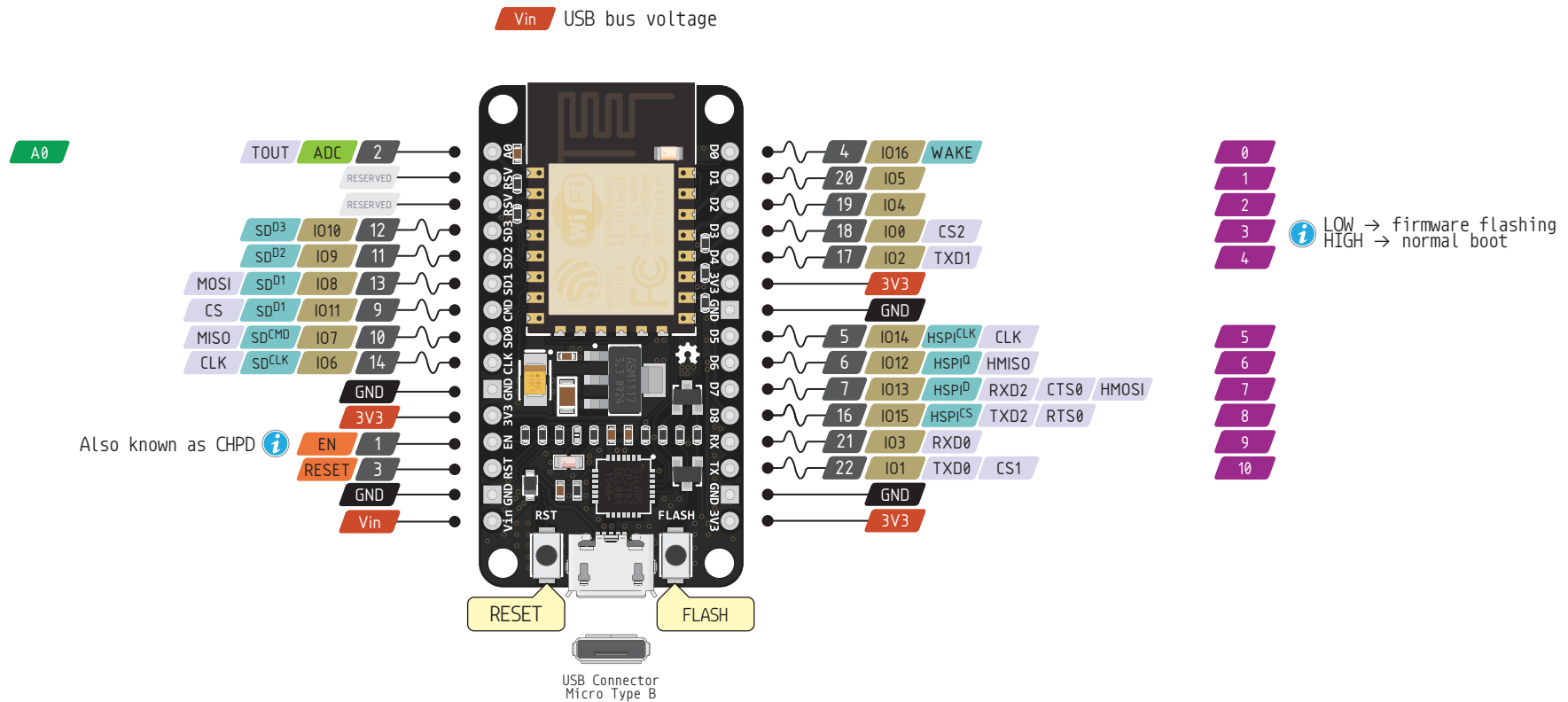

B6

0-1.es/B6


ESP-WROOM-32 Pinout

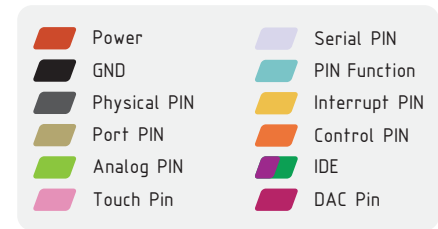

PWM Pin

Absolute MAX per pin
12mA, 6mA recommended

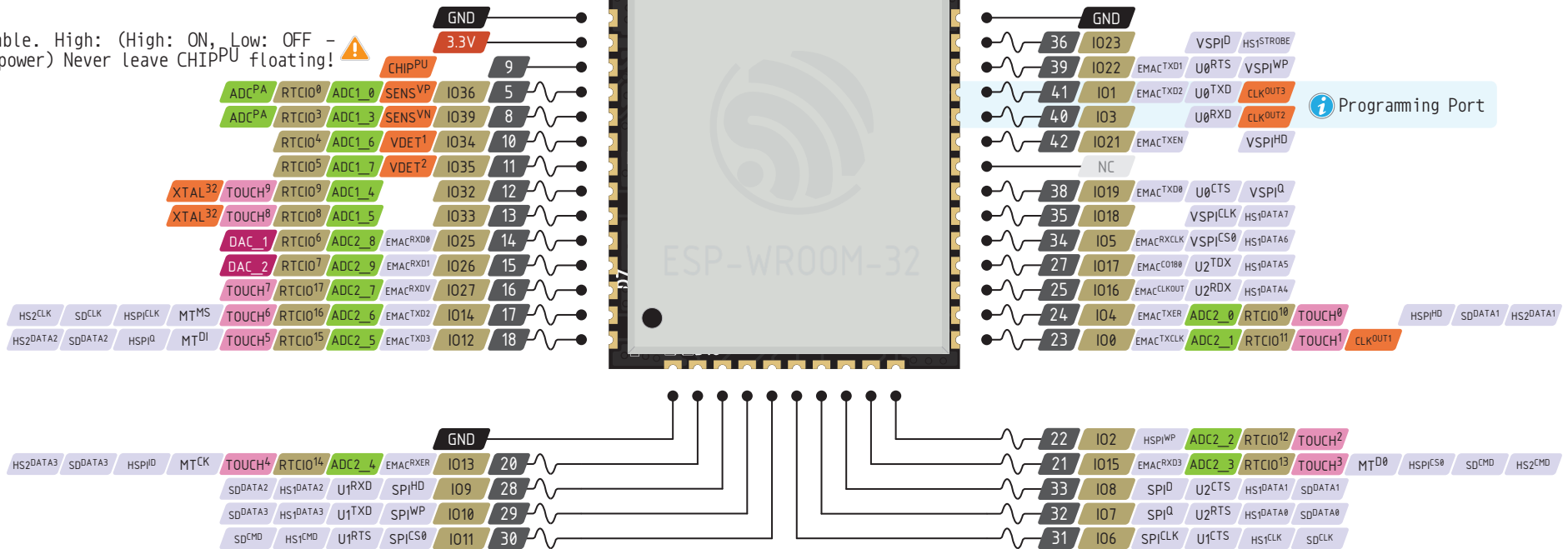Chip Enable. High: (High: ON, Low: OFF - minimum power) Never leave CHIP^{PU} floating!



B7

0-1.es/B7

DIY Microcontroller Board

Basic Connections



- Use the ICSP port to burn the bootloader
- Use the FTDI port to upload the sketch

Absolute MAX per pin
40mA, 20mA recommended

Absolute MAX per pin 200mA
for the entire package

The total current of each port
should not exceed 100mA

ICSP Connections

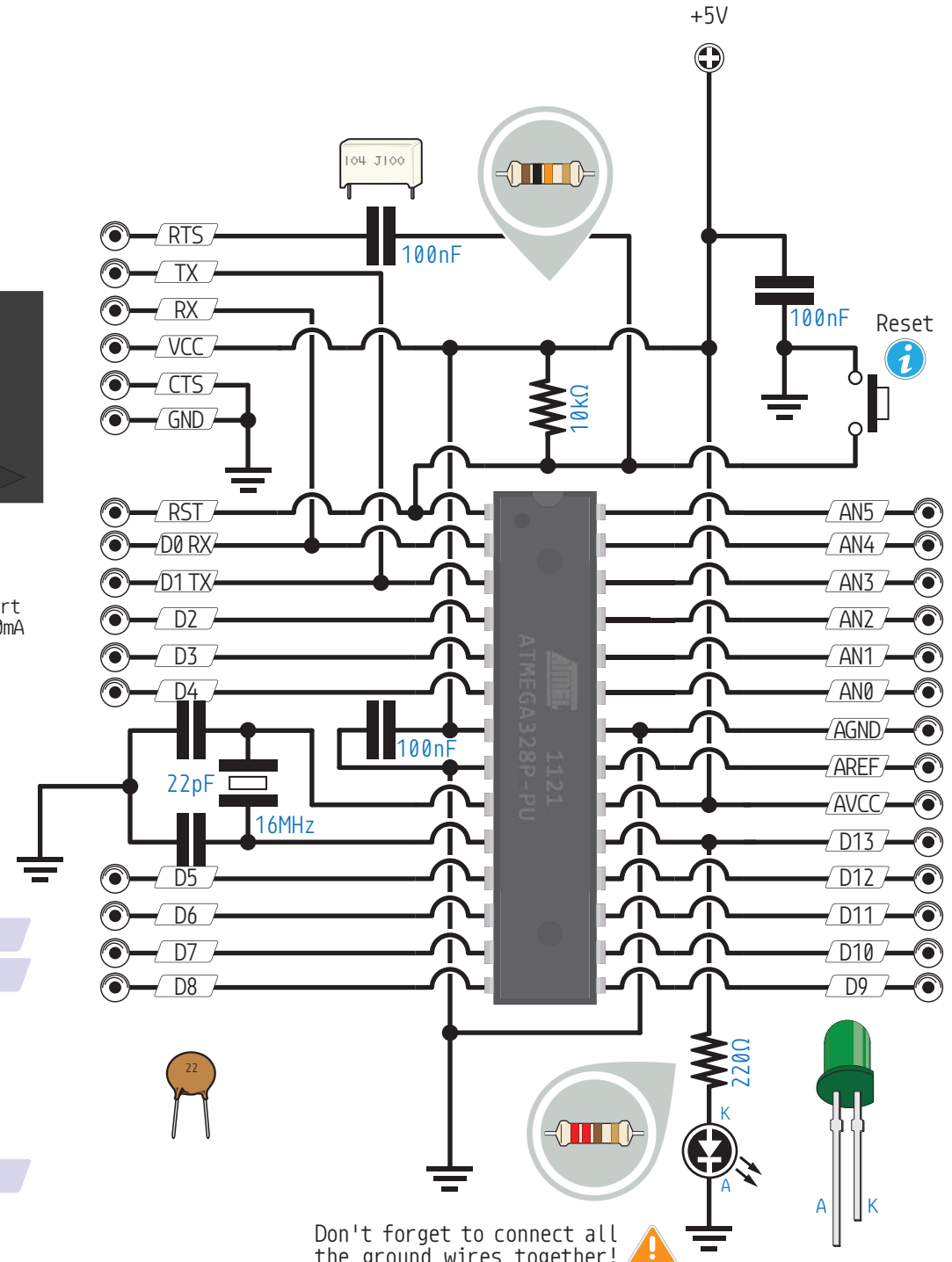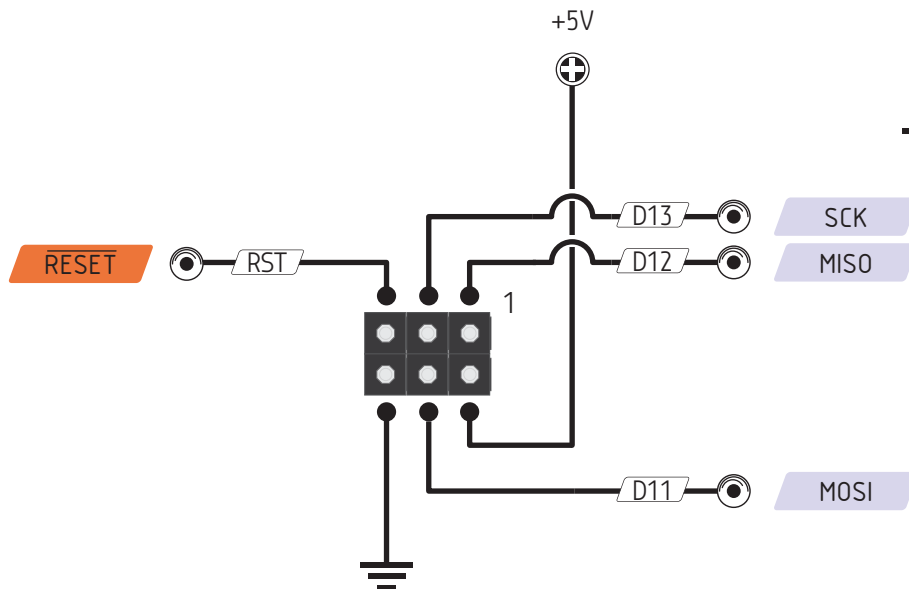

Don't forget to connect all the ground wires together!




B7


0-1.es/B7

DIY Microcontroller Board

Breadboard

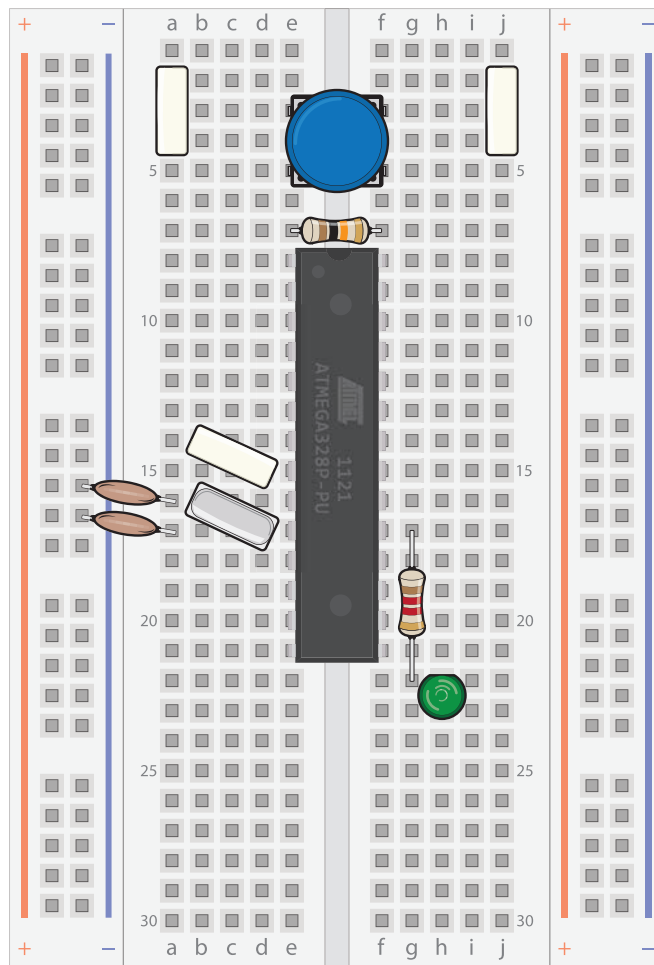

Step 1 of 2

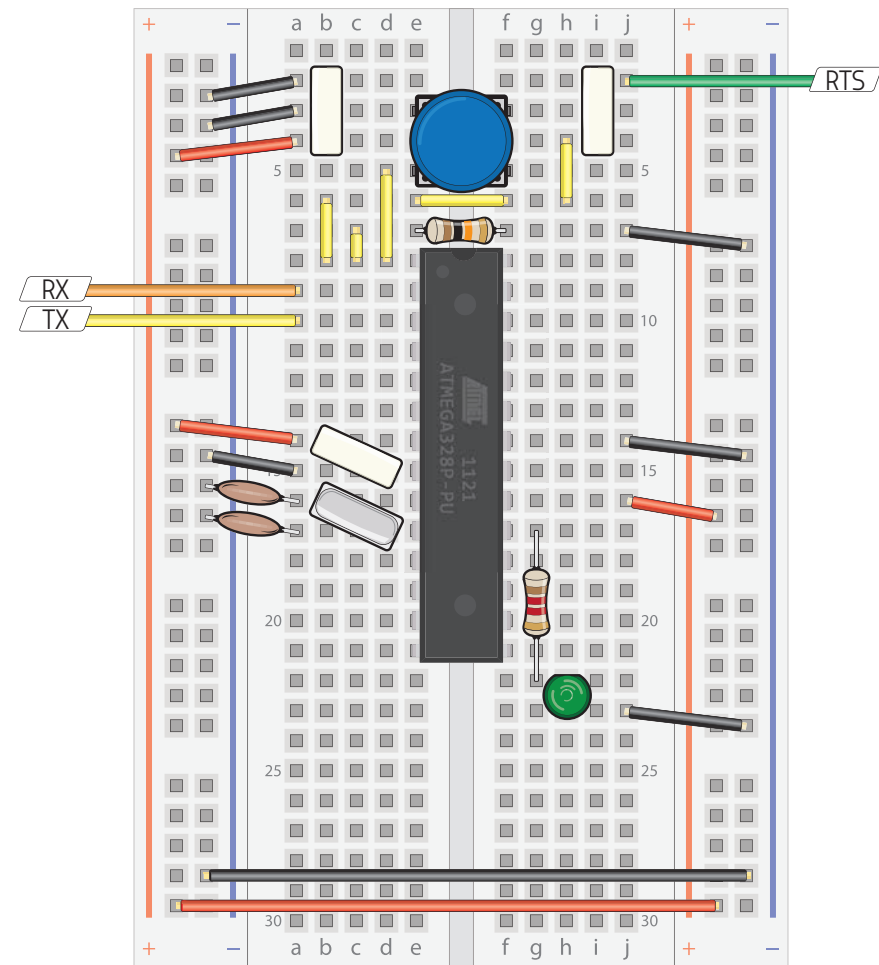

Step 2 of 2





B8


0-1.es/B8

Stepper Motor


Winding Configurations

 Not all manufacturers use the color schemes represented here, please check the datasheet


4-Lead Bipolar

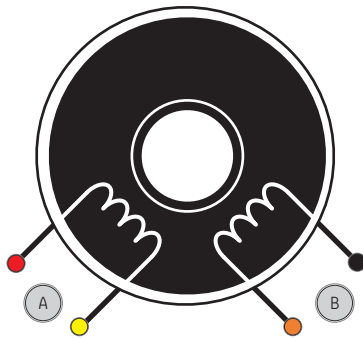


5-Lead Unipolar

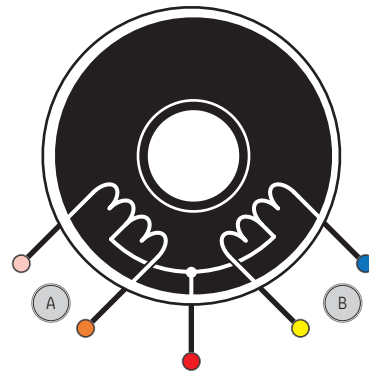


8-Lead Bipolar (Series)

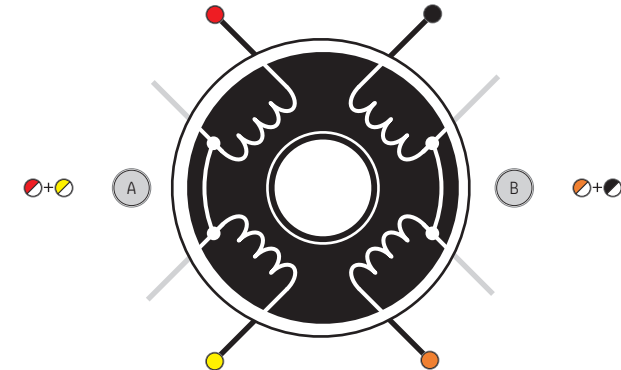


6-Lead Unipolar

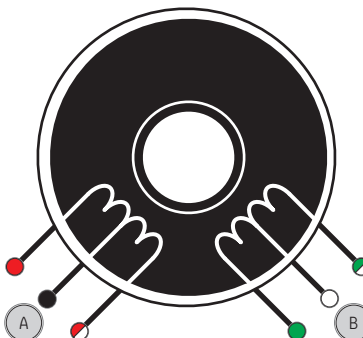


6-Lead Bipolar (Series)

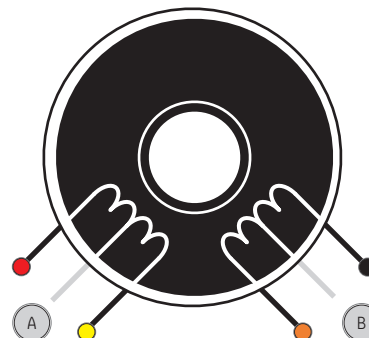

8-Lead Unipolar

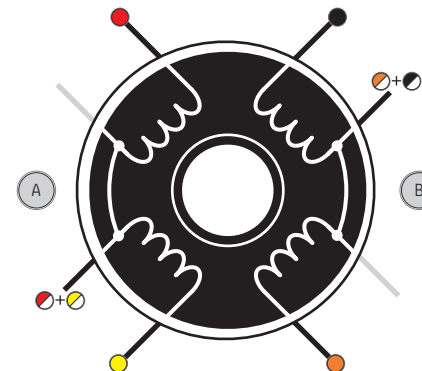

8-Lead Bipolar (Parallel)

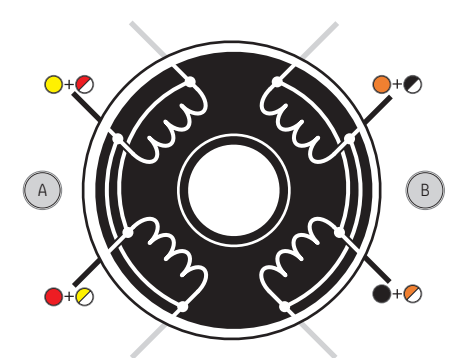



0-1.es/B9

